

Design Example Report

Title	<i>20 W Single Output, Power Factor Corrected LED Driver Using TOP247YN</i>
Specification	85 VAC – 277 VAC Input 12 V (12 V - 14 V LED Array), 1.67 A Output
Application	LED Driver
Author	Power Integrations Applications Department
Document Number	DER-167
Date	November 1, 2007
Revision	1.1

Summary and Features

- Single stage PFC based constant voltage, constant current output power supply
- Dimmable via standard phase dimmer
- Universal input range allows single design to be used worldwide
- Meets minimum PF requirement of 0.9 for industrial environment (0.9 worst case at 277 VAC)
- Meets harmonic content limits as specified in IEC 61000-3-2 for Class C
- Meets EN55015 B conducted EMI limits with >8 dB μ V margin
- Fully fault protected
 - Auto-restart withstands shorted output indefinitely
 - Integrated thermal shutdown protects the entire supply
 - Operates with no-load indefinitely
- Full load: 6 rows of 4 diodes part# LW W5SG/GYHY-5K8L-Z

PATENT INFORMATION

The products and applications illustrated herein (including transformer construction and circuits external to the products) may be covered by one or more U.S. and foreign patents, or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com. Power Integrations grants its customers a license under certain patent rights as set forth at www.powerint.com/ip.htm.

**Power Integrations**Tel: +1 408 414 9200 Fax: +1 408 414 9201
www.powerint.com

Table of Contents

1	Introduction	4
2	Power Supply Specification	5
3	Schematic	6
4	PCB Layout.....	7
5	Circuit Description.....	8
5.1	Input EMI Filtering.....	8
5.2	TOPSwitch Primary	8
5.3	Output Rectification	9
5.4	Output Feedback	9
5.4.1	Constant Voltage Operation	9
5.4.2	Constant Current Operation	10
5.4.3	Dimming	10
5.5	Soft-Start	10
6	Bill of Materials	12
7	Transformer Specification	14
7.1	Electrical Diagram.....	14
7.2	Electrical Specifications	14
7.3	Materials	14
7.4	Transformer Build Diagram.....	15
7.5	Transformer Construction	15
8	Transformer Spreadsheet.....	16
9	Performance Data.....	19
9.1	Output Characteristic.....	19
9.2	Efficiency	20
9.3	Line Regulation.....	20
9.4	Harmonic Content Chart.....	21
9.5	Harmonic Content Measurements	21
9.6	Power Factor vs. Line Voltage at Full Load	22
10	Thermal Performance.....	23
11	Waveforms	24
11.1	Drain Voltage and Current, Normal Operation.....	24
11.2	Output Voltage Start-up Profile	25
11.3	Drain Voltage and Current Start-up Profile	25
11.4	Output Ripple Measurements	26
11.4.1	Ripple Measurement Technique.....	26
11.4.2	Measurement Results.....	27
12	Conducted EMI	28
13	Revision History	29

Important Note:

Although this board is designed to satisfy safety isolation requirements, the engineering prototype has not been agency approved. Therefore, all testing should be performed using an isolation transformer to provide the AC input to the prototype board.



1 Introduction

The document presents a power supply design to be used in LED lighting applications. The design input voltage range is 85 to 277 VAC. This input can be adjusted with a phase control dimmer to control the output current of the supply and therefore to control the intensity of the LED array.

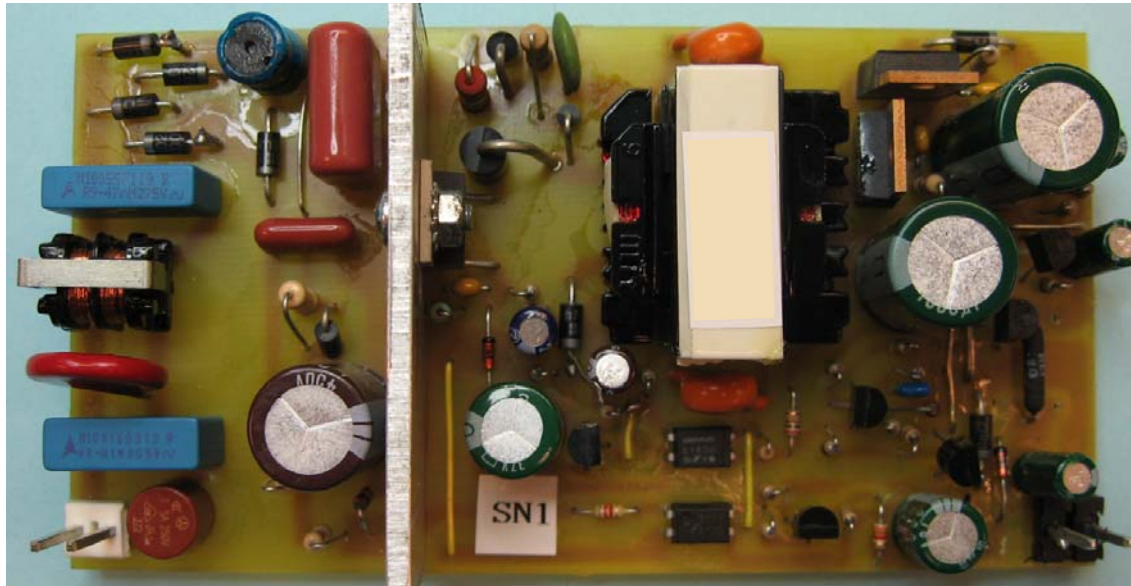


Figure 1 – Populated Circuit Board.

2 Power Supply Specification

Description	Symbol	Min	Typ	Max	Units	Comment
Input						
Voltage	V_{IN}	85		277	VAC	2 Wire – no P.E.
Frequency	f_{LINE}	47	50/60	64	Hz	
Power Factor	pf	0.95	0.97			115 VAC
Output						
Output Voltage 1	V_{OUT1}	12	14	18	V	± 5%
Output Current 1	I_{OUT1}	1.5	1.67	1.85	A	
Total Output Power						
Continuous Output Power	P_{OUT}	20			W	
Efficiency	η		80 (78)			115 (230) VAC
Environmental						
Conducted EMI						Meets EN55015B
Harmonic Content						Meets IEC-6100-3-2 Class C
Safety						Designed to meet IEC950, UL1950 Class II
Ambient Temperature	T_{AMB}	0		50	°C	Free convection, sea level



3 Schematic

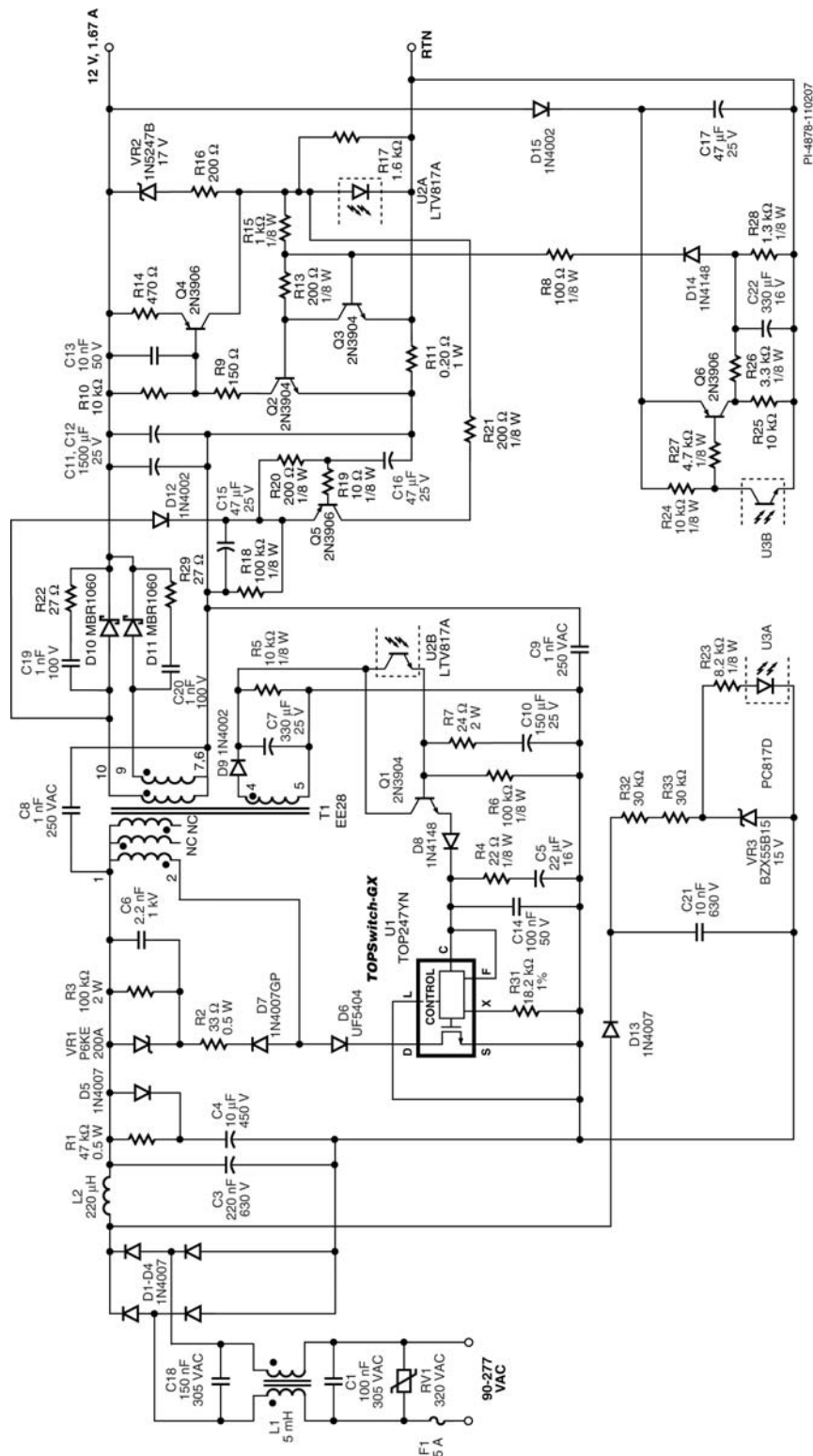


Figure 2 –Schematic.



5 Circuit Description

This design uses a discontinuous mode flyback power supply fed from an input stage with minimal capacitance. With a fixed duty cycle over an AC line cycle, this allows the peak drain current envelope, and therefore the input current, to follow the input AC voltage waveform to give high power factor and low harmonic content. Although this simple configuration gives both output regulation and power factor correction in a single stage converter, it does require higher peak drain currents compared to a standard power supply with substantiation input capacitance.

Detailed descriptions of each function block are given below.

5.1 Input EMI Filtering

In addition to the standard filtering (C1 and L1), L2 was added to provide increased differential mode filtering. This was required due to the small value of input capacitance (C3) and associated increase in switching currents seen by the AC input.

Common mode filtering is provided by L1, C8 and C9. Together with transformer E-Shields (that reduce the source of EMI common mode currents) this allowed the design to pass EN55015 B with good margin.

5.2 TOPSwitch Primary

On application of the AC input, the combination of the in-rush current to charge C1, C18 and C3, together with the inductance in the AC line, causes a voltage spike that appears across C3. In a design with a large input capacitance, this voltage is negligible; however, here the voltage spike was sufficiently large to exceed the BV_{DSS} rating of the MOSFET within TOP247YN. To prevent this, capacitor C4 and D5 limit the maximum voltage while R1 is the bleeder to discharge this capacitor on AC removal.

The discontinuous mode of operation needed for high power factor increases the primary RMS current for a given output power. By selecting a larger TOPSwitch device (TOP247YN) than needed for power delivery offsets, this increase in RMS current by reducing the $R_{DS(on)}$ conduction losses and giving higher efficiency and reduced dissipation. This was critical in this design in order to meet the maximum operating ambient of 50 °C.

As the DC input voltage across C3 falls to zero during normal operation, D6 was added in series with the drain to prevent the DRAIN ringing below SOURCE and reverse biasing the device. As reverse biasing of the device is not permitted, this diode must be used.

To provide high power factor using a single stage flyback converter, it is necessary to maintain the duty cycle of the MOSFET constant over a single AC line cycle (low bandwidth).



As the control characteristic of TOPSwitch-GX is CONTROL (C) pin current to duty cycle (of the internal MOSFET), this requires that the current into the C pin must be held constant. The simplest way to achieve this would be to use a very large value of CONTROL pin capacitance (C5). However, a large value of C5 causes a large startup time and also a large startup overshoot.

To overcome this difficulty, an emitter follower (Q1) was used as an impedance transformer with a capacitor C10 in its base. Looking into the emitter of Q1, C10 appears to be larger ($C10 \times Q1_{hfe}$), and R6 appears to be smaller ($R6 / Q1_{hfe}$). Capacitor C10, together with R6, sets the dominant pole of the circuit at approximately 0.01 Hz. Resistor R7 provides loop compensation, creating a zero at approximately 44 Hz, which gives additional phase starting at 4 Hz to improve phase margin at gain crossover. Gain crossover occurred in this design at approximately 30 Hz. Higher bandwidth is undesirable as this degrades power factor by increasing the third harmonic content in the input current waveform. Diode D8 prevents reverse current through Q1 during startup.

Feedback is provided from the secondary via optocoupler U2B, which in turn modulates the base voltage of Q1 and changes the current into the CONTROL pin.

The primary clamp circuit is formed by D7, R2, R3, C6 and VR1. During normal operation, R3 and C6 set the clamping voltage. Zener VR1 sets a defined upper clamping voltage and conducts only during startup and load transients. A standard recovery, glass passivated diode, D7, has a reverse recovery time of 2 μ s and helps recover some of the leakage energy, thereby improving efficiency. Note that the glass passivated version of the 1N4007 must be used to prevent excessive diode reverse current, unless the FR106 (500 ns) diode is substituted. Resistor R2 damps out high frequency ringing and helps reduce EMI.

5.3 Output Rectification

To reduce dissipation and increase efficiency, two output diodes were used (D10 and D11). These are connected to separate secondary windings to improve current sharing between the two diodes. Filtering is provided by C11 and C12. Relatively large values are necessary to reduce line frequency ripple that is present in the output due to the low loop bandwidth required for high power factor. These values may be reduced depending on the acceptable current ripple through the LED load.

Snubbers (R22, C19 and R29, C20) across D10 and D11 were added to reduce EMI.

5.4 Output Feedback

Output feedback is split into three functional blocks; constant voltage operation, constant current operation, and dimming.

5.4.1 Constant Voltage Operation

Voltage feedback is provided by VR2 and optocoupler U2A. Once the output exceeds the voltage defined by the forward drop of U2A, VR2 and R16, then current will flow



through the optocoupler and provide feedback to the primary. As the line and load change, the magnitude of current will change to reduce or increase the MOSFET duty cycle so as to maintain output regulation. Resistor R16 sets the loop gain in the constant voltage region.

The nominal output voltage regulation is set at 18 V, which is above the expected LED load voltage when operated at its rated current. Under normal operation, the supply will operate in constant current mode, and voltage feedback is used only when the output is unloaded.

5.4.2 Constant Current Operation

Transistor Q3 and the forward drop of the LED in U2A are used to create a bias voltage on the base on Q2. The additional drop across R11 needed to turn on Q2 is equal to the difference between the bias voltage and the V_{BE} of Q2 (~0.5 V). Once Q2 turns on, Q4 is also turned on, supplying current through U2A and providing feedback. Resistor R9 limits the base current from Q4, and R14 sets the gain of the CC loop. Resistor R10 keeps Q4 off until Q2 is on, while C13 provides loop compensation. This arrangement gave an average output current in CC operation of 0.3 A.

5.4.3 Dimming

The purpose of the dimming circuit is to control the supply output current, and therefore the intensity of the light, when a phase controlled dimmer is used at the AC input of the supply.

On the primary side of the supply, the rectified input AC is decoupled from the voltage across C3 via diode D13, and filtered by C21. Zener diode VR3 clamps the input AC waveform to 15 V, forming a pseudo square wave across R23 and U3A. Resistor R32 and R33 limit the Zener current at high line while R23 limits the opto led current.

As the phase control dimmer reduces the conduction angle, the opto couple conduction duty cycle also reduces.

On the secondary side, the duty cycle signal is inverted by Q6 and averaged by C22, R26 and R28. The amplitude of the voltage across C22 is directly proportional to the conduction angle of the input voltage and is used to control the output current by adjusting the CC threshold voltage across R11 (via D14 and R8). The larger the conduction angle of the AC line voltage, the higher the CC threshold and supply output current, then the higher the intensity of the light.

5.5 Soft-Start

The very low loop bandwidth presents a problem at startup. Once the loop closes and feedback is provided via U2A, it takes significant time for the loop to respond and therefore allows a significant output overshoot. This is due to the need for C10 to charge above 5.8 V before current will be supplied into the CONTROL pin of U1.



The standard solution to output overshoot is to provide a soft-finish circuit. Typically this consists of a capacitor that allows current to flow in the feedback loop before the output has reached regulation. Here such a passive approach is not practical because of the size of capacitor that would be required.

To overcome this, the circuit formed around Q5 is used to overdrive the feedback loop during startup. Using an element with gain (Q5) allows high enough feedback current to pre-charge C10 before the output reaches regulation.

A separate auxiliary supply is created by D12 and C15 so that the voltage across C15 rises faster than the main output across C11 and C12. While C16 charges, Q5 is on, supplying current to charge C10 via the optocoupler, with resistor R21 limiting the maximum current. Once the voltage across C16 reaches $V_O - V_{BE(Q5)}$, Q5 turns off and the circuit becomes inactive. At power down, C16 is discharged via R18, resetting the circuit for the next power-up. The time constant of C16 and R18 appears very long; however, in practice, C10 also takes a significant time to discharge on power down, and even momentary AC drop outs do not result in any output overshoot.



6 Bill of Materials

Item	Qty	Part Ref	Value	Description	Mfg Part Number	Mfg
1	1	C1	100 nF	100 nF, 305 VAC, X2	B32922A2104M	Epcos
2	1	C3	220 nF	220 nF, 630 V, Film	ECQ-E6224KF	Panasonic
3	1	C4	10 μ F	10 uF, 450 V, Electrolytic, (12.5 x 20)	EKMG451ELL100MK20S	United Chemi-Con
4	1	C5	22 μ F	22 uF, 16 V, Electrolytic, Gen. Purpose, (5 x 11)	ECA1CM220	Panasonic
5	1	C6	2.2 nF	2.2 nF, 1 kV, Disc Ceramic	NCD222K1KVY5FF	NIC Components Corp
6	1	C7	330 μ F	330 uF, 25 V, Electrolytic, Very Low ESR, 53 m Ω , (10 x 12.5)	EKZE250ELL331MJC5S	Nippon Chemi-Con
7	2	C8 C9	1 nF	1 nF, Ceramic, Y1	440LD10-R	Vishay
8	1	C10	150 μ F	150 uF, 25 V, Electrolytic, Low ESR, 180 m Ω , (6.3 x 15)	ELXZ250ELL151MF15D	Nippon Chemi-Con
9	2	C11 C12	1500 μ F	1500 μ F, 25 V, Electrolytic, Very Low ESR, 18 m Ω , (12.5 x 25)	EKZE250ELL152MK25S	Nippon Chemi-Con
10	1	C13	10 nF	10 nF, 50 V, Ceramic, Z5U	B37982N5103M000	Epcos
11	1	C14	100 nF	100 nF, 50 V, Ceramic, X7R	B37987F5104K000	Epcos
12	3	C15 C16 C17	47 μ F	47 μ F, 25 V, Electrolytic, Very Low ESR, 300 m Ω , (5 x 11)	EKZE250ELL470ME11D	Nippon Chemi-Con
13	1	C18	150 nF	150 nF, 305 VAC, X2	B32922A2154M	Epcos
14	2	C19 C20	1 nF	1 nF, 100 V, Ceramic, COG	B37979G1102J000	Epcos
15	1	C21	10 nF	10 nF, 630 V, Film	ECQ-E6103KF	Panasonic
16	1	C22	330 μ F	330 μ F, 16 V, Electrolytic, Low ESR, 120 m Ω , (8 x 12)	ELXZ160ELL331MH12D	Nippon Chemi-Con
17	5	D1 D2 D3 D4 D13	1N4007	1000 V, 1 A, Rectifier, DO-41	1N4007	Vishay
18	1	D5	1N4007	1000 V, 1 A, Rectifier, DO-41	1N4007-E3/54	Vishay
19	1	D6	UF5404	400 V, 3 A, Ultrafast Recovery, 75 ns, DO-201AD	UF5404-E3	Vishay
20	1	D7	1N4007GP	1000 V, 1 A, Rectifier, Glass Passivated, 2 us, DO-41	1N4007GP	Vishay
21	2	D8 D14	1N4148	75 V, 300 mA, Fast Switching, DO-35	1N4148	Vishay
22	3	D9 D12 D15	1N4002	100 V, 1 A, Rectifier, DO-41	1N4002	Vishay
23	2	D10 D11	MBR1060	60 V, 10 A, Schottky, TO-220AC	MBR1060	Vishay
24	1	F1	5 A	5 A, 250V, Slow, TR5	3721500041	Wickman
25	1	HS1	HEATSINK	HEATSINK, Alum, TO-220 2 hole, 2 mtg pins		Power Integrations
26	2	J1 J2	CON2	2 Position (1 x 2) header, 0.156 pitch, Vertical	26-48-1021	Molex



27	1	L1	5 mH	5 mH, 0.3 A, Common Mode Choke	SU9V-03050	Tokin
28	1	L2	220 μ H	220 μ H, 0.68 A, 9 x 11.5 mm	SBC3-221-681	Tokin
29	3	Q1 Q2 Q3	2N3904	NPN, Small Signal BJT, 40 V, 0.2 A, TO-92	2N3904RLRAG	On Semiconductor
30	3	Q4 Q5 Q6	2N3906	PNP, Small Signal BJT, 40 V, 0.2 A, TO-92	2N3906	Fairchild
31	1	R1	47 k	47 k, 5%, 1/2 W, Carbon Film	CFR-50JB-47K	Yageo
32	1	R2	33	33 R, 5%, 1/2 W, Carbon Film	CFR-50JB-33R	Yageo
33	1	R3	100 k	100 k, 5%, 2 W, Metal Oxide	RSF200JB-100K	Yageo
34	1	R4	22	22 R, 5%, 1/8 W, Carbon Film	CFR-12JB-22R	Yageo
35	4	R5 R10 R24 R25	10 k	10 k, 5%, 1/8 W, Carbon Film	CFR-12JB-10K	Yageo
36	2	R6 R18	100 k	100 k, 5%, 1/8 W, Carbon Film	CFR-12JB-100K	Yageo
37	1	R7	24	24 R, 5%, 1/8 W, Carbon Film	CFR-12JB-24R	Yageo
38	1	R8	100	100 R, 5%, 1/8 W, Carbon Film	CFR-12JB-91R	Yageo
39	1	R9	150	150 R, 5%, 1/8 W, Carbon Film	CFR-12JB-150R	Yageo
40	1	R11	0.20	0.20 R, 1%, 1 W	2306 327 52007	Phonex
41	4	R13 R16 R20 R21	200	200 R, 5%, 1/8 W, Carbon Film	CFR-12JB-200R	Yageo
42	1	R14	470	470 R, 5%, 1/8 W, Carbon Film	CFR-12JB-470R	Yageo
43	1	R15	1 k	1 k, 5%, 1/8 W, Carbon Film	CFR-12JB-1K0	Yageo
44	1	R17	1.6 k	1.6 k, 5%, 1/8 W, Carbon Film	CFR-12JB-1K6	Yageo
45	1	R19	10	10 R, 5%, 1/8 W, Carbon Film	CFR-12JB-10R	Yageo
46	2	R22 R29	27	27 R, 5%, 1/4 W, Carbon Film	CFR-25JB-27R	Yageo
47	1	R23	8.2 k	8.2 k, 5%, 1/8 W, Carbon Film	CFR-12JB-8K2	Yageo
48	1	R26	3.3 k	3.3 k, 5%, 1/8 W, Carbon Film	CFR-12JB-3K3	Yageo
49	1	R27	4.7 k	4.7 k, 5%, 1/8 W, Carbon Film	CFR-12JB-4K7	Yageo
50	1	R28	1.3 k	1.3 k, 5%, 1/8 W, Carbon Film	CFR-12JB-1K3	Yageo
51	1	R31	18.2 k	18.2 k, 1%, 1/4 W, Metal Film	MFR-25FBF-18K2	Yageo
52	2	R32 R33	30 k	30 k, 5%, 1/4 W, Carbon Film	CFR-25JB-30K	Yageo
53	1	RV1	320 Vac	320V, 84J, 15.5 mm, RADIAL	S14K320	Epcos
54	1	T1	EE28	Bobbin, EE28. Vertical, Extended creepage, 10 pins	YW-490-00B	Yih-Hwa Enterprises
55	1	U1	TOP247YN	TOPSwitch-GX, TOP247YN, TO220-7C	TOP247YN	Power Integrations
56	1	U2	LTV817A	Optocoupler, 35 V, CTR 80-160%, 4-DIP	LTV-817A	Liteon
57	1	U3	PC817D	Optocoupler, 35 V, CTR 300-600%, 4-DIP	PC817X4	Sharp
58	1	VR1	P6KE200A	200 V, 600 W, 5%, TVS, DO204AC (DO-15)	P6KE200ARLG	OnSemi
59	1	VR2	1N5247B	17 V, 5%, 500 mW, DO-35	1N5247B	Microsemi
60	1	VR3	BZX55B15	15 V, 500 mW, 2%, DO-35	BZX55B15	Vishay



7 Transformer Specification

7.1 Electrical Diagram

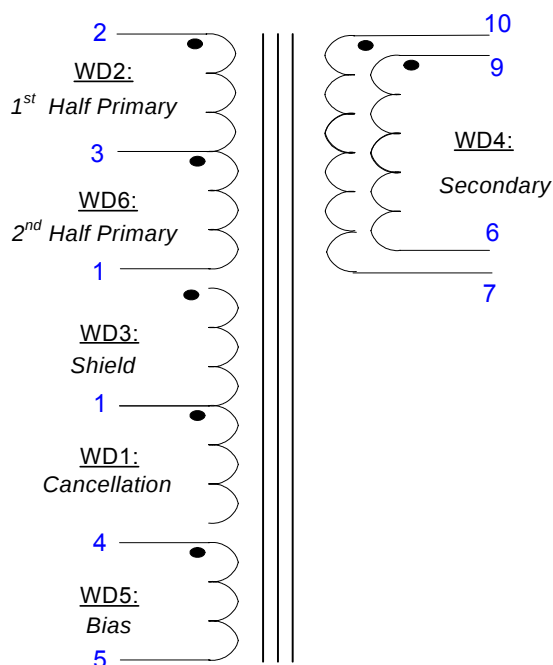


Figure 4 – Transformer Electrical Diagram.

7.2 Electrical Specifications

Electrical Strength	60 second, 60 Hz, from Pins 1-5 to Pins 6-10.	3000 VAC
Primary Inductance	Pins 1-2, all other windings open, measured at 100 kHz.	724 μ H, -0/+10%
Resonant Frequency	Pins 1-2, all other windings open.	855 kHz (Min.)
Primary Leakage Inductance	Pins 1-2, with Pins 6-7-8-9-10 shorted, measured at 100 kHz.	10 μ H (Max.)

7.3 Materials

Item	Description
[1]	Core: EE28 PC40 or equivalent gapped for 452 nH/T ²
[2]	Bobbin: Vertical EE28 10 pins, safety rated.
[3]	Magnet Wire: 33AWG
[4]	Magnet Wire: 27AWG
[5]	Magnet Wire: 25AWG
[6]	Magnet Wire: 30AWG
[7]	Triple Insulated Wire: 23AWG
[8]	Tape: 9.6 mm
[9]	Varnish



7.4 Transformer Build Diagram

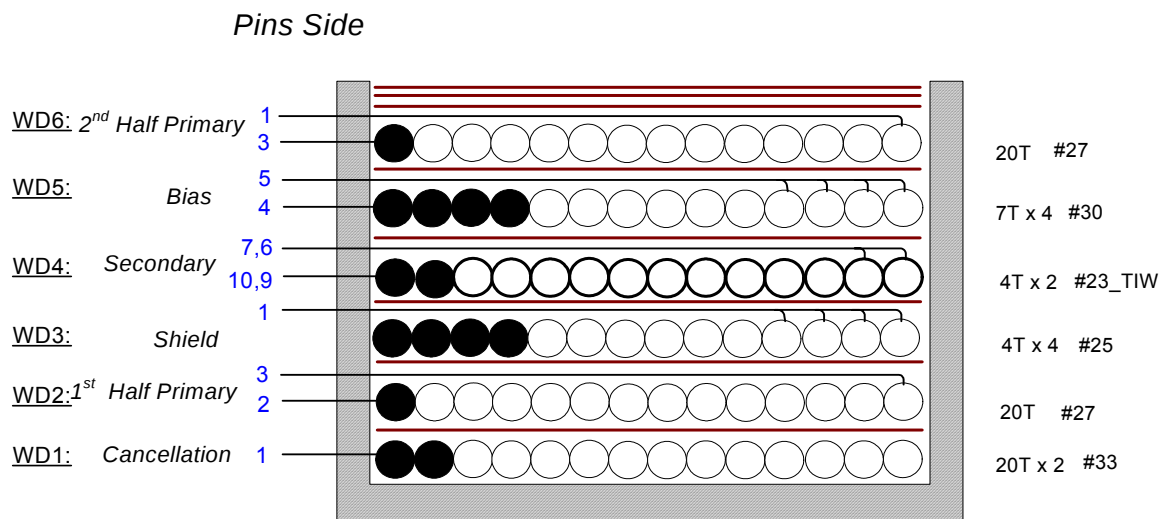


Figure 5 – Transformer Build Diagram.

7.5 Transformer Construction

Bobbin Preparation	Place Bobbin, item [2], on the winding machine with pins side oriented to the left hand side.
WD1 Core Cancellation	Start at pin 1, wind from left to right 20 bifilar turns of item [3] in a uniform, tightly wound layer. Cut finish lead at the end of the winding.
Tape	Use 1 layer of tape, item [8], to hold the winding.
WD2 First Half Primary	Start at pin 2, wind from left to right 20 turns of item [4] in a uniform, tightly wound layer. Finish at pin 3.
Tape	Use 1 layer of tape, item [8], to hold the winding.
WD3 Shield	Using 4 parallel wires of item [5], attach starting lead temporarily to pin 3. Wind 4 quad-filar turns from left to right in a uniform, tightly layer. Finish at pin 1. Disconnect the starting wire from pin 3 and cut it at the starting of the winding.
Tape	Use 1 layer of tape, item [8], to hold the winding.
WD4 Secondary	Start at pins 10 and 9 using 2 wires of item [7]. Wind 4 turns of parallel wires from left to right in a single layer. Finish at pins 7 and 6 respectively.
Tape	Use 1 layer of tape, item [8], to hold the winding.
WD6 Bias	Start at pin 4, wind 7 quad-filar turns of item [6] from left to right in a single and tight layer. Finish at pin 5.
WD7 Second Half Primary.	Start at pin 3, wind from left to right 20 turns of item [4] in a uniform, tightly wound layer. Finish at pin 1.
Tape	Use 3 layer of tape, item [8].
Final Assembly	Assemble and secure core halves with bobbin. Varnish impregnate item [9].

8 Transformer Spreadsheet

ACDC_TOPSwitchGX_043007; Rev.2.15; Copyright Power Integrations 2007	INPUT	INFO	OUTPUT	UNIT	TOP_GX_FX_043007: TOPSwitch-GX/FX Continuous/Discontinuous Flyback Transformer Design Spreadsheet
ENTER APPLICATION VARIABLES					Design with 85-277VAC EE28 HF
VACMIN	85			Volts	Minimum AC Input Voltage
VACMAX	277			Volts	Maximum AC Input Voltage
fL	50			Hertz	AC Mains Frequency
VO	12.00			Volts	Output Voltage (main)
PO	33.00			Watts	Output Power
n	0.80				Efficiency Estimate
Z	0.50				Loss Allocation Factor
VB	20			Volts	Bias Voltage
tC	3.00			mSeconds	Bridge Rectifier Conduction Time Estimate
CIN	99999.00			uFarads	Input Filter Capacitor
ENTER TOPSWITCH-GX VARIABLES					
TOP-GX	TOP247			Universal	115 Doubled/230V
Chosen Device		TOP247	Power Out	125W	165W
KI	0.44				External Ilimit reduction factor (KI=1.0 for default ILIMIT, KI <1.0 for lower ILIMIT)
ILIMITMIN			1.426	Amps	Use 1% resistor in setting external ILIMIT
ILIMITMAX			1.742	Amps	Use 1% resistor in setting external ILIMIT
Frequency (F)=132kHz, (H)=66kHz					Half (H) frequency option - 66kHz
fS			66000	Hertz	TOPSwitch-GX Switching Frequency: Choose between 132 kHz and 66 kHz
fSmin			61500	Hertz	TOPSwitch-GX Minimum Switching Frequency
fSmax			70500	Hertz	TOPSwitch-GX Maximum Switching Frequency
VOR	125.00			Volts	Reflected Output Voltage
VDS	10.00			Volts	TOPSwitch on-state Drain to Source Voltage
VD	0.50			Volts	Output Winding Diode Forward Voltage Drop
VDB	0.70			Volts	Bias Winding Diode Forward Voltage Drop
KP	1.00				Ripple to Peak Current Ratio (0.4 < KRP < 1.0 : 1.0 < KDP < 6.0)
ENTER TRANSFORMER CORE/CONSTRUCTION VARIABLES					
Core Type	EI28				
Core		EI28	P/N:		PC40EI28-Z
Bobbin		EI28_BO BBIN	P/N:		BE-28-1110CPL
AE			0.86	cm^2	Core Effective Cross Sectional Area



LE			4.82	cm	Core Effective Path Length
AL			4300	nH/T ²	Ungapped Core Effective Inductance
BW			9.6	mm	Bobbin Physical Winding Width
M	0.00			mm	Safety Margin Width (Half the Primary to Secondary Creepage Distance)
L	2.00				Number of Primary Layers
NS	4				Number of Secondary Turns
DC INPUT VOLTAGE PARAMETERS					
VMIN			120	Volts	Minimum DC Input Voltage
VMAX			392	Volts	Maximum DC Input Voltage
CURRENT WAVEFORM SHAPE PARAMETERS					
DMAX			0.53		Maximum Duty Cycle
IAVG			0.34	Amps	Average Primary Current
IP			1.29	Amps	Peak Primary Current
IR			1.29	Amps	Primary Ripple Current
IRMS			0.54	Amps	Primary RMS Current
TRANSFORMER PRIMARY DESIGN PARAMETERS					
LP			724	uHenries	Primary Inductance
NP			40		Primary Winding Number of Turns
NB			7		Bias Winding Number of Turns
ALG			452	nH/T ²	Gapped Core Effective Inductance
BM			2717	Gauss	Maximum Flux Density at PO, VMIN (BM<3000)
BP			3666	Gauss	Peak Flux Density (BP <4200)
BAC			1359	Gauss	AC Flux Density for Core Loss Curves (0.5 X Peak to Peak)
ur			1918		Relative Permeability of Ungapped Core
LG			0.21	mm	Gap Length (Lg > 0.1 mm)
BWE			19.2	mm	Effective Bobbin Width
OD			0.48	mm	Maximum Primary Wire Diameter including insulation
INS			0.06	mm	Estimated Total Insulation Thickness (= 2 * film thickness)
DIA			0.42	mm	Bare conductor diameter
AWG			26	AWG	Primary Wire Gauge (Rounded to next smaller standard AWG value)
CM			256	Cmils	Bare conductor effective area in circular mils
CMA			471	Cmils/Amp	Primary Winding Current Capacity (200 < CMA < 500)



TRANSFORMER SECONDARY DESIGN PARAMETERS (SINGLE OUTPUT EQUIVALENT)					
Lumped parameters					
ISP			12.92	Amps	Peak Secondary Current
ISRMS			5.10	Amps	Secondary RMS Current
IO			2.75	Amps	Power Supply Output Current
IRIPPLE			4.30	Amps	Output Capacitor RMS Ripple Current
CMS			1021	Cmils	Secondary Bare Conductor Minimum Circular Mils
AWGS			20	AWG	Secondary Wire Gauge (Rounded up to next larger standard AWG value)
DIAS			0.81	mm	Secondary Minimum Bare Conductor Diameter
ODS			2.40	mm	Secondary Maximum Outside Diameter for Triple Insulated Wire
INSS			0.79	mm	Maximum Secondary Insulation Wall Thickness
VOLTAGE STRESS PARAMETERS					
VDRAIN			674	Volts	Maximum Drain Voltage Estimate (Includes effect of leakage inductance)
PIVS			51	Volts	Output Rectifier Maximum Peak Inverse Voltage
PIVB			85	Volts	Bias Rectifier Maximum Peak Inverse Voltage



9 Performance Data

All measurements performed at room temperature, 60 Hz input frequency.

9.1 Output Characteristic

As LED arrays have a defined operating range, the CC circuit does not have to maintain operation down to a short circuit. During a output short, the power supply enters auto-restart, reducing output power to ~3% of maximum.

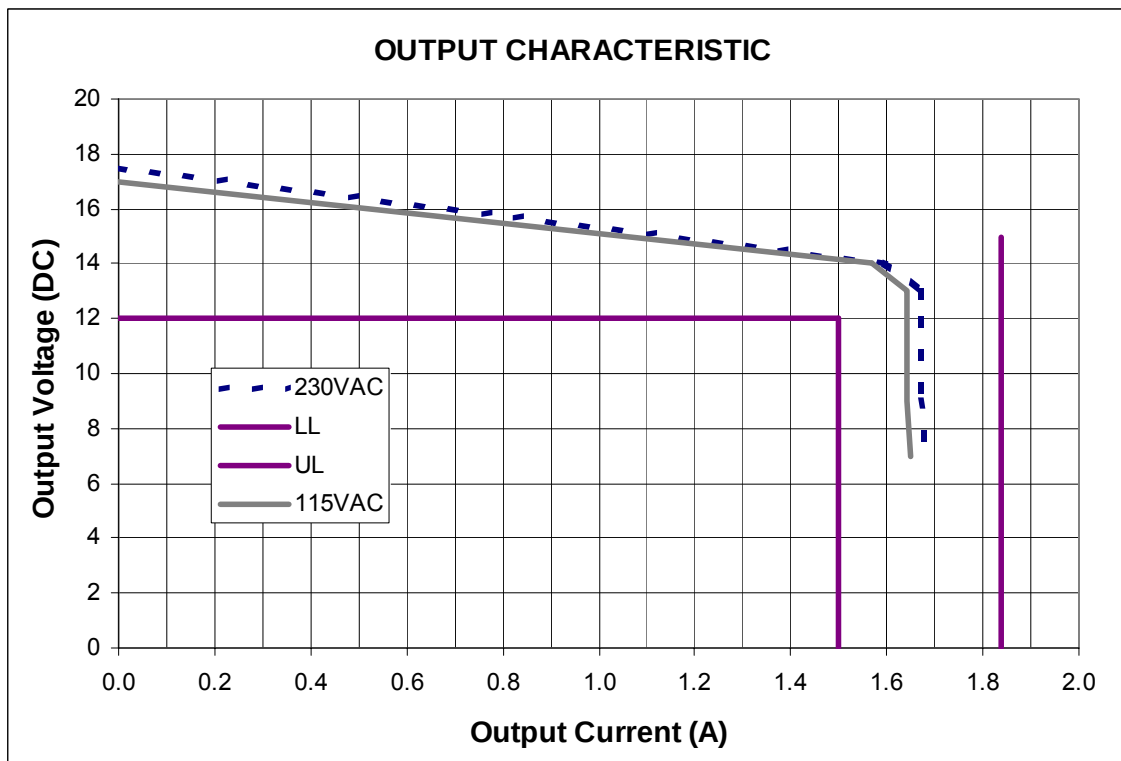


Figure 6 – Output Characteristic, Including Limits.

9.2 Efficiency

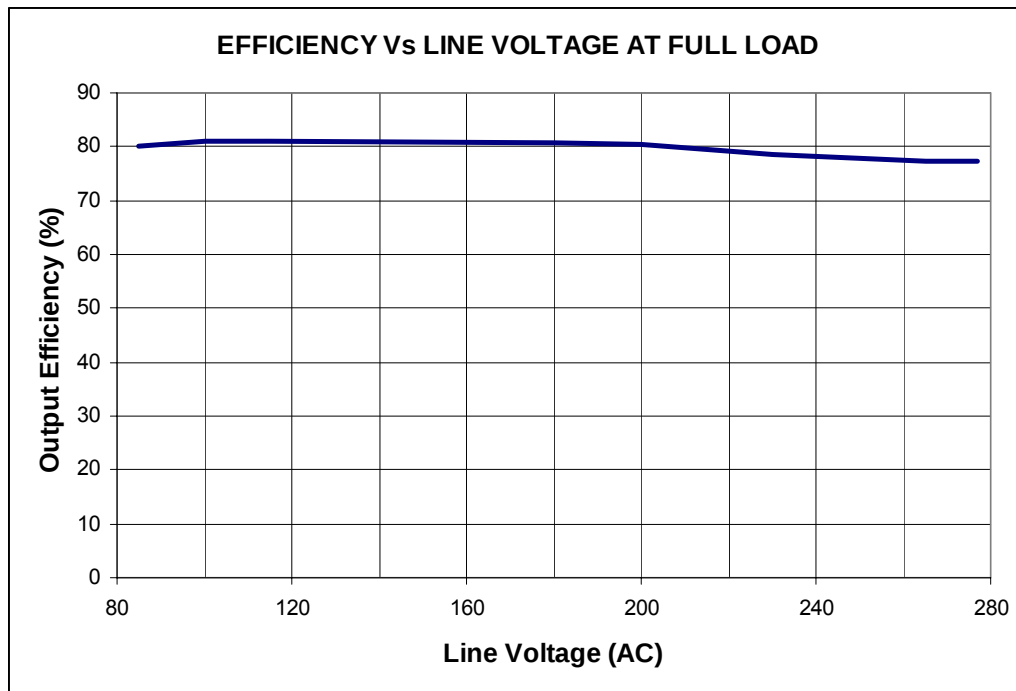


Figure 7 – Efficiency vs. Input Voltage, Room Temperature, 60 Hz.

9.3 Line Regulation

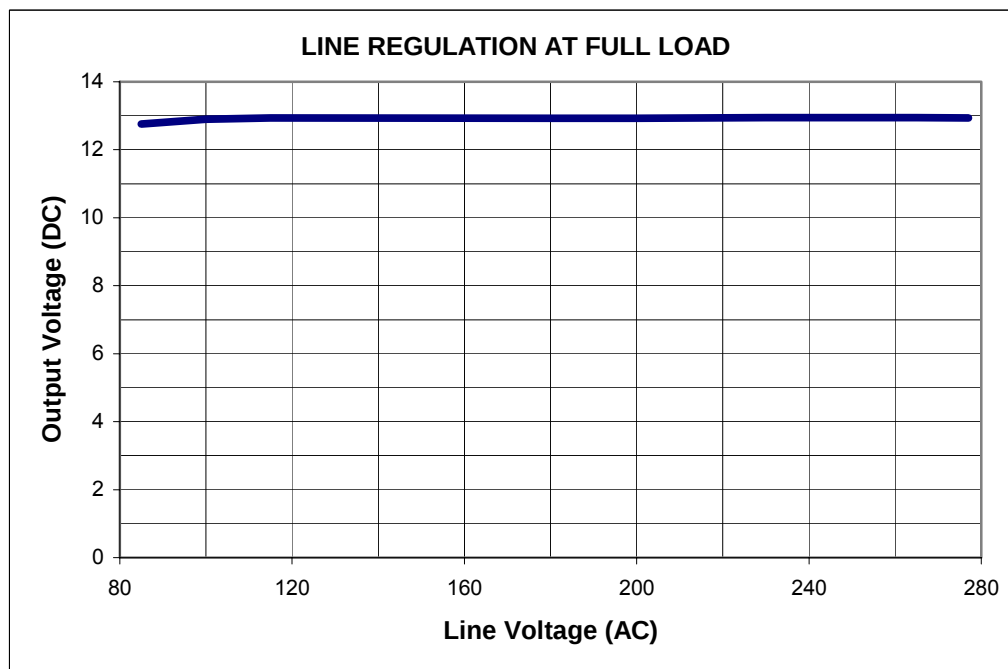


Figure 8 – Line Regulation, Room Temperature, Full Load.



9.4 Harmonic Content Chart

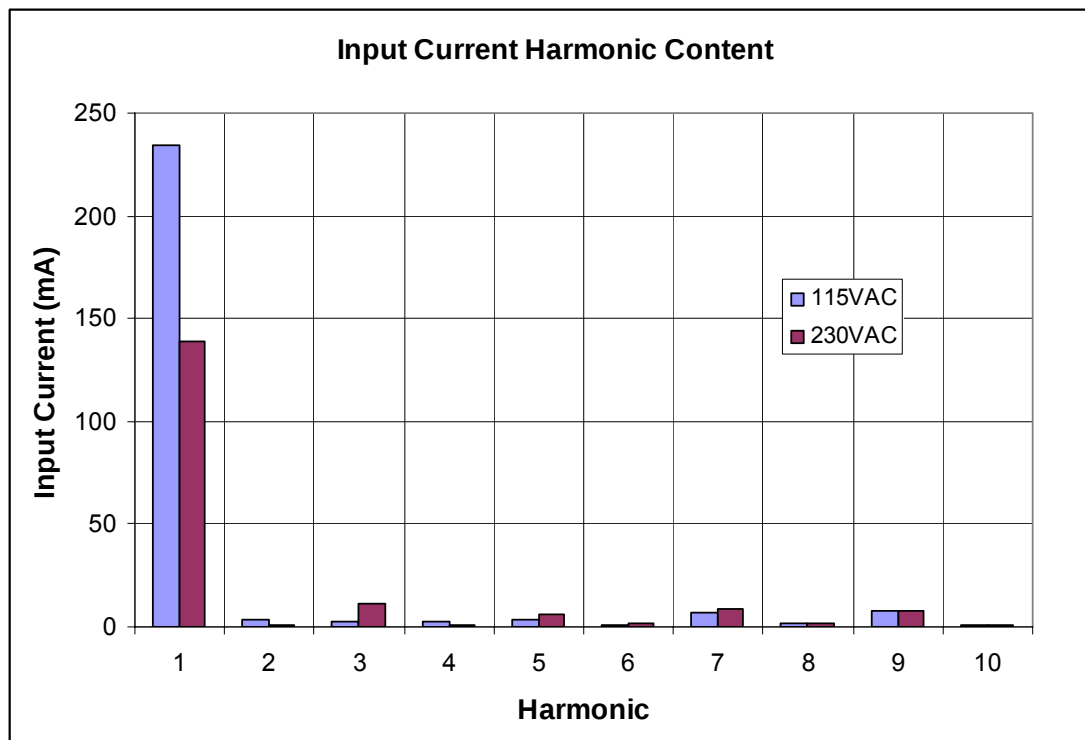


Figure 9 – Input Current Harmonic Content at Full Load.

9.5 Harmonic Content Measurements

Harmonic	115 AC $I_{IN}(mA)$	% of Funda- mental	IEC 61000-3-2 Limit (%)	230 AC $I_{IN}(mA)$	% of Funda- mental	IEC 61000-3-2 Limit (%)
1	234			139		
2	3.2	1.37	2	0.9	0.65	2
3	2.9	1.24	29.7	11	7.91	28.0
4	2.6	1.11		0.6	0.43	
5	3.6	1.54	10	6.1	4.39	10
6	0.8	0.34		1.5	1.08	
7	6.9	2.95	7	8.5	6.12	7
8	1.6	0.68		1.6	1.15	
9	7.6	3.25	5	7.8	5.61	5
10	1.3	0.56		0.9	0.65	

Figure 10 – Harmonic Contents in Percentage of Fundamental and IEC 61000-3-2 Limits for C Class Equipment.

NOTE: Third Harmonic Specification Follows the Formula: $30 \times \text{PFC}$. (Power Factor at 115/230 VAC)



9.6 Power Factor vs. Line Voltage at Full Load

Power factor is more critical for 115 VAC line voltages as PF is requirement whereas for 230 VAC harmonic content is the requirement.

Vin	PF
85	0.970
115	0.990
230	0.934
277	0.902

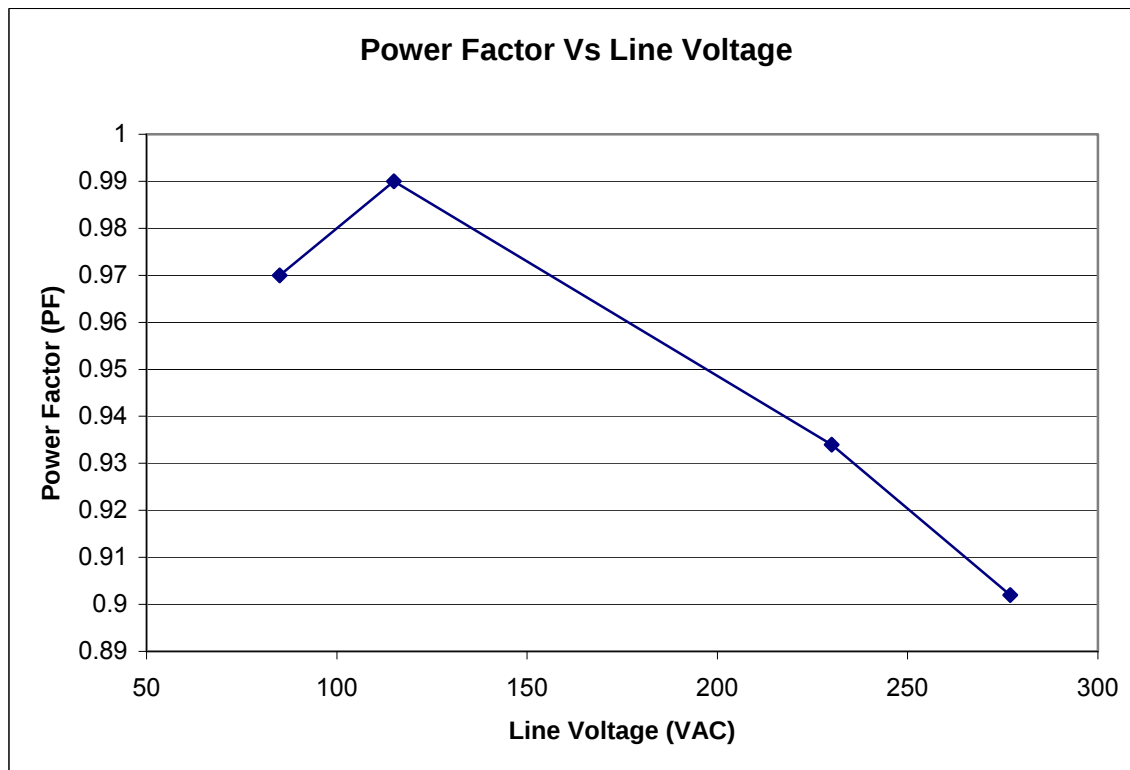


Figure 11 – Power Factor (PF) vs Input line voltage (VAC).



10 Thermal Performance

Thermal data was taken with unit inside a cardboard box to prevent air flow.

Item	Temperature (°C)	
	85 VAC	277 VAC
Ambient Outside the Box	25	25
TOPSwitch (U1)	42	53
Transformer (T1)	46	52
Output Rectifiers (D10, D11)	58	60

Result indicate adequate margin for >50 °C ambient operation.



11 Waveforms

11.1 Drain Voltage and Current, Normal Operation

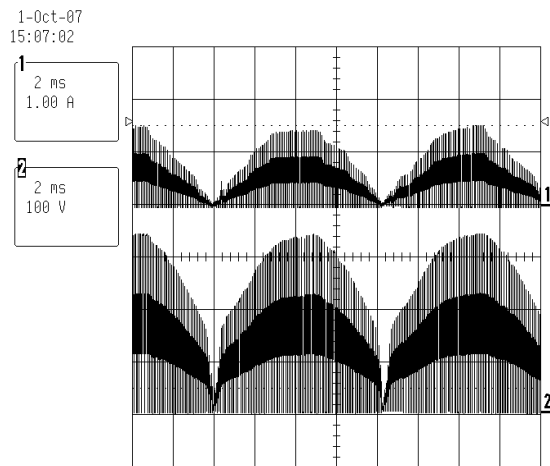


Figure 12 – 115 VAC, Full Load.
Upper: I_{DRAIN} , 1.0 A / div.
Lower: V_{DRAIN} , 100 V, 2 ms / div.

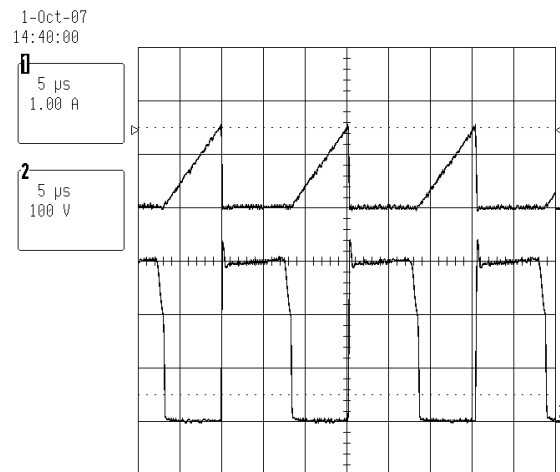


Figure 13 – 115 VAC, Full Load.
Upper: I_{DRAIN} , 1.0 A / div.
Lower: V_{DRAIN} , 100 V, 5 μs / div.

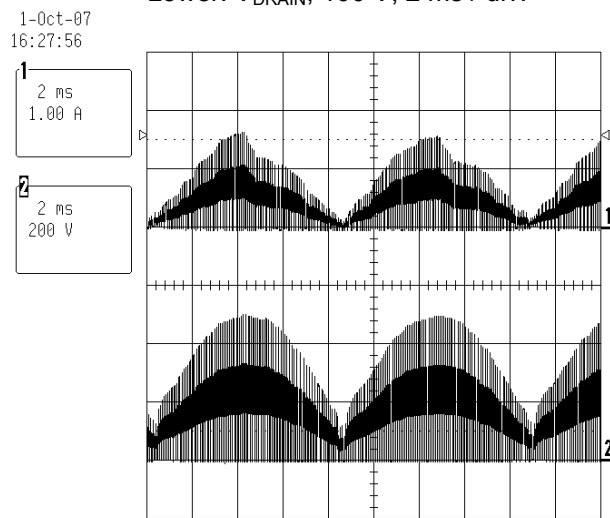


Figure 14 – 230 VAC, Full Load.
Upper: I_{DRAIN} , 1.0 A / div.
Lower: V_{DRAIN} , 200 V, 2 ms / div.

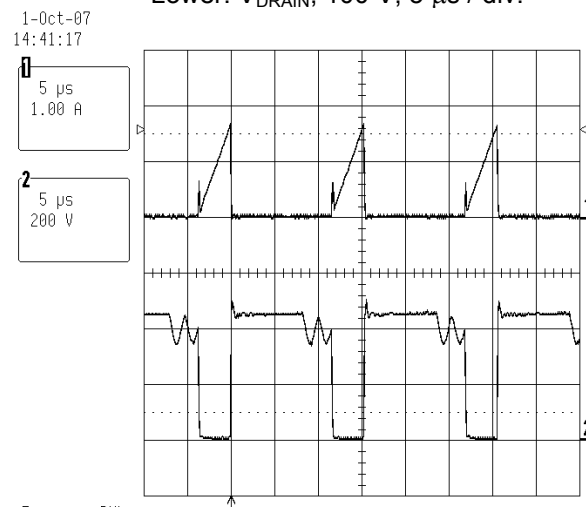


Figure 15 – 230 VAC, Full Load
Upper: I_{DRAIN} , 1.0 A / div.
Lower: V_{DRAIN} , 200 V, 5 μs / div.



11.2 Output Voltage Start-up Profile

2-Oct-07
9:37:07

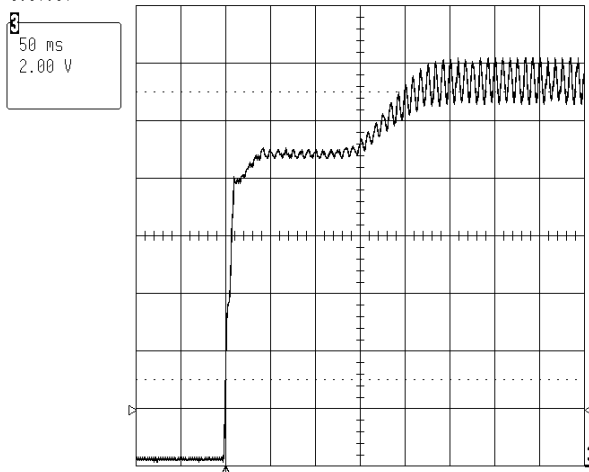


Figure 16 – Start-up Profile, 115 VAC
2 V, 50 ms / div.

2-Oct-07
9:37:56

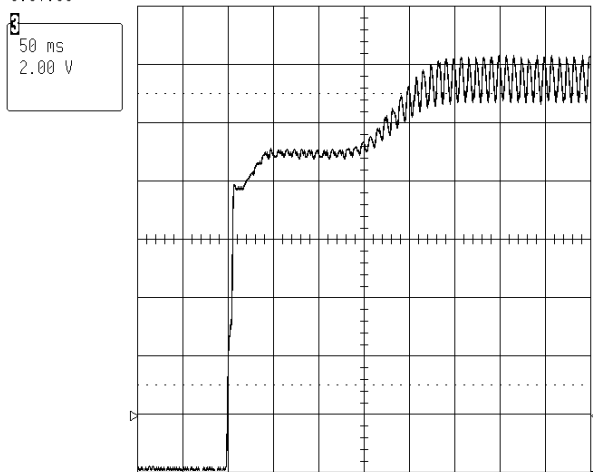


Figure 17 – Start-up Profile, 230 VAC
2 V, 50 ms / div.

11.3 Drain Voltage and Current Start-up Profile

2-Oct-07
8:54:03

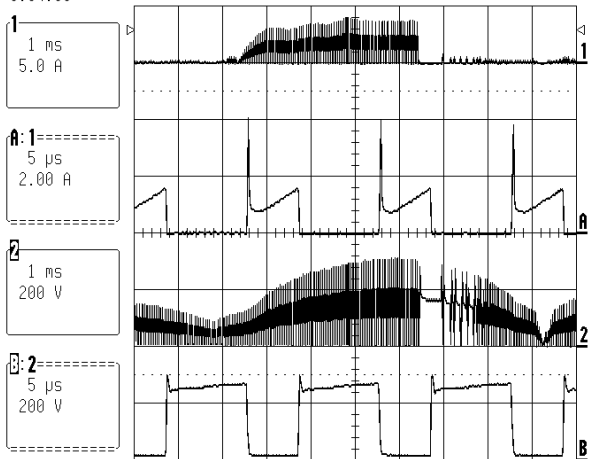


Figure 18 – 115 VAC Input and Maximum Load.
Upper: I_{DRAIN}
Lower: V_{DRAIN}

2-Oct-07
8:57:13

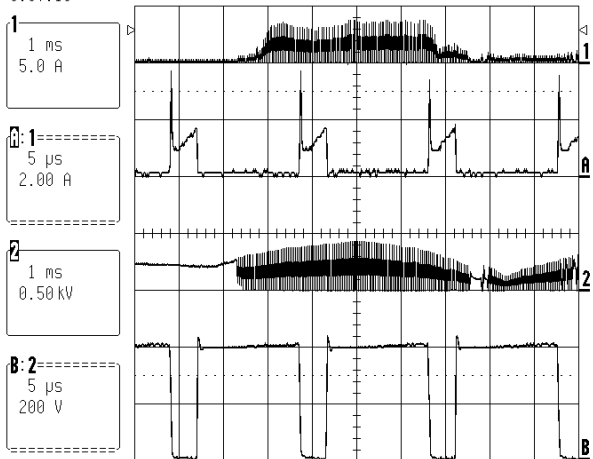


Figure 19 – 230 VAC Input and Maximum Load.
Upper: I_{DRAIN}
Lower: V_{DRAIN}

11.4 Output Ripple Measurements

11.4.1 Ripple Measurement Technique

For DC output ripple measurements, a modified oscilloscope test probe must be utilized in order to reduce spurious signals due to pickup. Details of the probe modification are provided in the figures below.

The 4987BA probe adapter is affixed with two capacitors tied in parallel across the probe tip. The capacitors include one (1) 0.1 μF /50 V ceramic type and one (1) 1.0 μF /50 V aluminum electrolytic. The aluminum electrolytic type capacitor is polarized, so proper polarity across DC outputs must be maintained (see below).

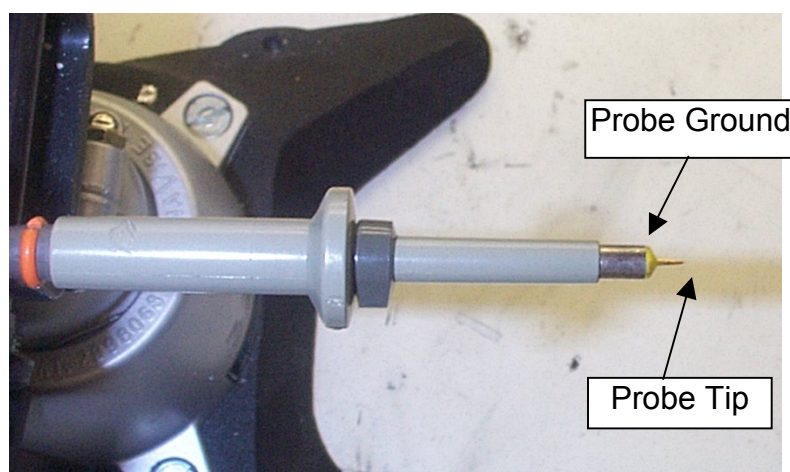


Figure 20 – Oscilloscope Probe Prepared for Ripple Measurement (End Cap and Ground Lead Removed).



Figure 21 – Oscilloscope Probe with Probe Master (www.probemaster.com) 4987A BNC Adapter (Modified with wires for ripple measurement, and two parallel decoupling capacitors added).

11.4.2 Measurement Results

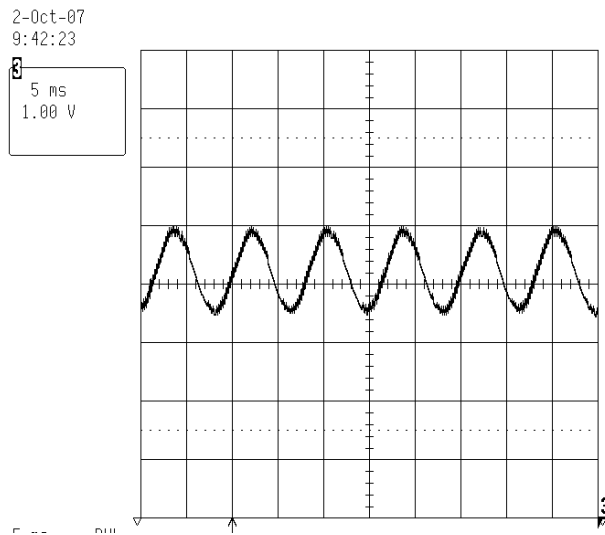


Figure 22 – Ripple, 115 VAC, Full Load.
5 ms, 1 V / div.

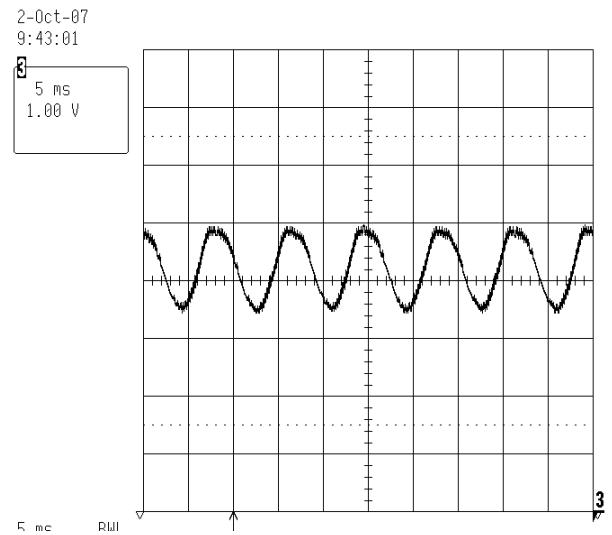


Figure 23 – Ripple, 230 VAC, Full Load.
5 ms, 1 V /div.

12 Conducted EMI

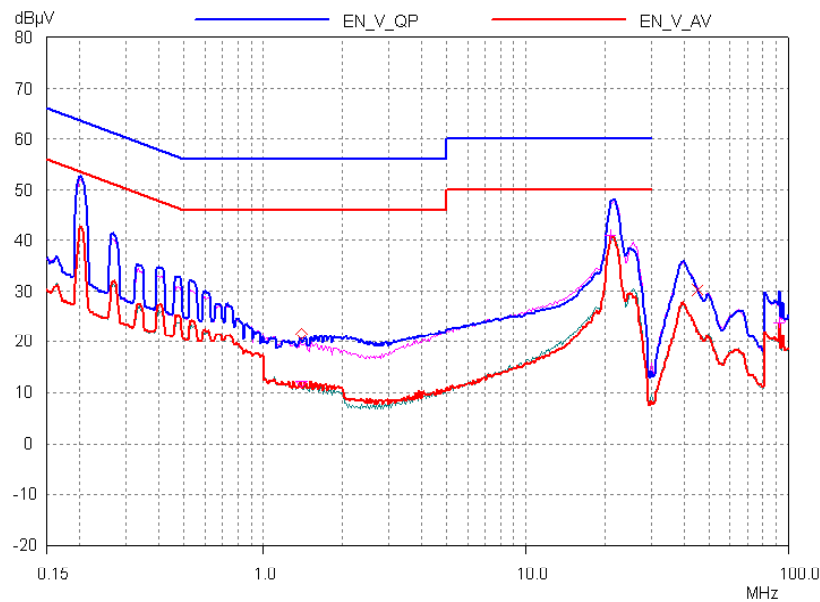


Figure 24 – Conducted EMI, 115 VAC Full Load, LIGHT Traces: NTL, BOLD Traces: L1. OUTRET Grounded.

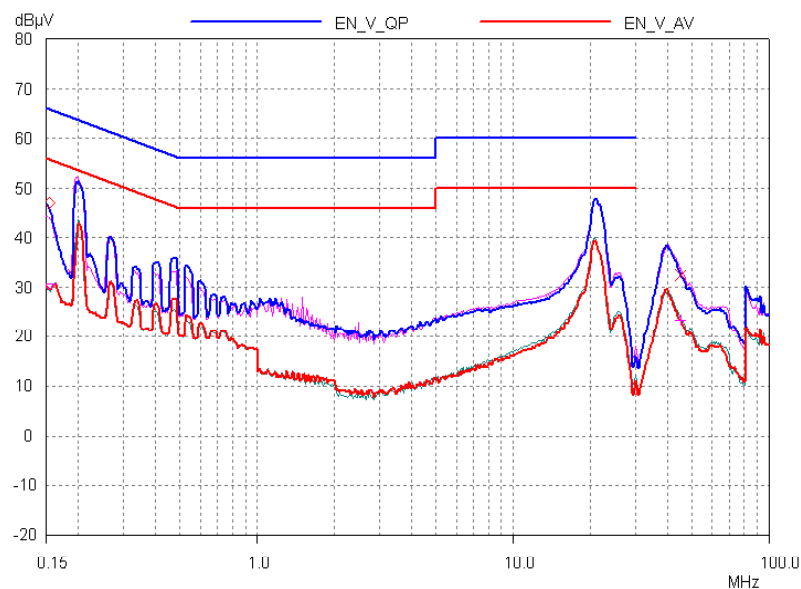


Figure 25 – Conducted EMI, 230 VAC. Full Load, LIGHT Traces: NTL, BOLD Traces L1. OUTRET Grounded.



13 Revision History

Date	Author	Revision	Description & changes
1-Nov-07	PV	1.1	Final Release



Notes



Power Integrations

Tel: +1 408 414 9200 Fax: +1 408 414 9201
www.powerint.com

Notes



For the latest updates, visit our website: www.powerint.com

Power Integrations reserves the right to make changes to its products at any time to improve reliability or manufacturability. Power Integrations does not assume any liability arising from the use of any device or circuit described herein. POWER INTEGRATIONS MAKES NO WARRANTY HEREIN AND SPECIFICALLY DISCLAIMS ALL WARRANTIES INCLUDING, WITHOUT LIMITATION, THE IMPLIED WARRANTIES OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, AND NON-INFRINGEMENT OF THIRD PARTY RIGHTS.

PATENT INFORMATION

The products and applications illustrated herein (including transformer construction and circuits external to the products) may be covered by one or more U.S. and foreign patents, or potentially by pending U.S. and foreign patent applications assigned to Power Integrations. A complete list of Power Integrations' patents may be found at www.powerint.com. Power Integrations grants its customers a license under certain patent rights as set forth at <http://www.powerint.com/ip.htm>.

The PI Logo, **TOPSwitch**, **TinySwitch**, **LinkSwitch**, **DPA-Switch**, **PeakSwitch**, **EcoSmart**, **Clampless**, **E-Shield**, **Filterfuse**, **StackFET**, **PI Expert** and **PI FACTS** are trademarks of Power Integrations, Inc. Other trademarks are property of their respective companies. ©Copyright 2007 Power Integrations, Inc.

Power Integrations Worldwide Sales Support Locations

WORLD HEADQUARTERS

5245 Hellyer Avenue
San Jose, CA 95138, USA.
Main: +1-408-414-9200
Customer Service:
Phone: +1-408-414-9665
Fax: +1-408-414-9765
e-mail: usasales@powerint.com

GERMANY

Rueckertstrasse 3
D-80336, Munich
Germany
Phone: +49-89-5527-3911
Fax: +49-89-5527-3920
e-mail: eurosales@powerint.com

JAPAN

Kosei Dai-3 Bldg.,
2-12-11, Shin-Yokohama,
Kohoku-ku, Yokohama-shi,
Kanagawa 222-0033
Phone: +81-45-471-1021
Fax: +81-45-471-3717
e-mail:
japansales@powerint.com

TAIWAN

5F, No. 318, Nei Hu Rd., Sec. 1
Nei Hu Dist.
Taipei, Taiwan 114, R.O.C.
Phone: +886-2-2659-4570
Fax: +886-2-2659-4550
e-mail:
taiwansales@powerint.com

CHINA (SHANGHAI)

Rm 807-808A,
Pacheer Commercial Centre,
555 Nanjing Rd. West
Shanghai, P.R.C. 200041
Phone: +86-21-6215-5548
Fax: +86-21-6215-2468
e-mail: chinasales@powerint.com

INDIA

#1, 14th Main Road
Vasanthanagar
Bangalore-560052 India
Phone: +91-80-41138020
Fax: +91-80-41138023
e-mail: indiasales@powerint.com

KOREA

RM 602, 6FL
Korea City Air Terminal B/D,
159-6
Samsung-Dong, Kangnam-Gu,
Seoul, 135-728, Korea
Phone: +82-2-2016-6610
Fax: +82-2-2016-6630
e-mail:
koreasales@powerint.com

UNITED KINGDOM

1st Floor, St. James's House
East Street, Farnham
Surrey, GU9 7TJ
United Kingdom
Phone: +44 (0) 1252-730-141
Fax: +44 (0) 1252-727-689
e-mail: eurosales@powerint.com

CHINA (SHENZHEN)

Room A, B & C 4th Floor, Block C
Elec. Sci. Tech. Bldg.
2070 Shennan Zhong Rd.
Shenzhen, Guangdong,
China, 518031
Phone: +86-755-8379-3243
Fax: +86-755-8379-5828
e-mail: chinasales@powerint.com

ITALY

Via De Amicis 2
20091 Bresso MI – Italy
Phone: +39-028-928-6000
Fax: +39-028-928-6009
e-mail: eurosales@powerint.com

SINGAPORE

51 Newton Road,
#15-08/10 Goldhill Plaza,
Singapore, 308900
Phone: +65-6358-2160
Fax: +65-6358-2015
e-mail:
singaporesales@powerint.com

APPLICATIONS HOTLINE

World Wide +1-408-414-9660

APPLICATIONS FAX

World Wide +1-408-414-9760



Power Integrations

Tel: +1 408 414 9200 Fax: +1 408 414 9201
www.powerint.com