
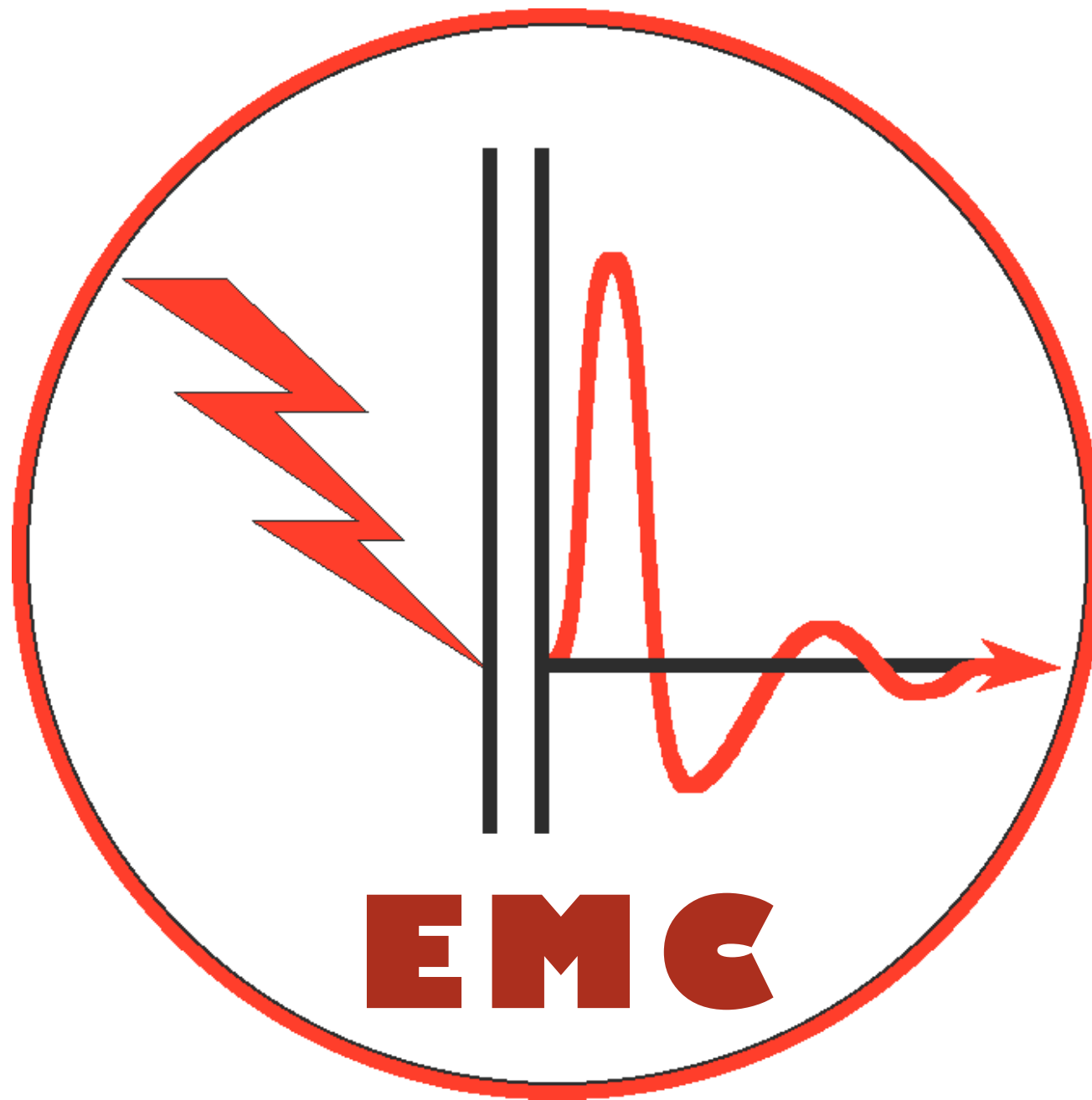


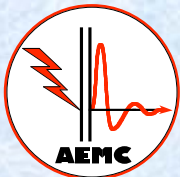

WARRINGTON - Monday 17 May - Alain CHAROY

- **Introduction**
- **Differential Mode Immunity**
- **Differential Mode Emissions**
- **Common Mode Emissions**
- **Electromagnetic Radiations**



EMC terms and lab assessment conditions

Electromagnetic emission

Electromagnetic susceptibility

Standardized test

Standardized test

Given EM disturbance

Given EM disturbance

Defined Measuring equipment

Defined Disturbance source

Standardized Measuring conditions

Standardized Measuring conditions

Emission-test level

Immunity-test level

Emission-test limit


Immunity-test limit

**The best situation is
to undertake EMC tests
& to solve EMC problems
before they appear *in situ***


Single emitter
Deterministic situation

Single victim
Deterministic situation



EMC best controlling conditions

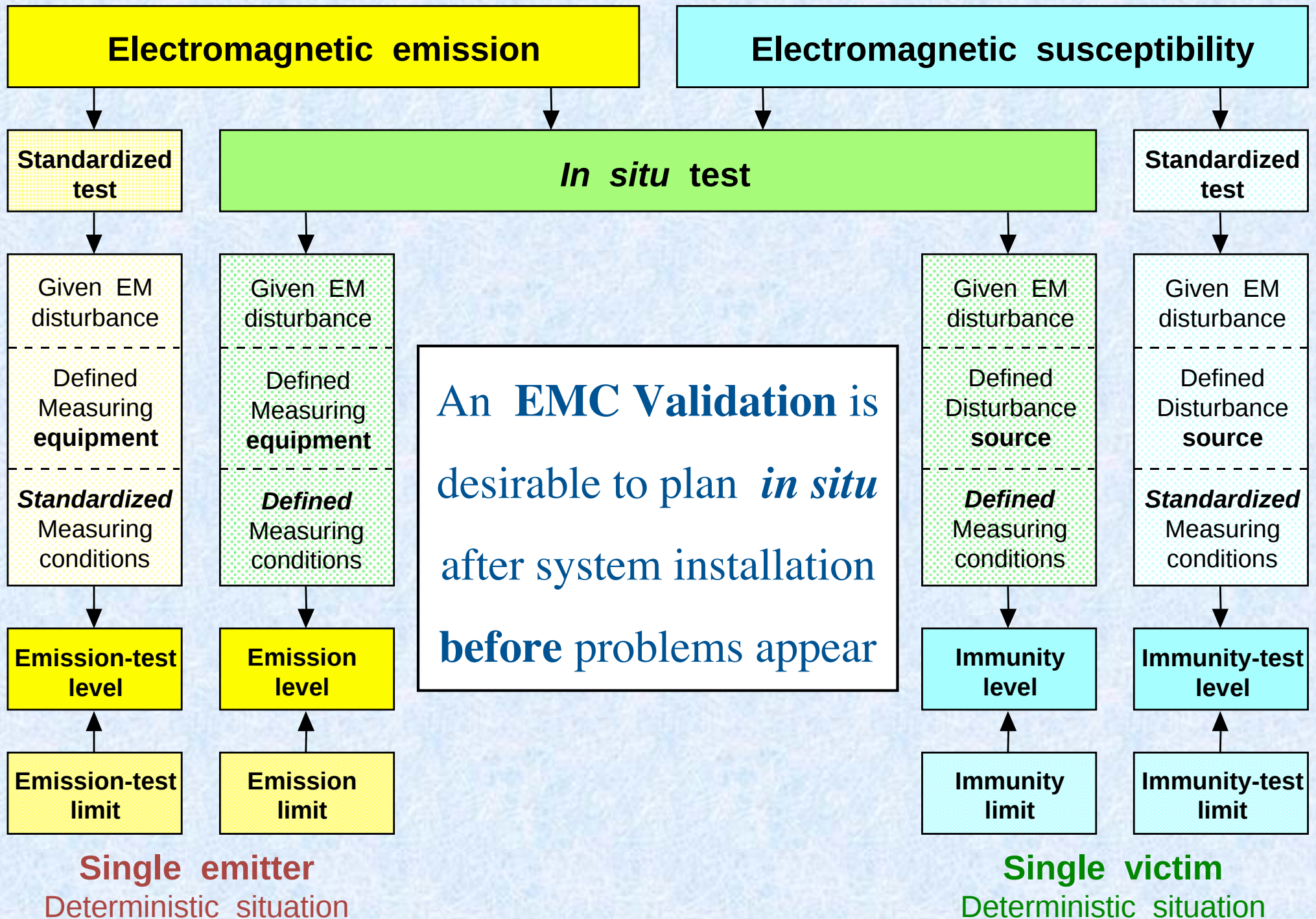


EMC troubleshooting

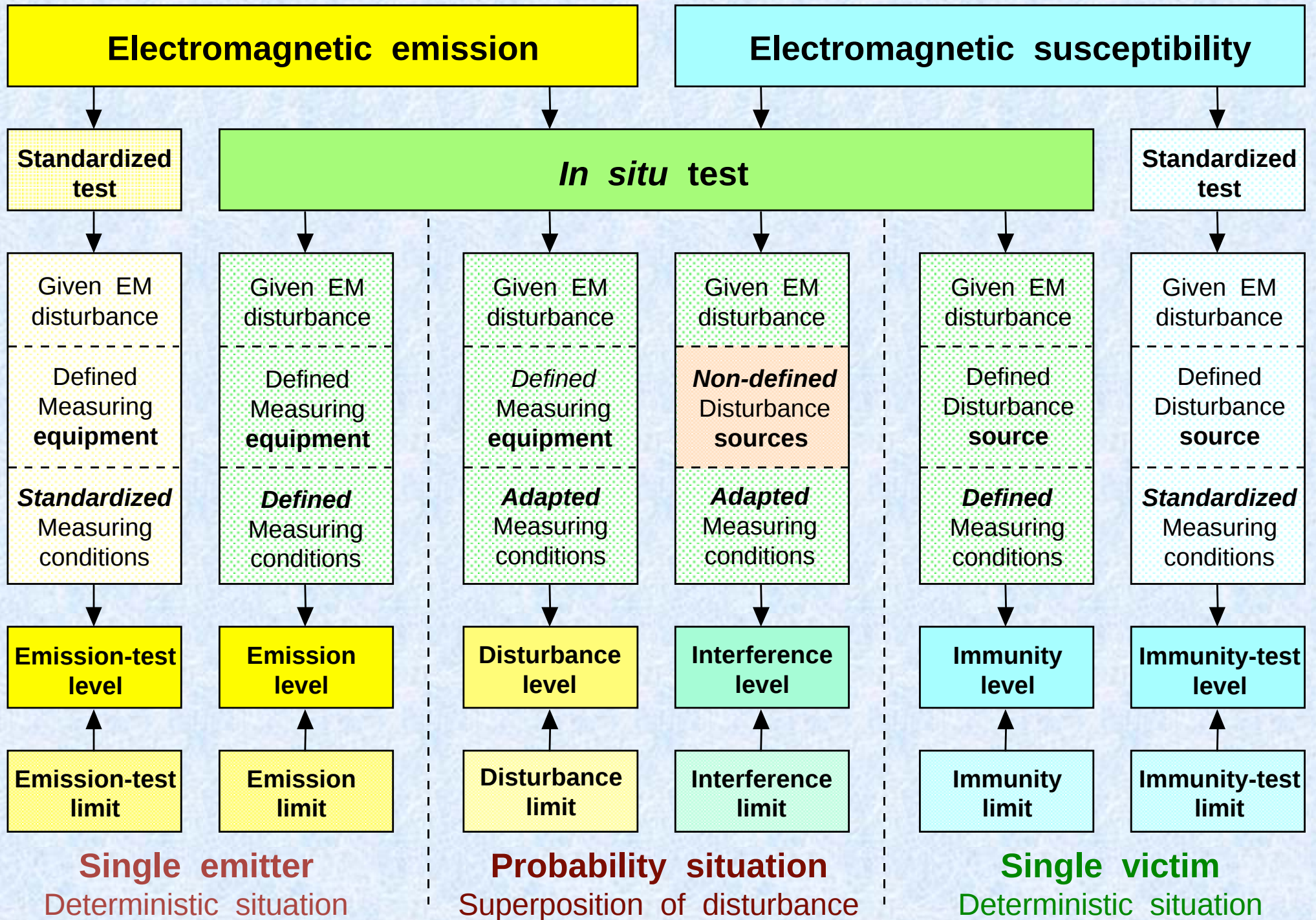

Common Mode & Differential Mode

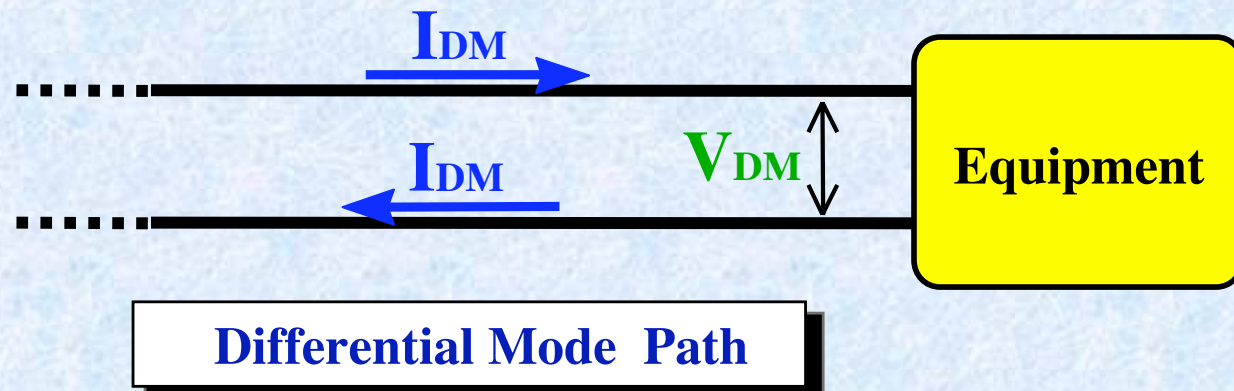
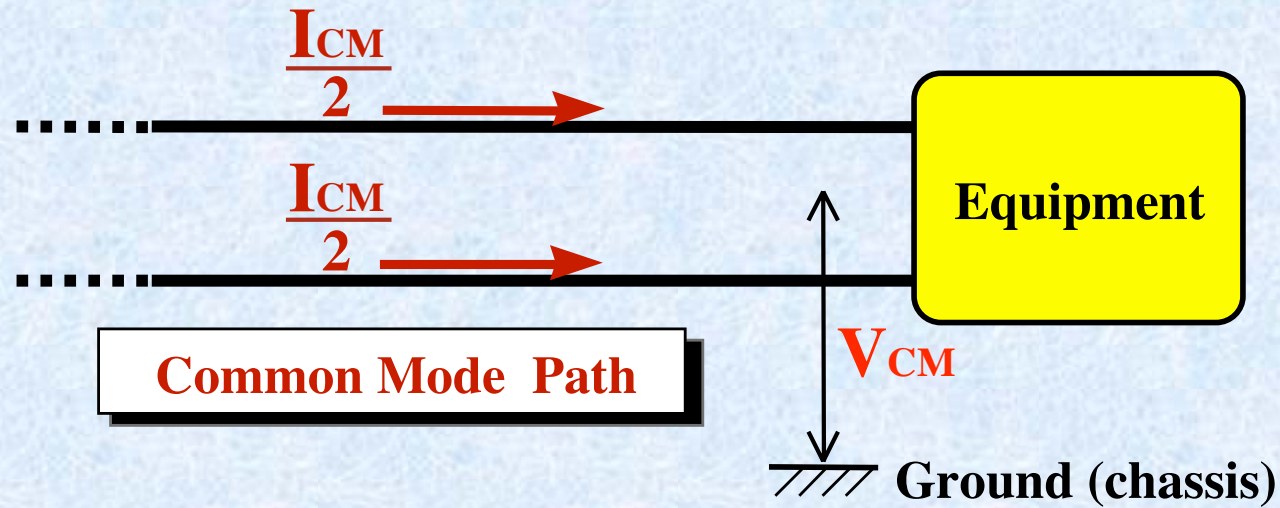


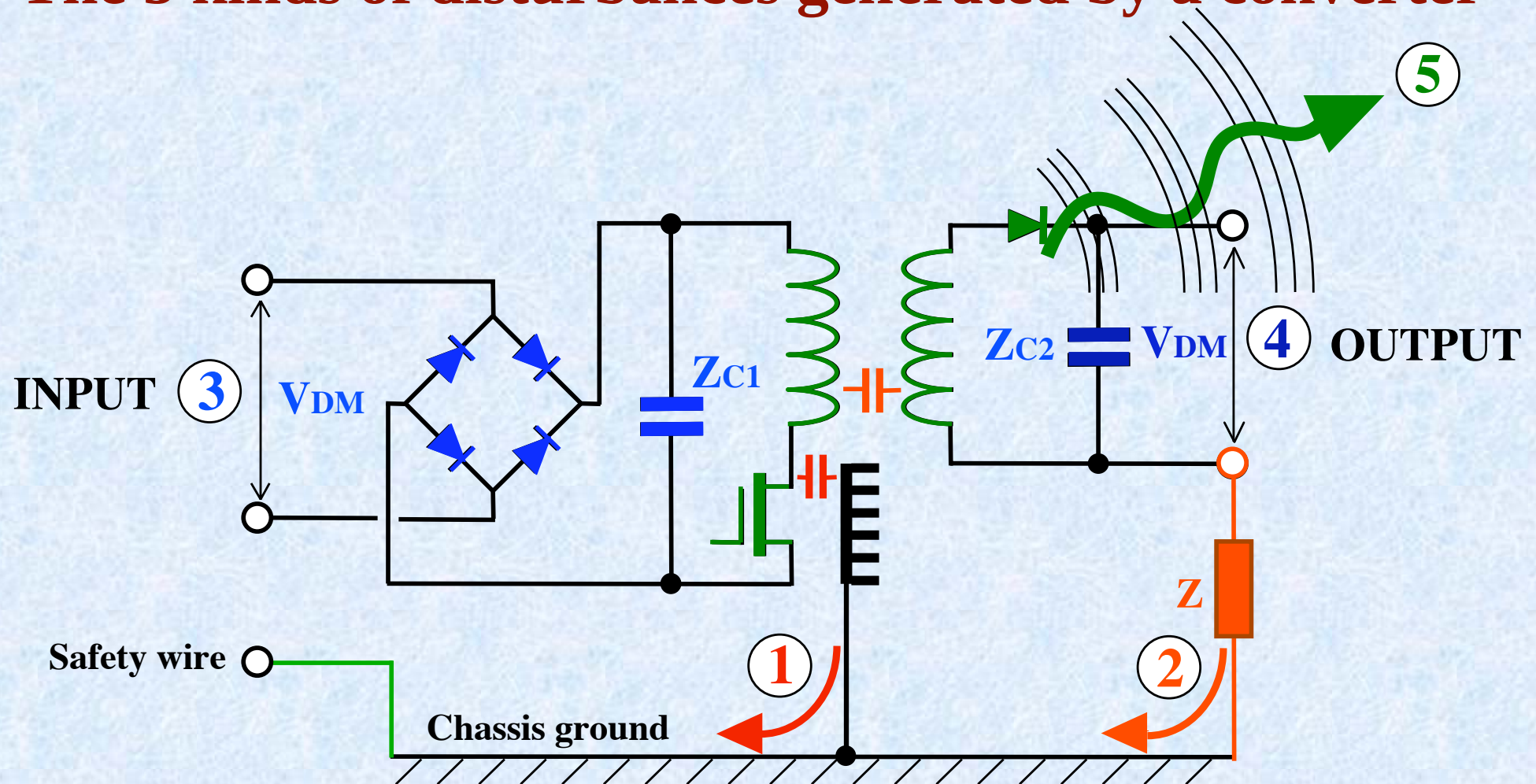The 5 kinds of disturbances generated by a converter





- ① **Input-to-Chassis Common Mode**
- ② **Input-to-Output Common Mode**
- ③ **Input Differential Mode**
- ④ **Output Differential Mode**
- ⑤ **Electromagnetic radiations (E & H)**




How to measure CM & DM currents ?

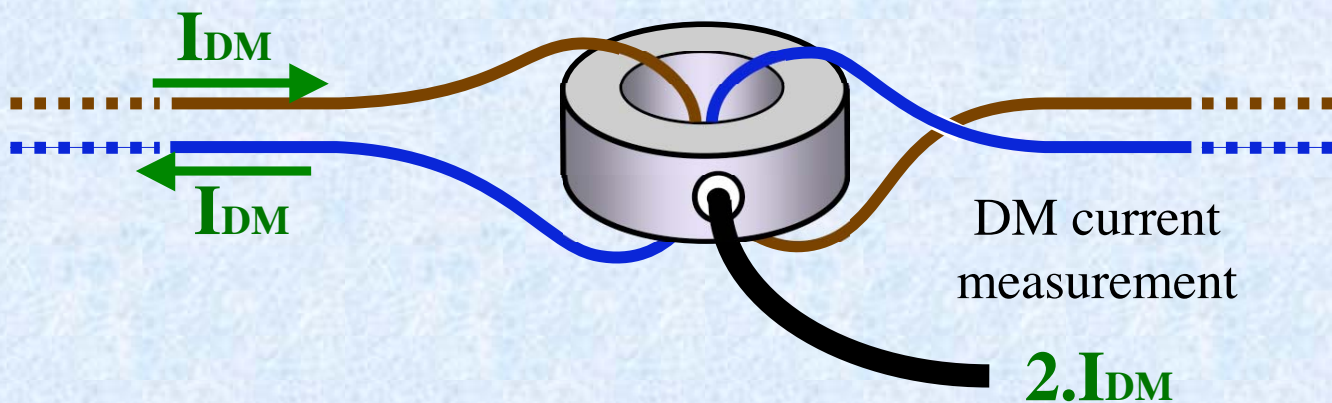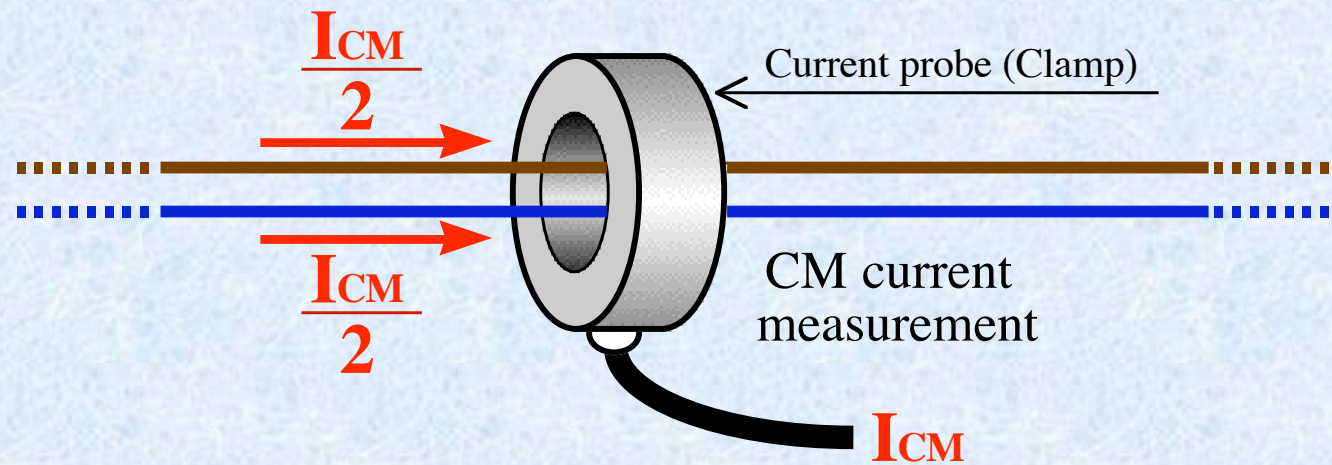

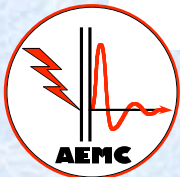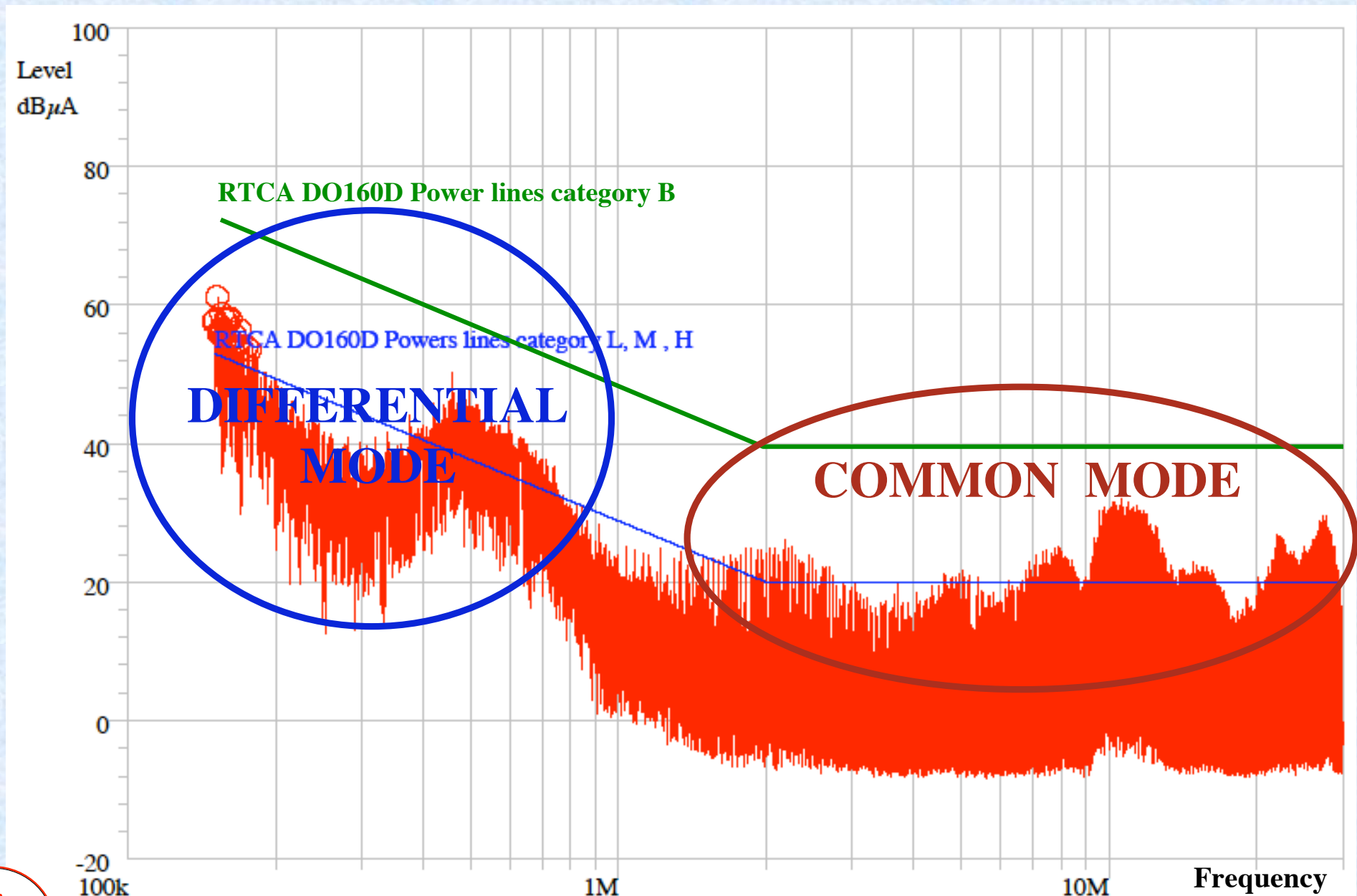
Typical input current of a 5 kVA filtered converter



How to measure a disturbing voltage ?

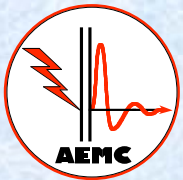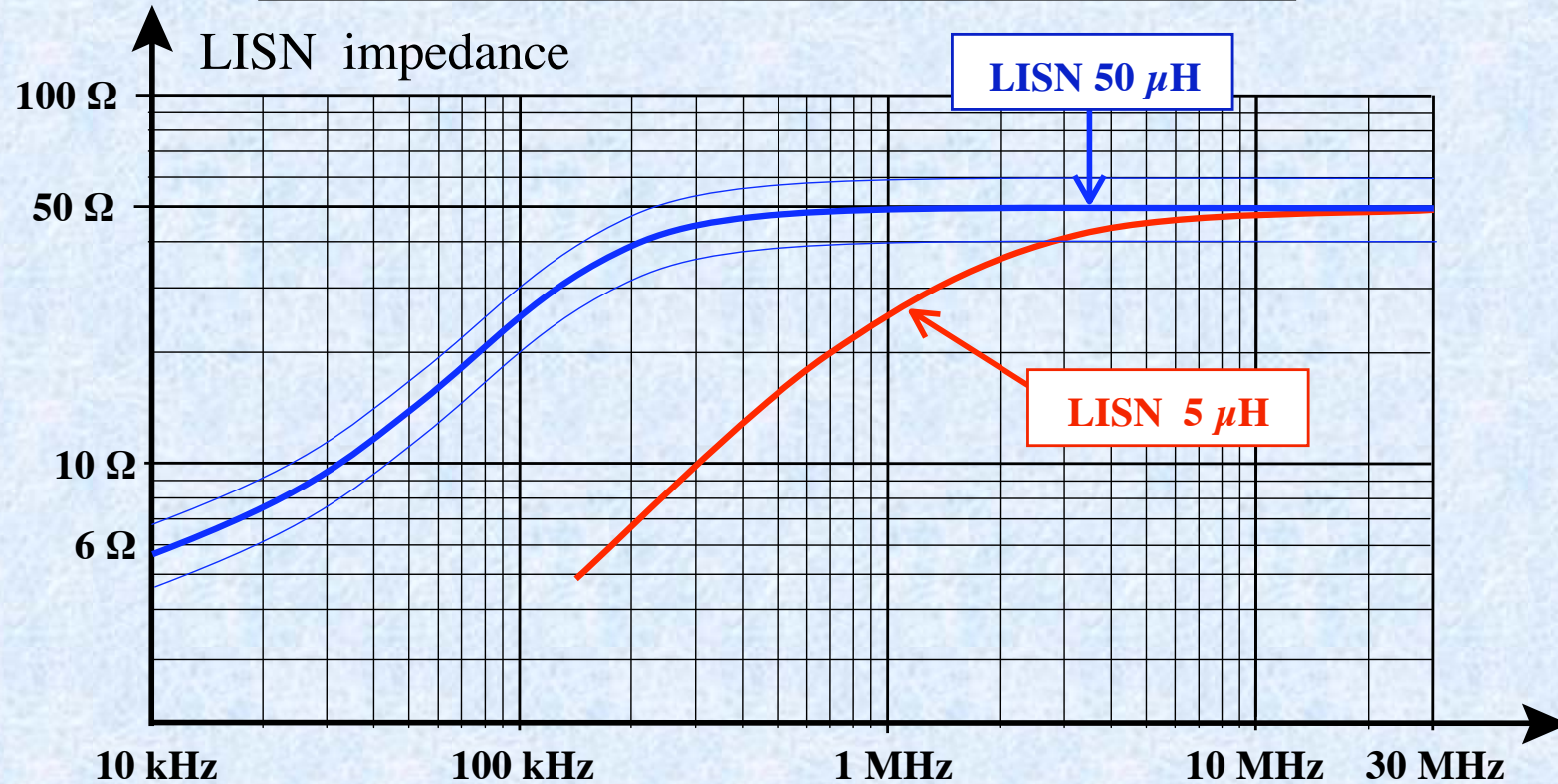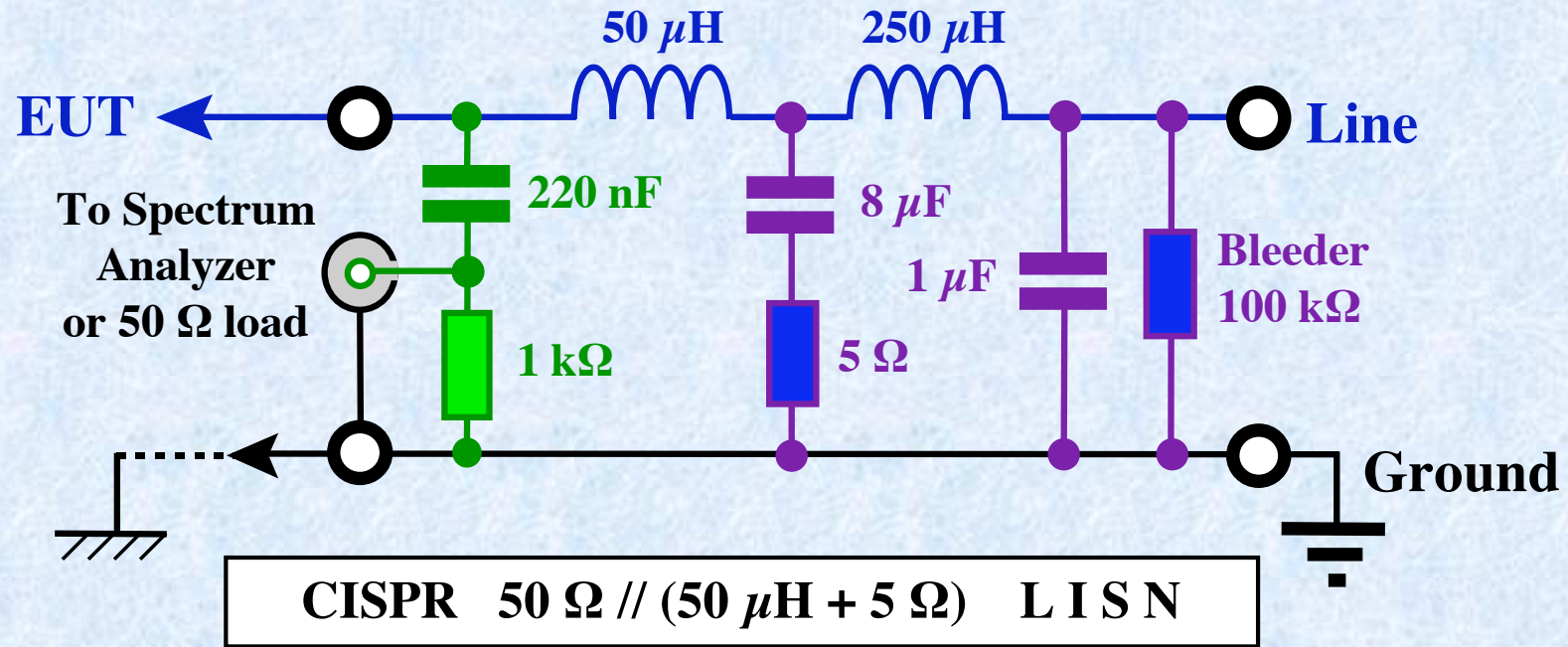

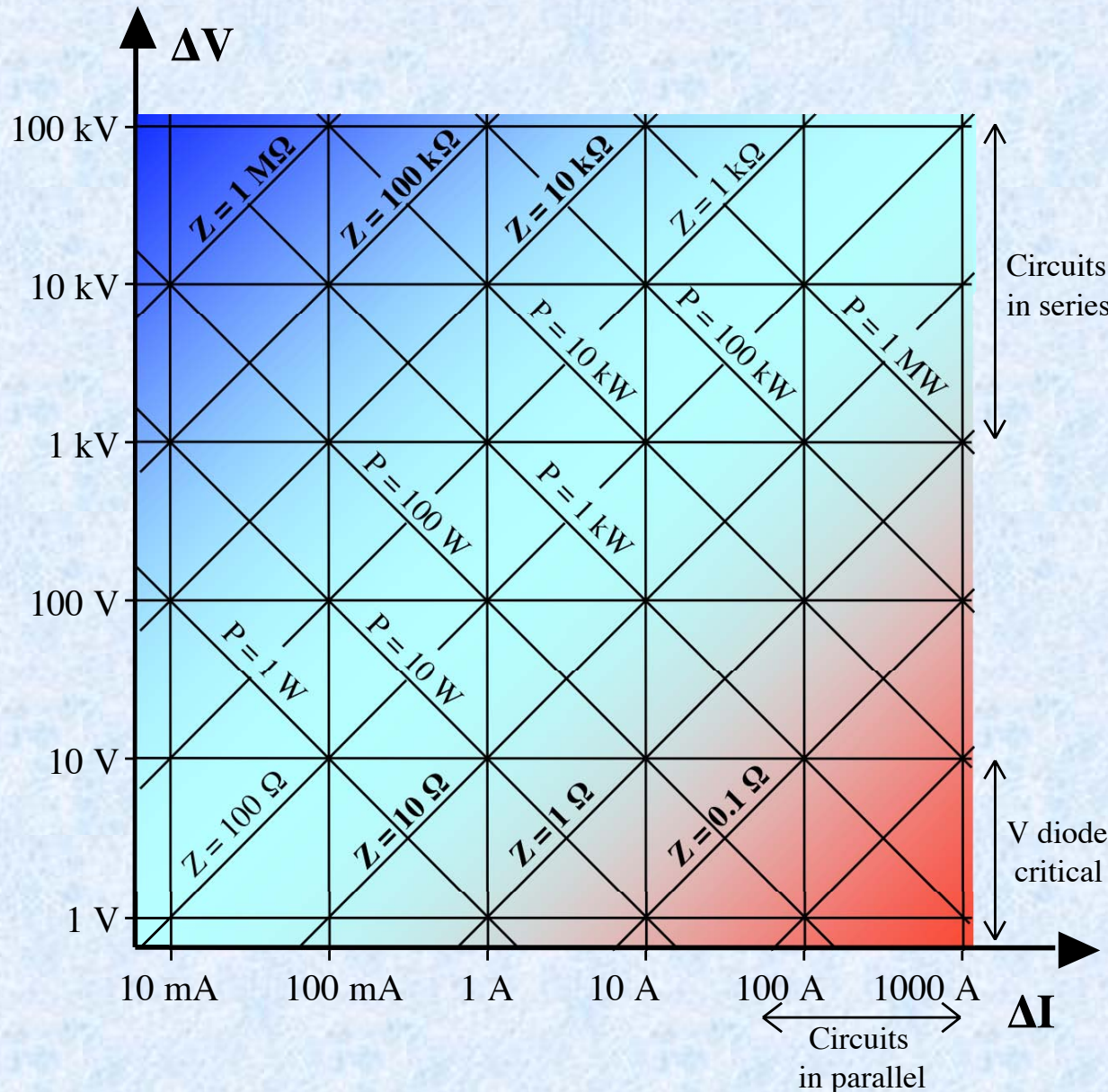
A concealed key point: the switching dynamic impedance



**High
impedance
zone**

E field dominates, so:

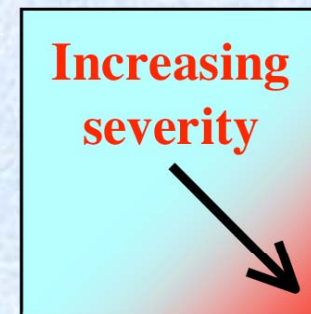
- Reduce parasitic capacitors
- Limit high $\Delta V/\Delta t$ trace lengths
- Choose low ϵ_r materials (air !)
- Use lower V circuits in series



**Low
impedance
zone**


H field dominates, so:

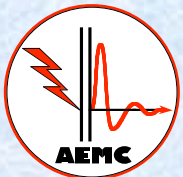- Reduce ESR and ESL
- Limit high $\Delta I/\Delta t$ loop areas
- Choose “sandwich” geometries
- Use lower I circuits in parallel





**Any switching circuit should
be positioned in this plane...**

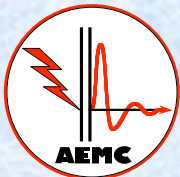- Introduction
- **Differential Mode Immunity**
- Differential Mode Emissions
- Common Mode Emissions
- Electromagnetic Radiations






The voltage tolerance boundary

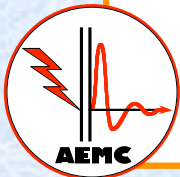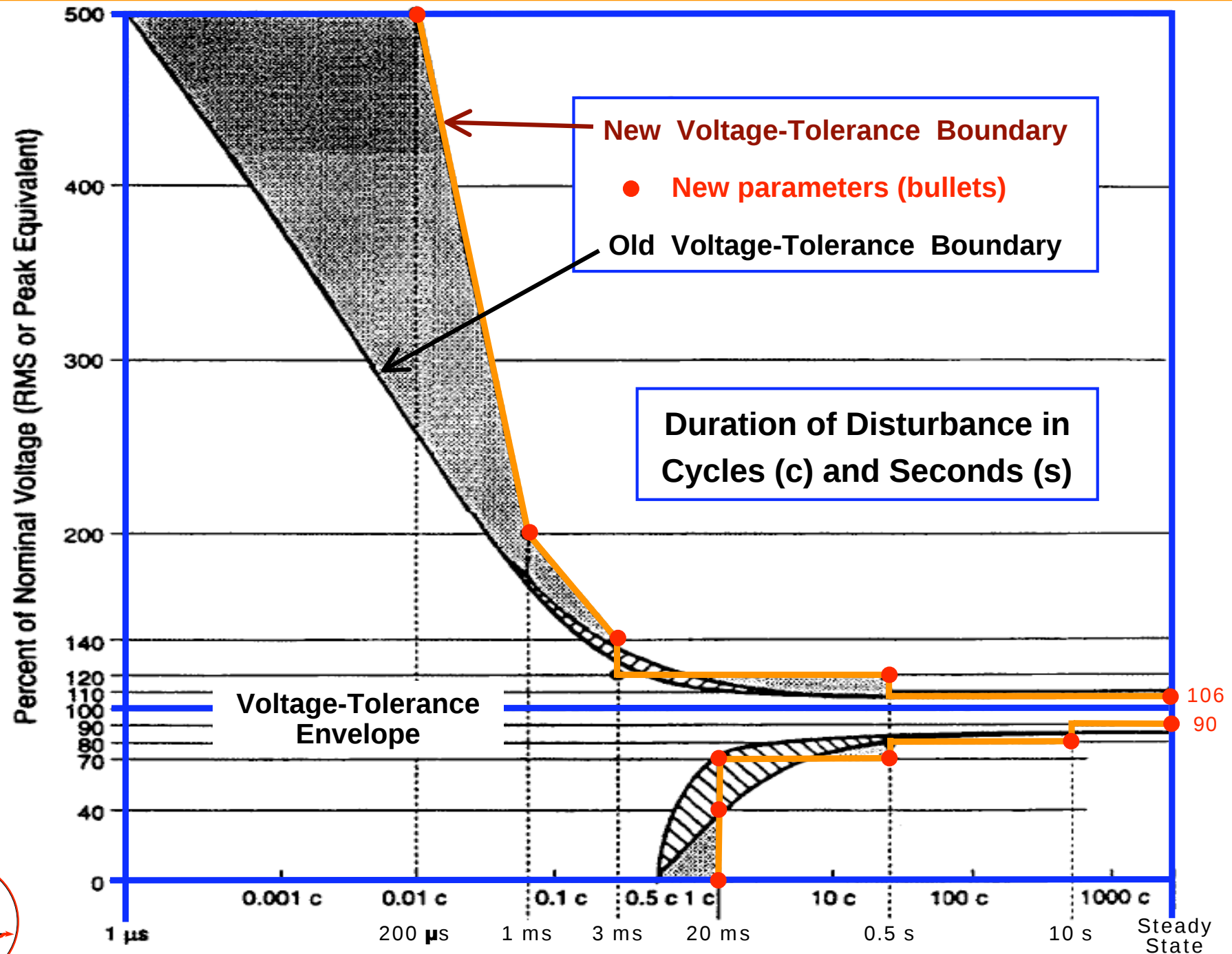


Transient Turn-on Overvoltage

Self-pulsation : $\omega_0 = \frac{1}{\sqrt{L.C}}$

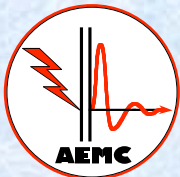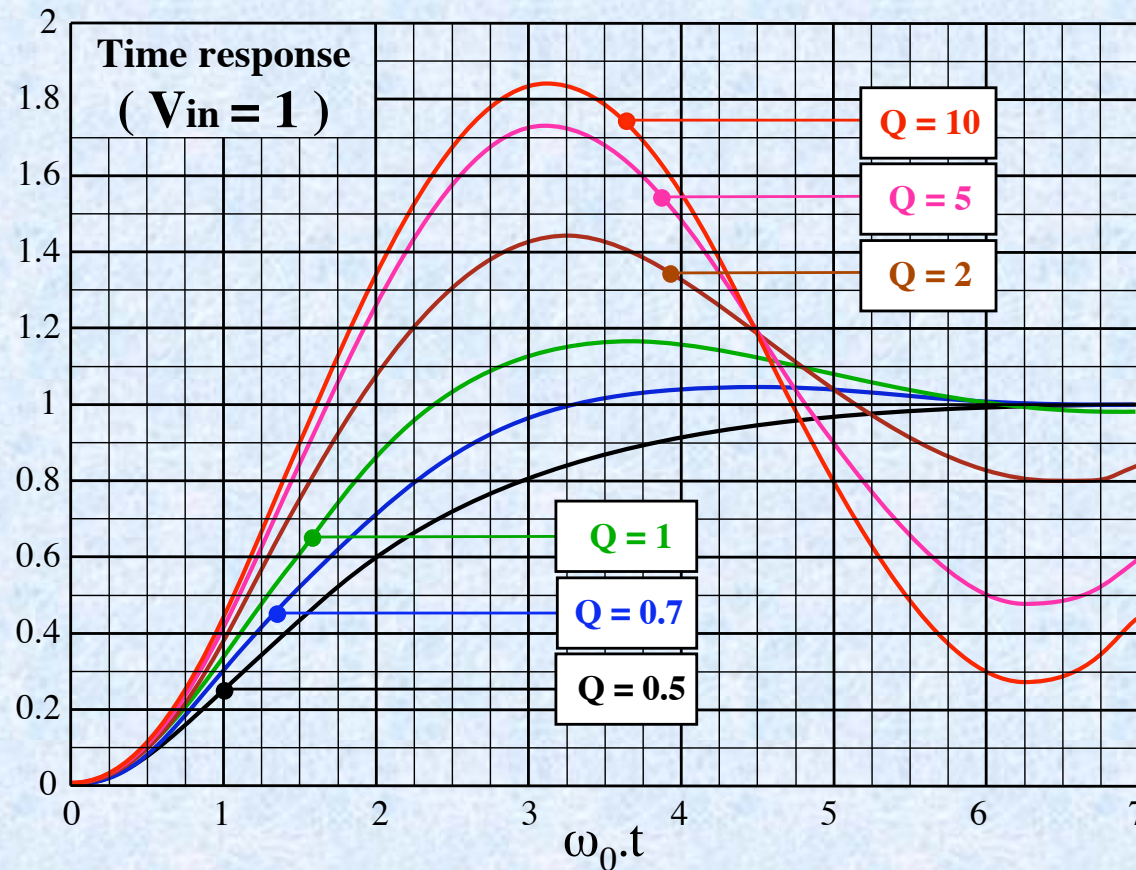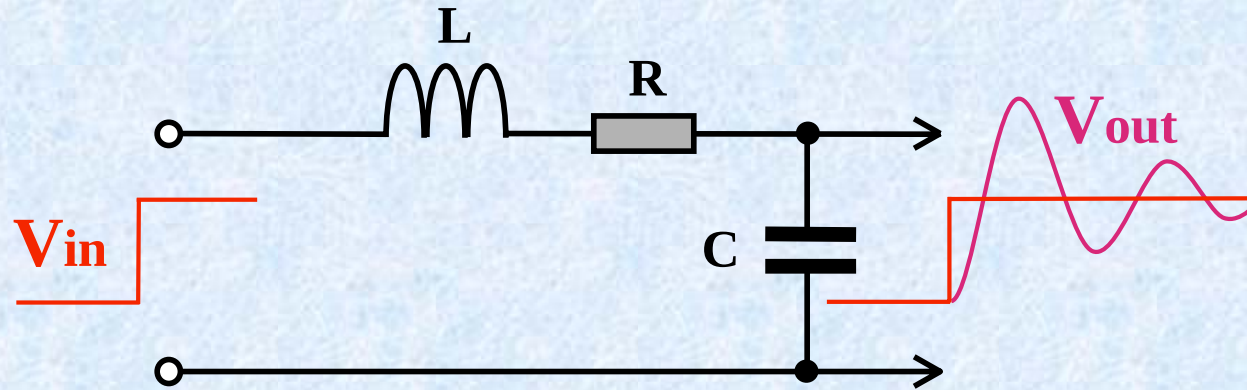
Quality Factor : $Q = \frac{L.\omega_0}{R}$



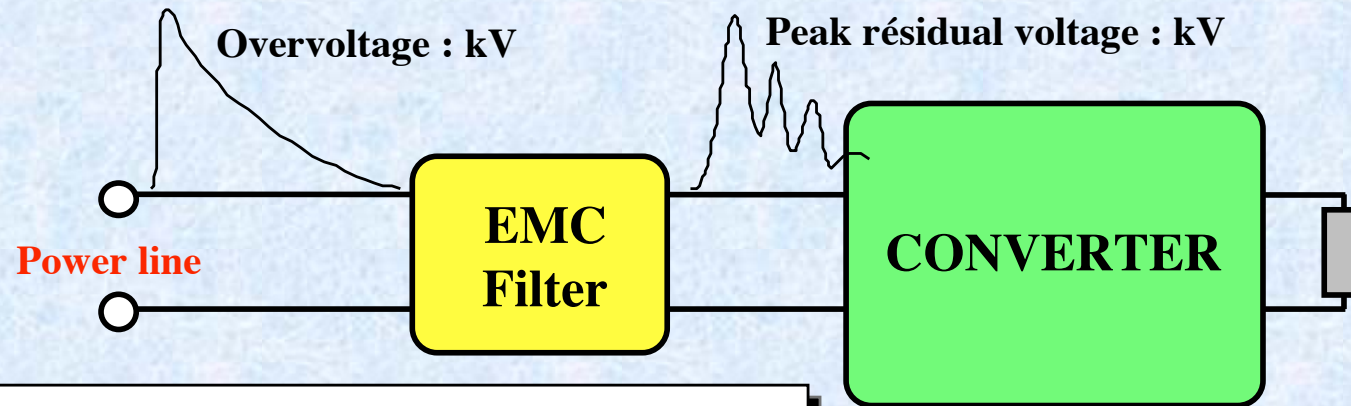
Where to install a DM Voltage Transient Suppressor ?



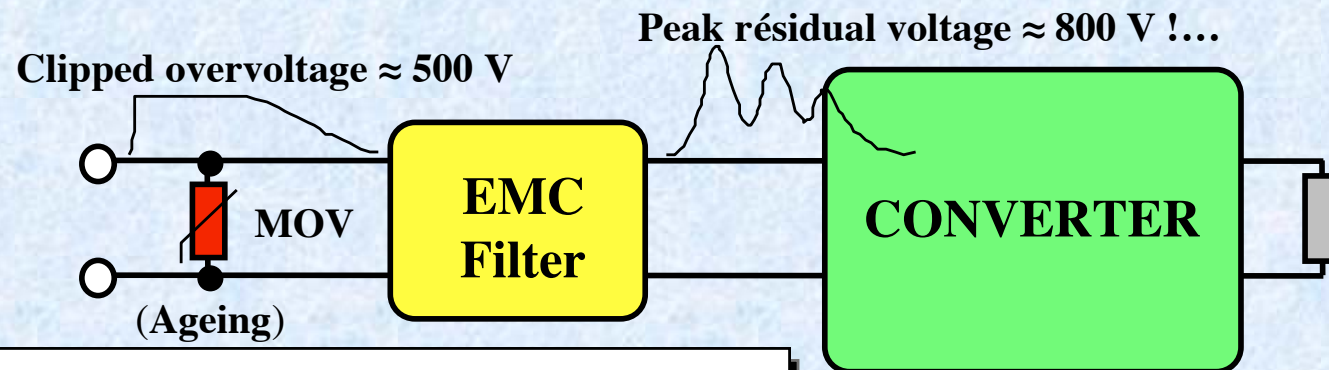Without TVS : serious risk of destruction




Varistor on line input : a risk remains

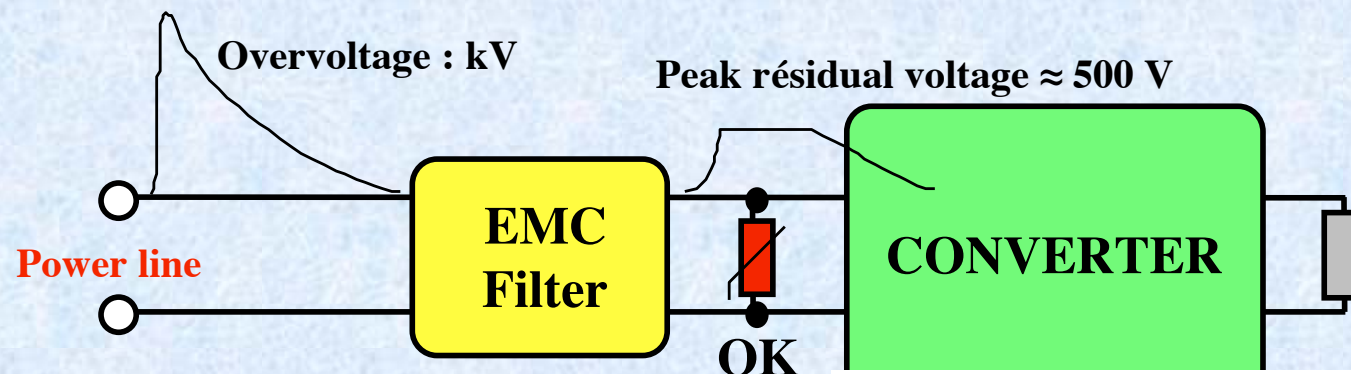


Varistor at converter input : best results

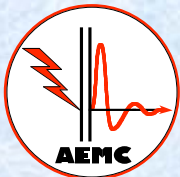& Filter inductance prevents TVS premature triggering





Where to add protection components ?

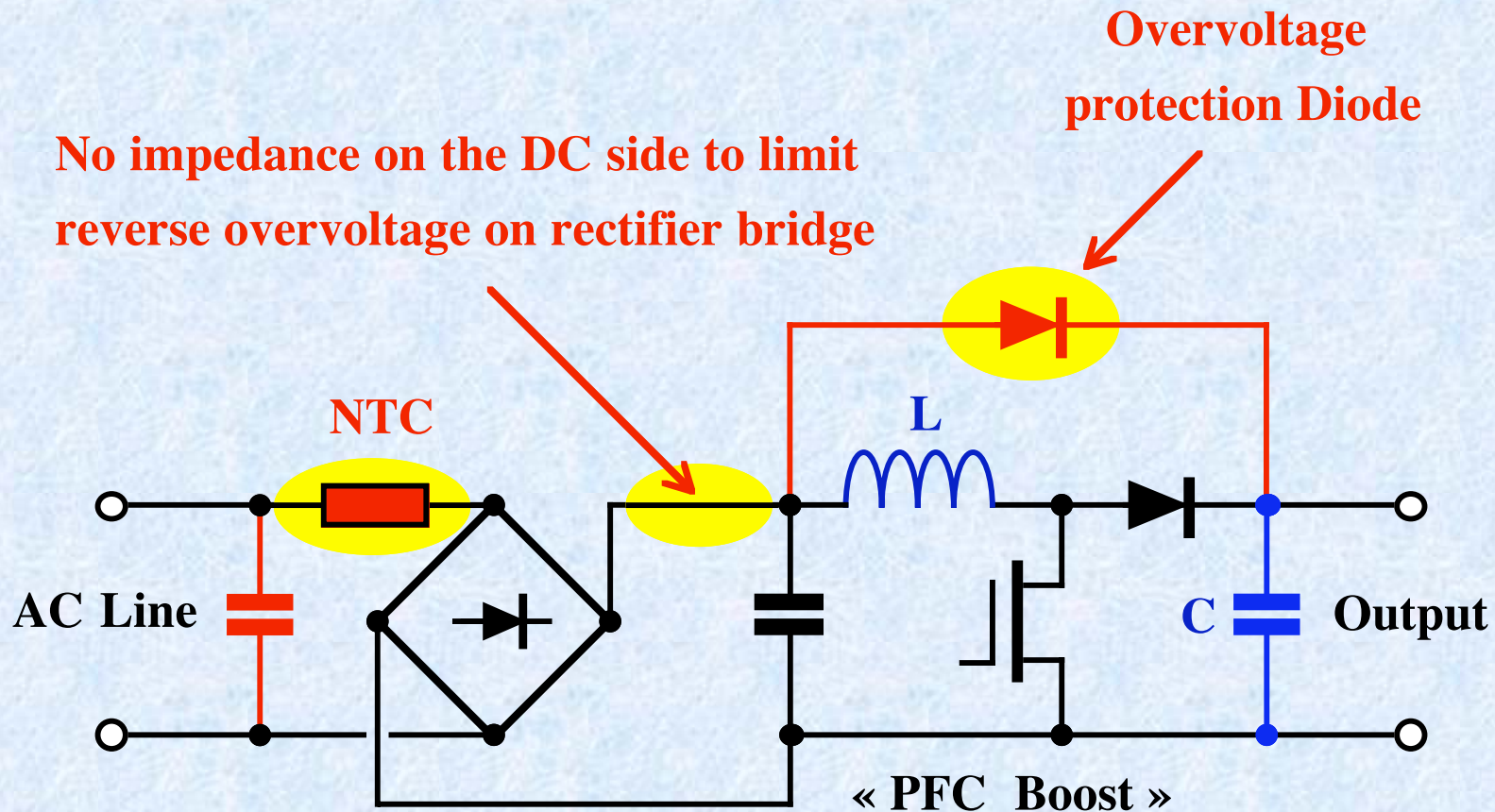

A **Diode** avoids output voltage doubling
A **NTC thermistor** limits inrush current

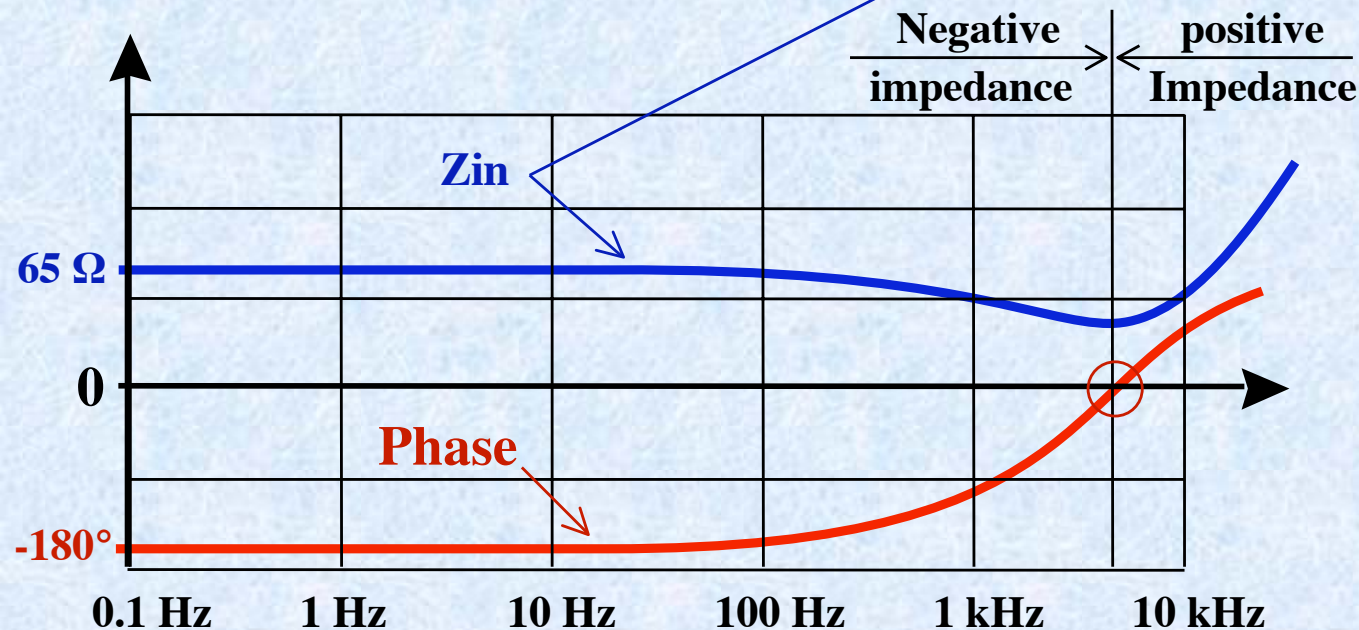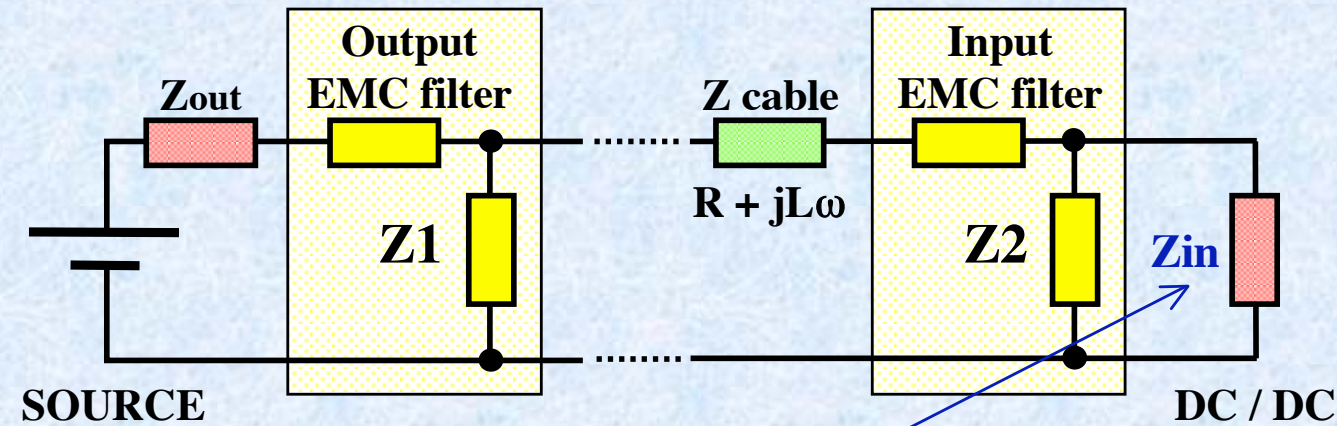The problem of the negative impedance of a DC/DC converter




Risks :


- No Start Up
- Output voltage instability
- Destruction of DC / DC converter

Solutions :

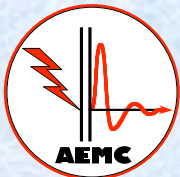- Add a large capacitor at DC / DC input
- Reduce cable inductance (several pairs in //)
- Reduce the converter regulation bandwidth




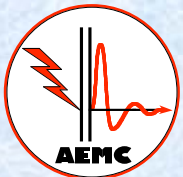- Introduction
- Differential Mode Immunity
- **Differential Mode Emissions**
- Common Mode Emissions
- Electromagnetic Radiations




Some problems of converters harmonics

- Harmonics are generated by non sinusoidal currents. For an electric network, harmonics are a low frequency problem (< 2 kHz and in Differential Mode only).
- Usually, even harmonics are low (because + and – half-waves look the same).
Most of inverters and AC / DC converters without PFC exceed normalized levels.
- Odd harmonics of converters can be severe ($> 50\%$ @ H3 ; $> 30\%$ @ H5).
- For most single – phase converters without PFC on a 3 phase network, the 3rd harmonics (150 Hz) is an “homopolar” current. So, I_{neutral} can exceed I_{phase} .
- Anti-harmonic or active filters are useful for a low power source (electric generator).
- For a high power network, the problem of harmonics is not the voltage distortion but the mastering of cabling protection scheme (cables & circuits breakers).

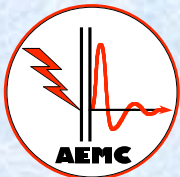

Differential Mode interferences

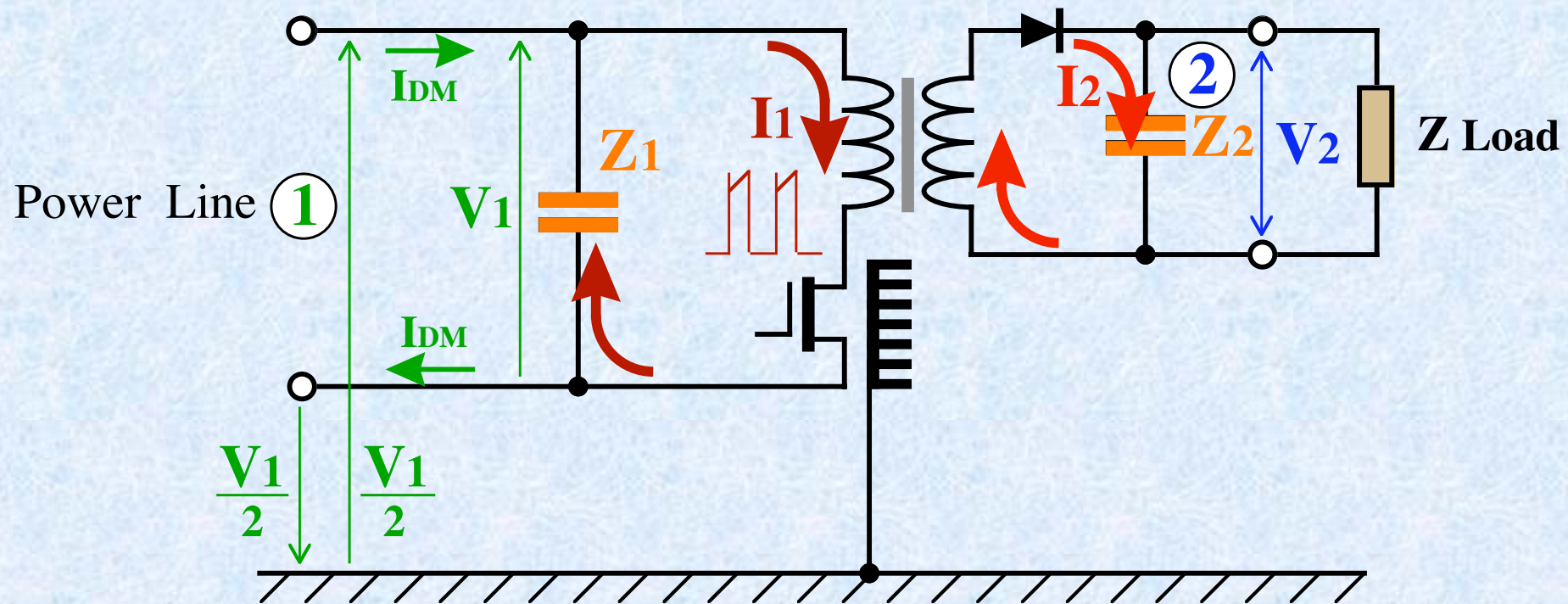


① $V_1 \approx Z_1 \cdot I_1$ (If $Z_{LISN} \gg Z_1$ - Generally, $V_1 = f(F)$)

V_1 is not applied to the secondary, so it does not disturb the load.

② $V_2 \approx Z_2 \cdot I_2$ (If $Z_{Load} \gg Z_2$ - Generally, $V_2 = f(t)$)

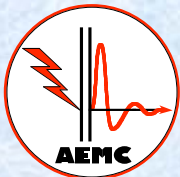V_2 may be disturbing (typically if peak-to-peak $V_2 \geq 1 \text{ V}$)







Differential Mode Emission Spectrum Without Filtering

Converter DM Equivalent Scheme


Switching frequency = F_0

Z capacitor


Transition time = τ_r

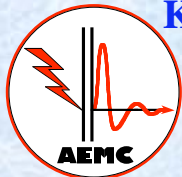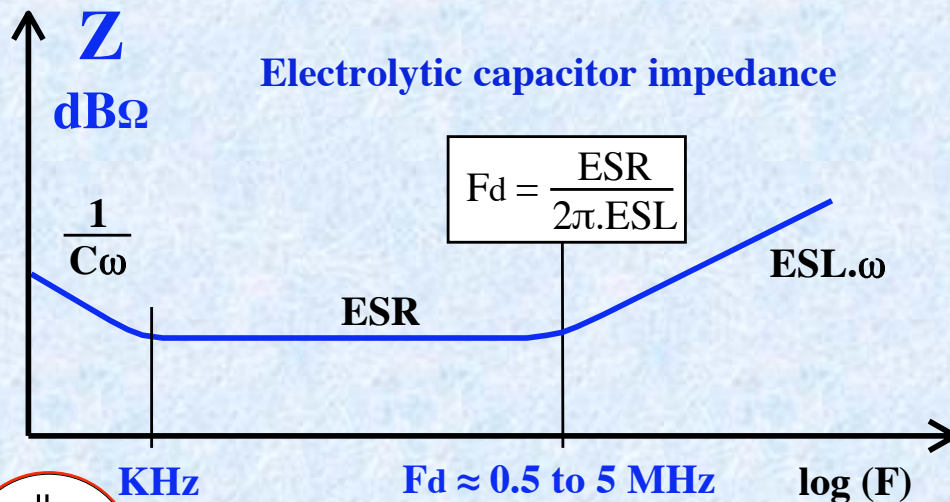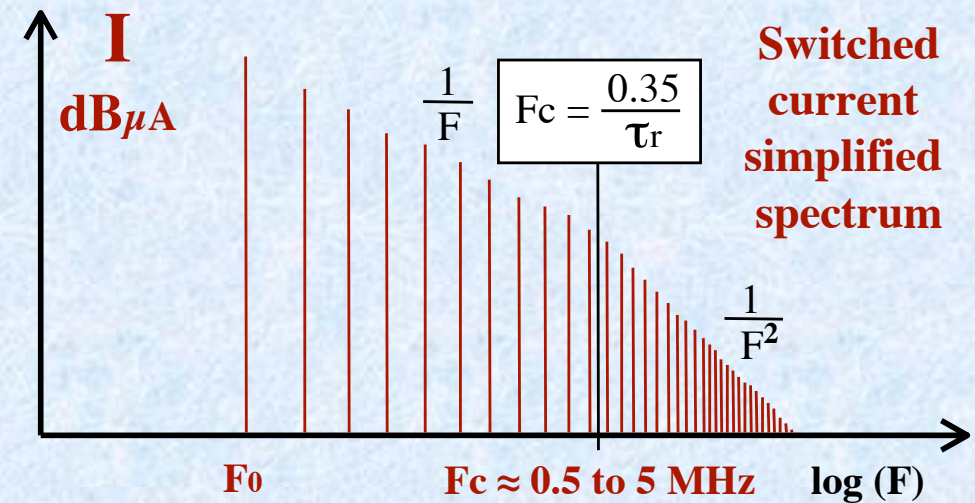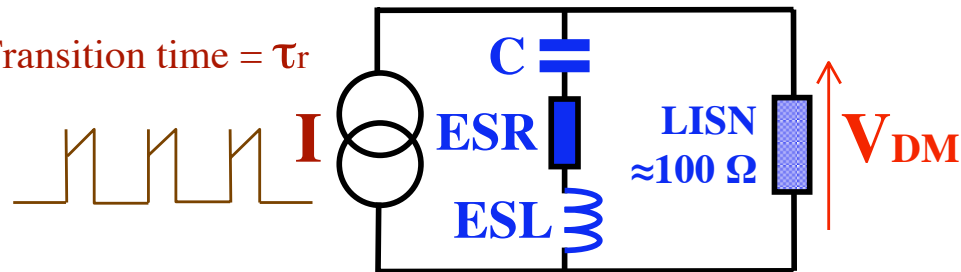



Convolution Result

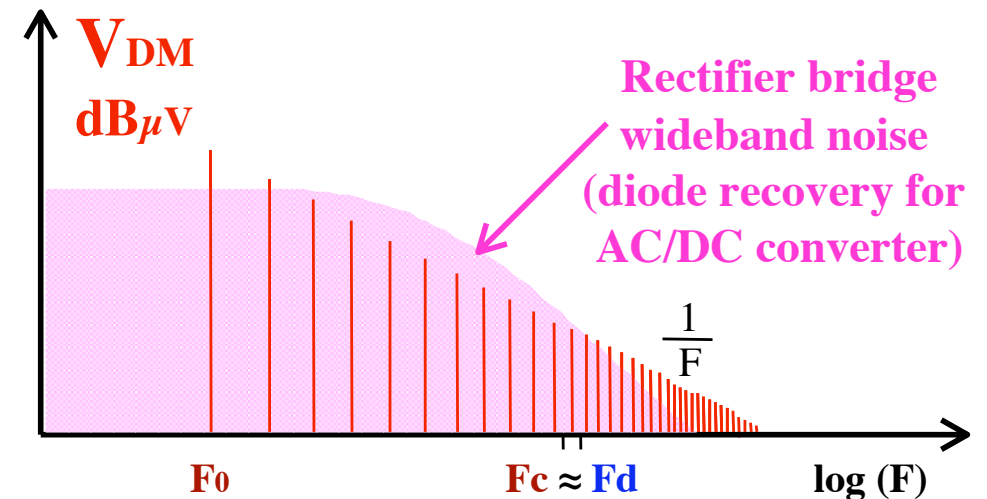

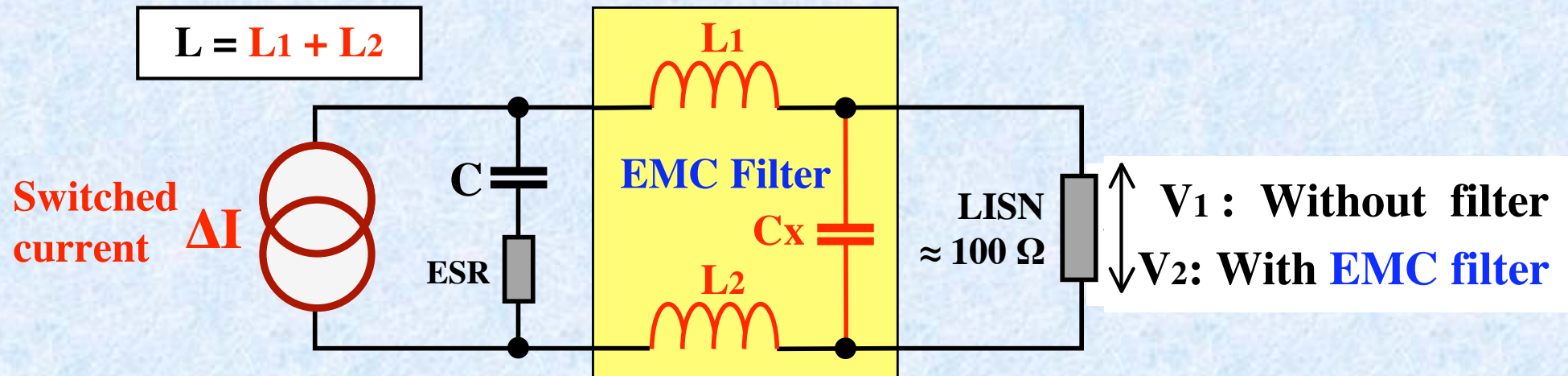
Insertion Loss of a Differential Mode EMC Filter



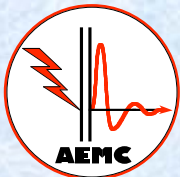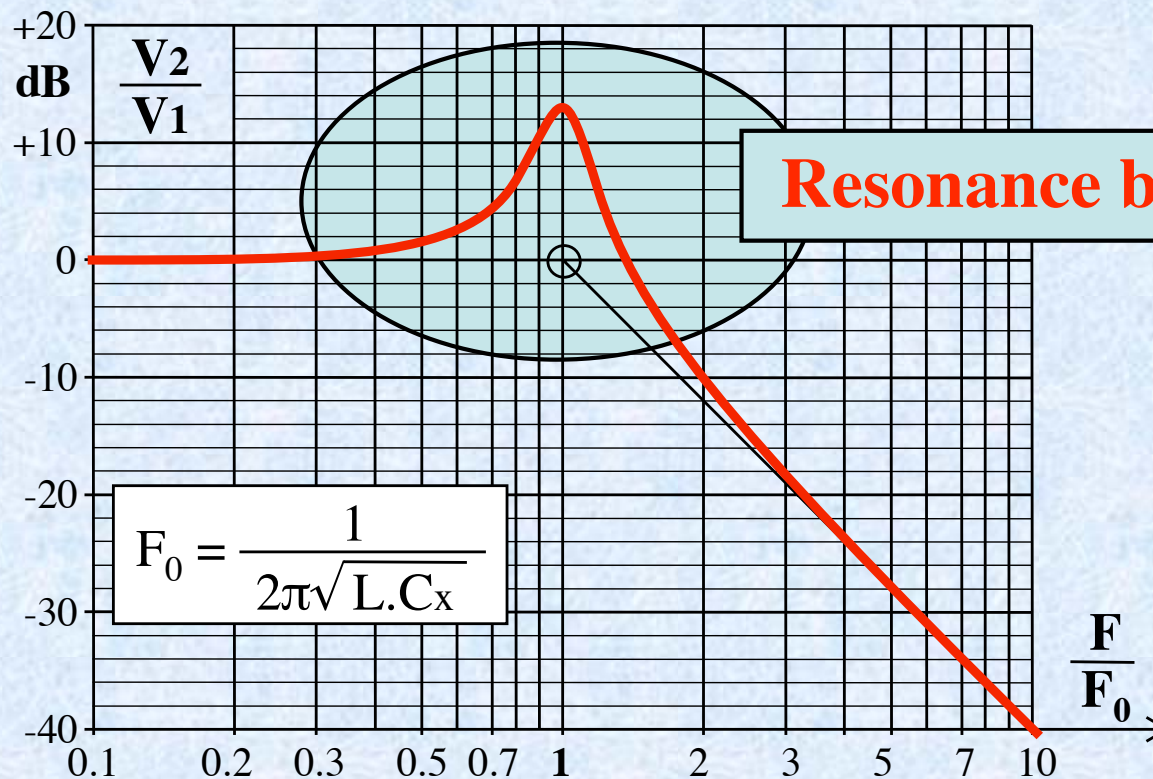
DM equivalent scheme of a converter with an **EMC filter**




Traps of a Differential Mode EMI filter

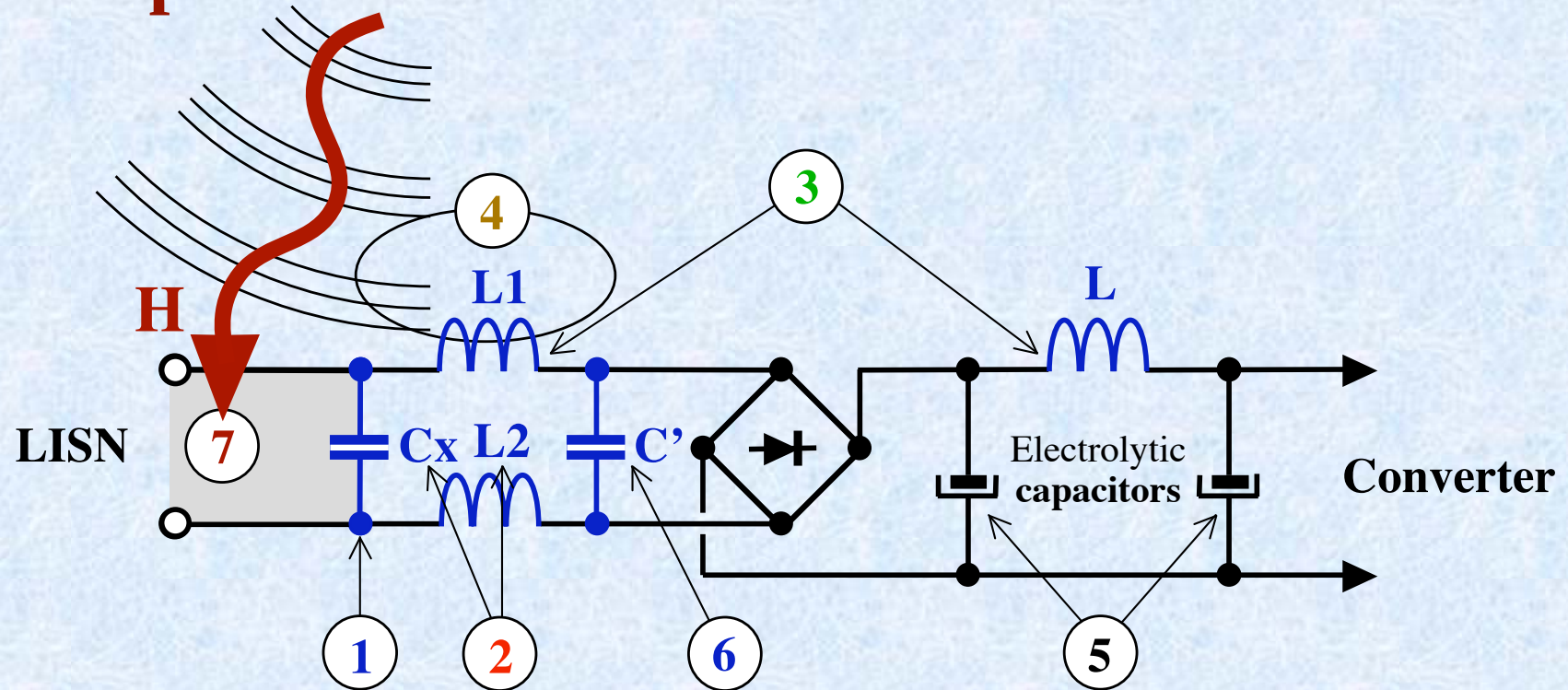



- 1 - Choose the proper structure (to mismatch the impedances)
- 2 - Choose $(L_1 + L_2) \times C_x$ value so that $F_{\text{resonance}} < \text{lowest frequency to filter}$
- 3 - Verify that no inductance saturates at max current (Max P & Min V)
- 4 - Limit H field coupling to leakage inductance (in air) of L_1 & L_2
- 5 - Safety margin necessary to compensate electrolytic caps ESR dispersion
- 6 - Add C' as needed to reduce wideband recovery noise of rectifier bridge
- 7 - Limit H field-to-loop coupling to avoid parasitic voltage pick-up.

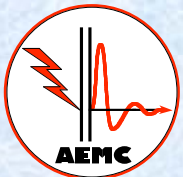

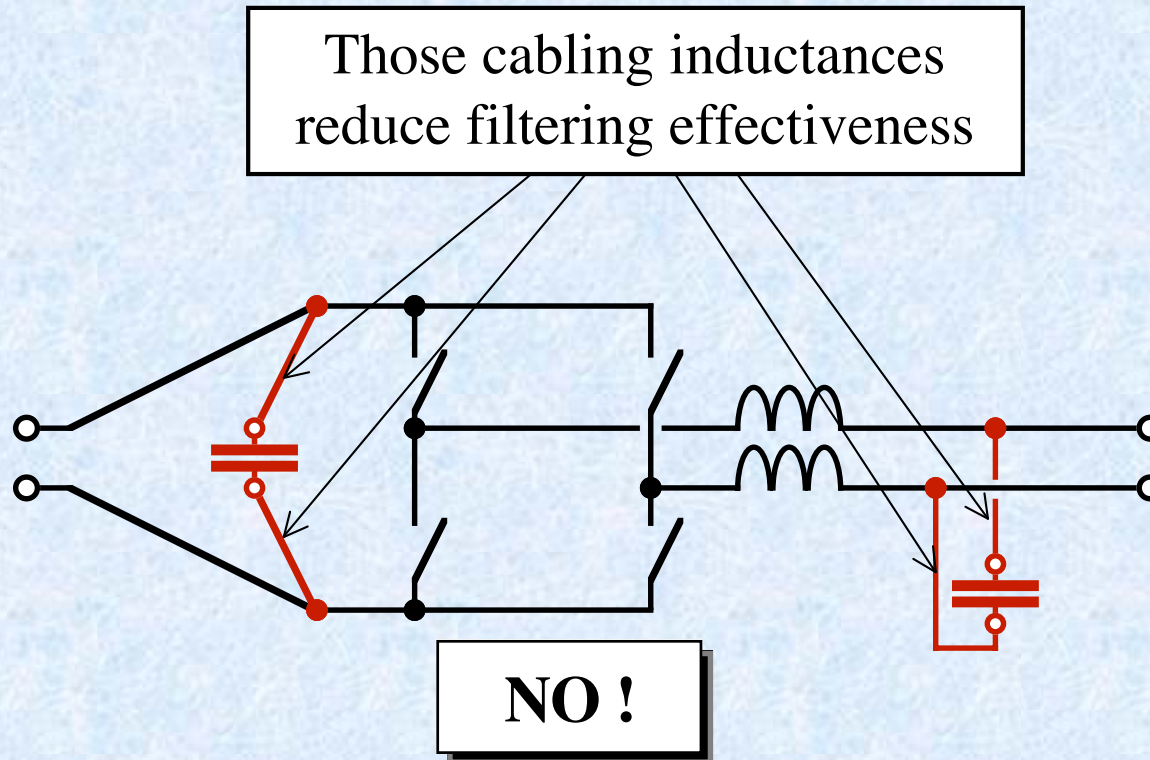
Take care of Differential Mode cabling...



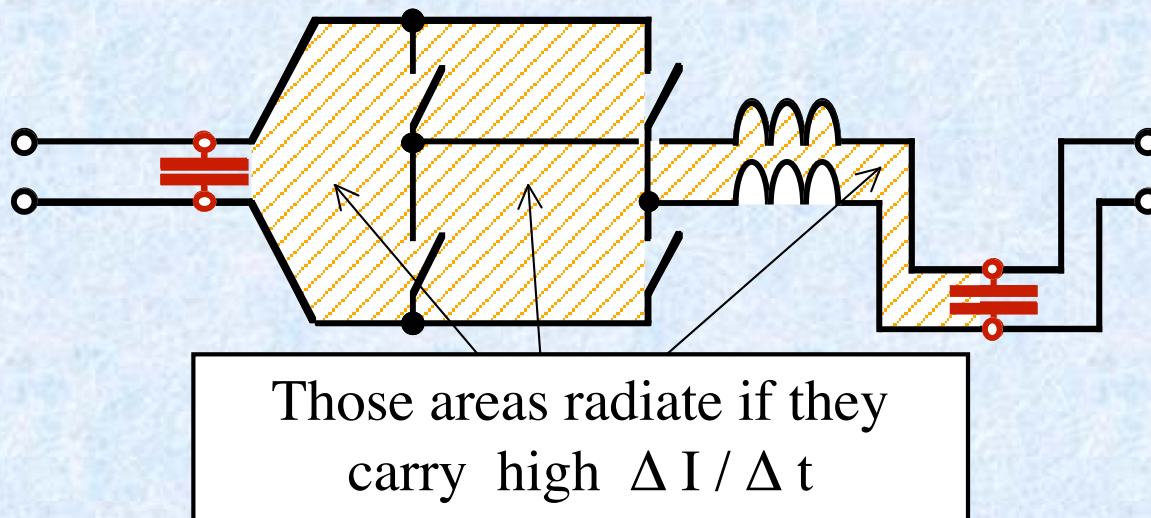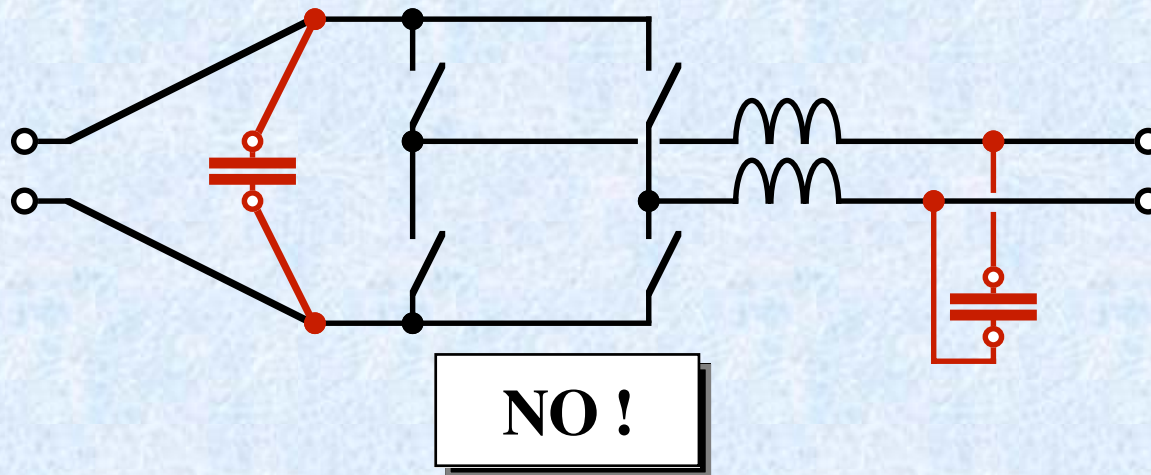
Take care of Differential Mode cabling...



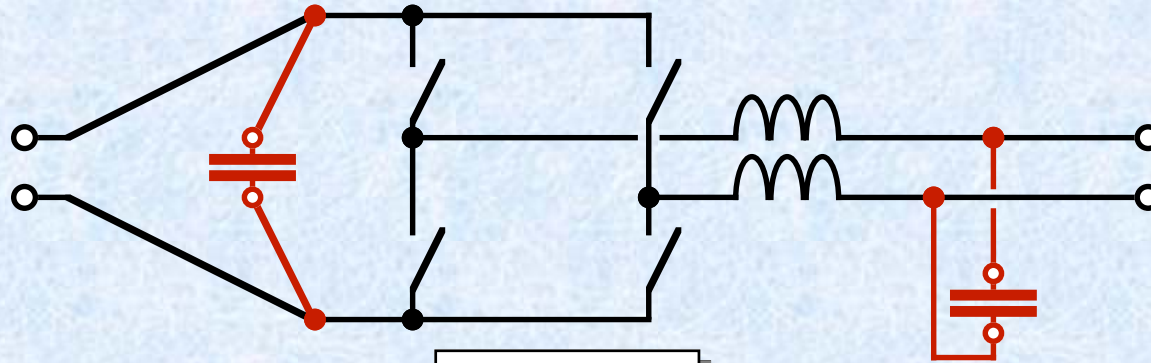
Take care of Differential Mode cabling...



NO !

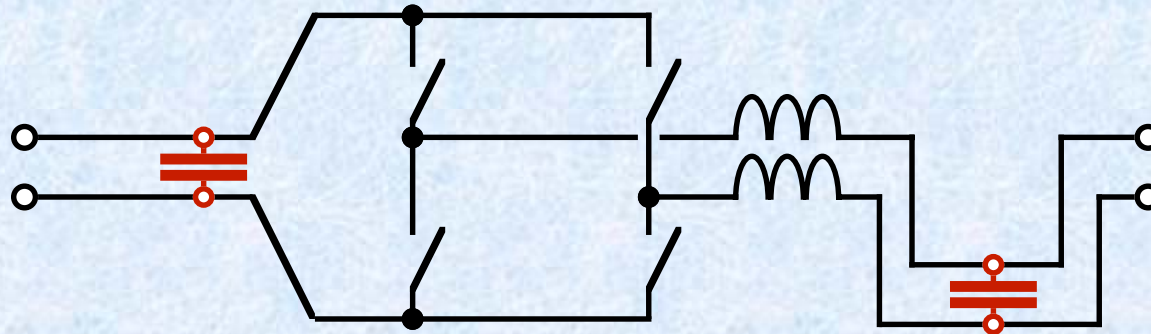


BETTER

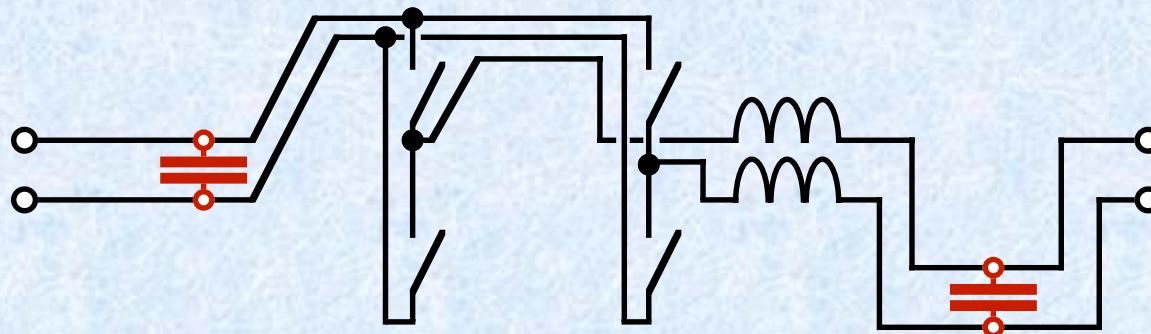


BEST !

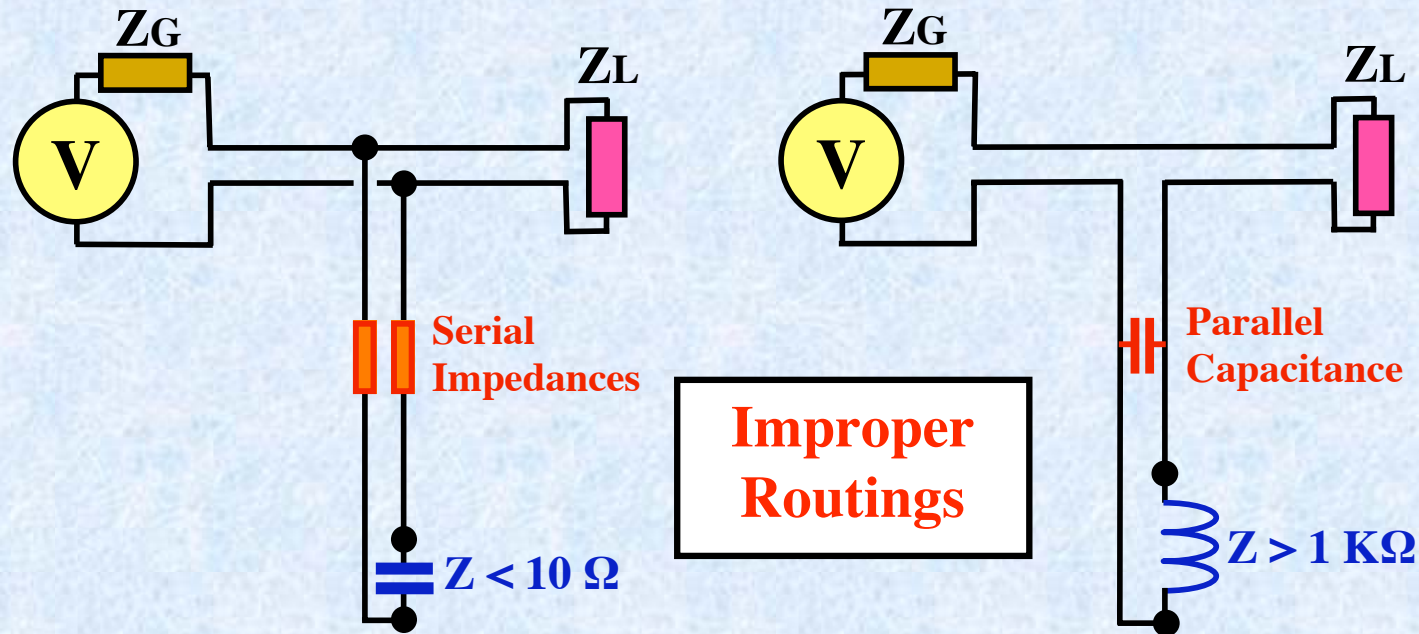
How to reduce cabling parasitic impedances...





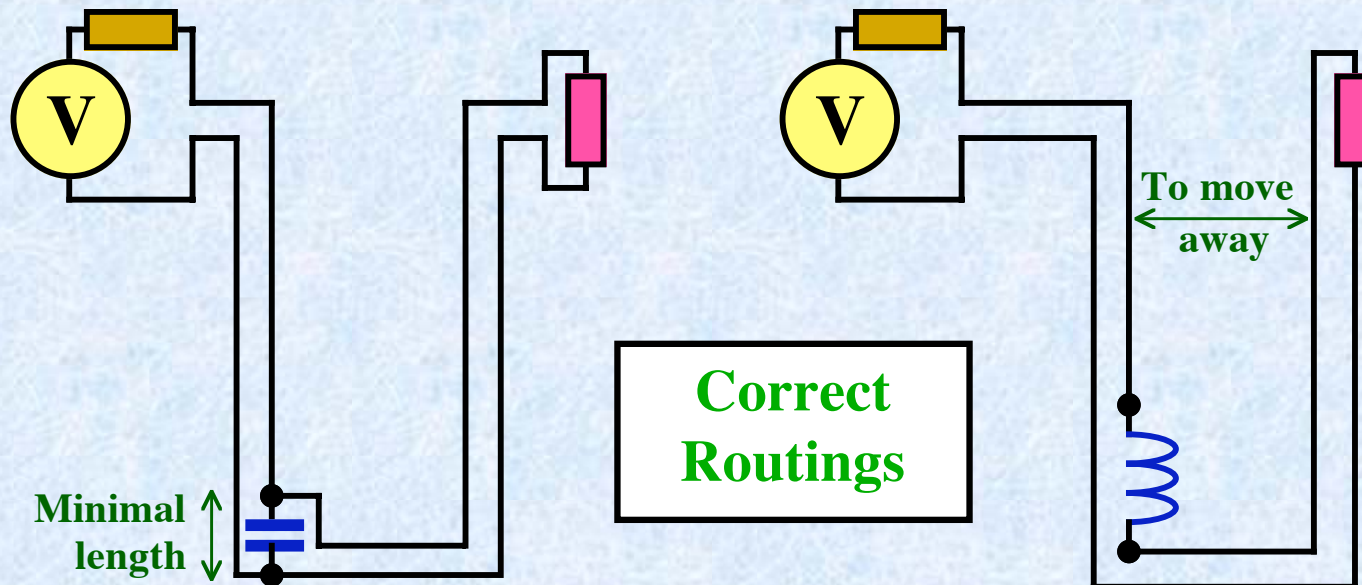
To reduce the cabling areas is necessary, but insufficient



How to measure Output Ripple...

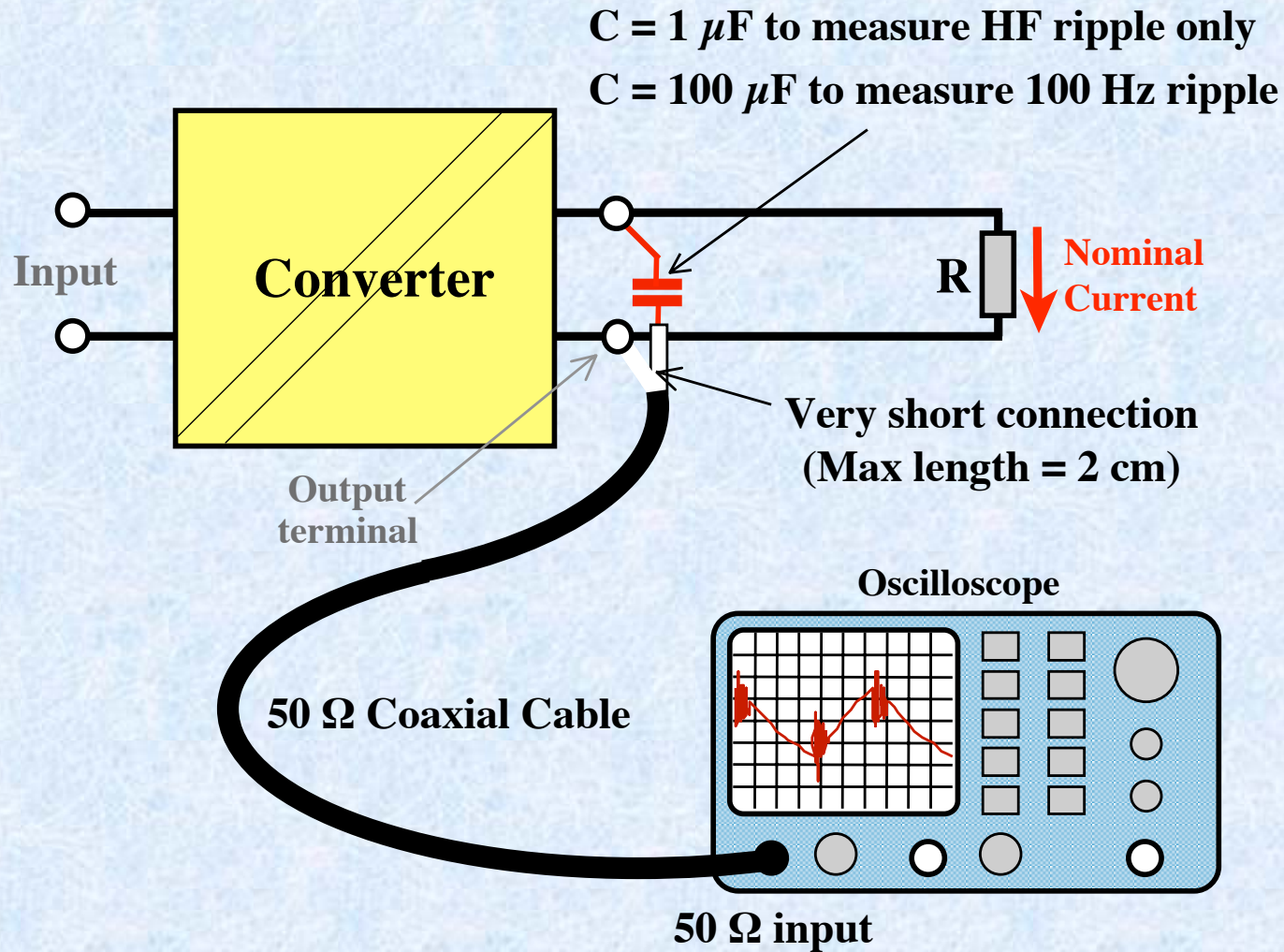

How to analyse Output Ripple

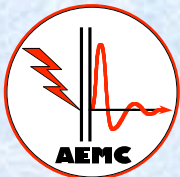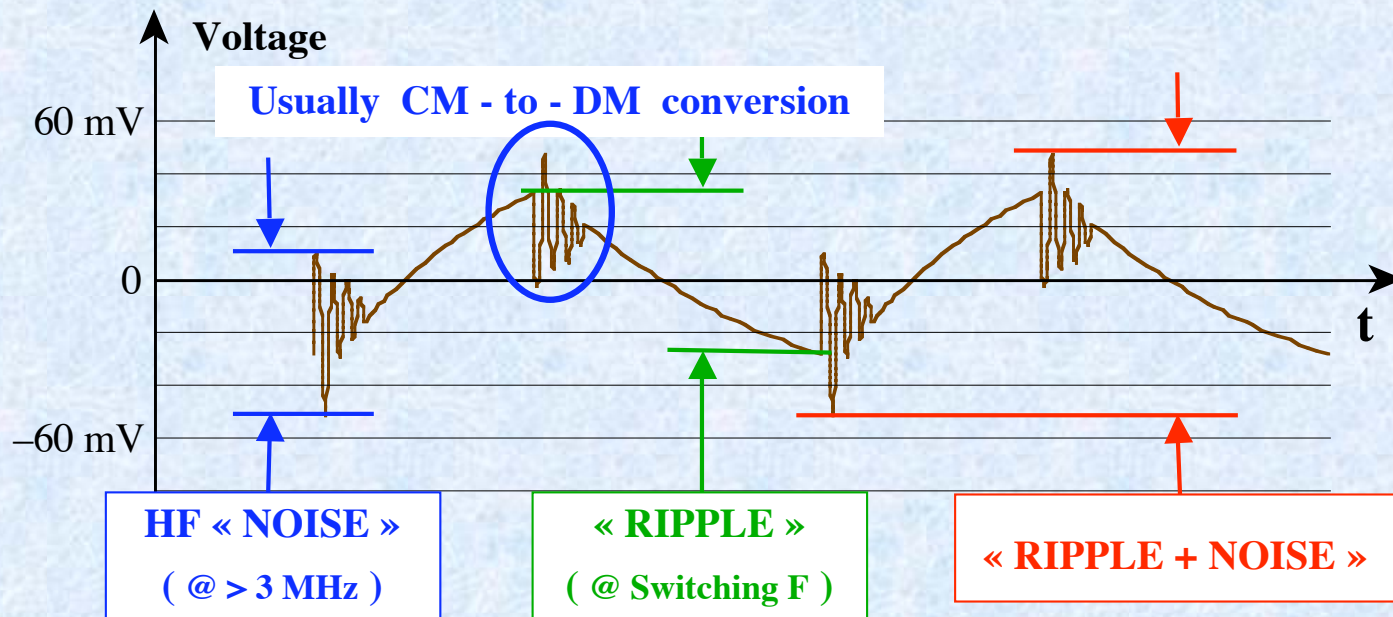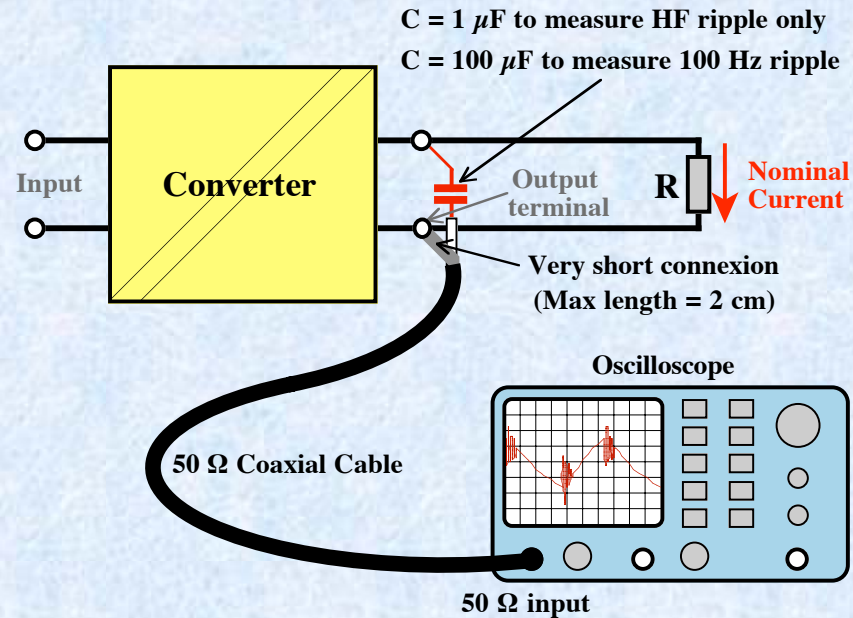

10 mV : Excellent


—

100 mV : Average


—

1 V : Excessive

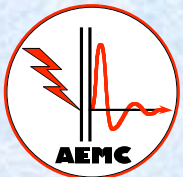- Introduction
- Differential Mode Immunity
- Differential Mode Emissions
- **Common Mode Emissions**
- Electromagnetic Radiations



Common Mode interferences

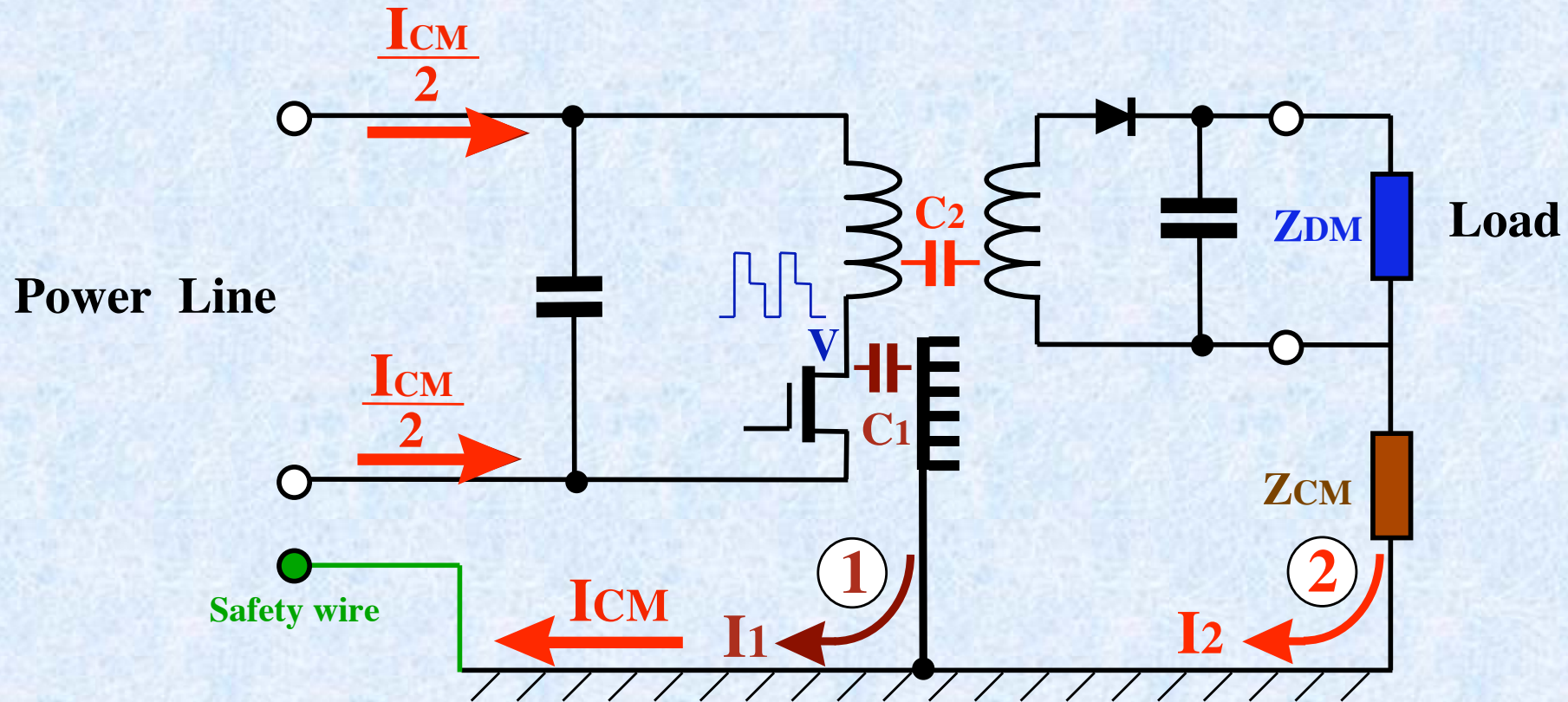


① $I_1 = C_1 \cdot \Delta V / \Delta t$

I_1 doesn't circulate through the load, so it is little disturbing.

② $I_2 \approx C_2 \cdot \Delta V / \Delta t$ (but possibly modified by Z_{CM})

I_2 can circulate through the load, so it may be very disturbing.

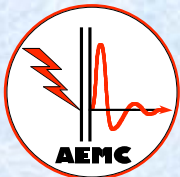Measured total CM current : $I_{CM} = I_1 + I_2$




Common Mode Emission Spectrum Without Filtering




Converter CM Equivalent Scheme

Switching Frequency = F_0


Transition Time = τ_r

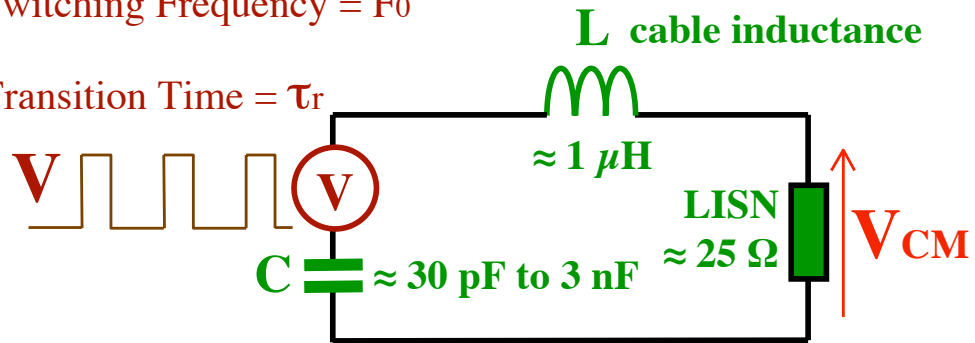

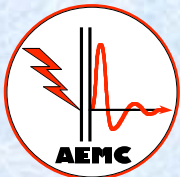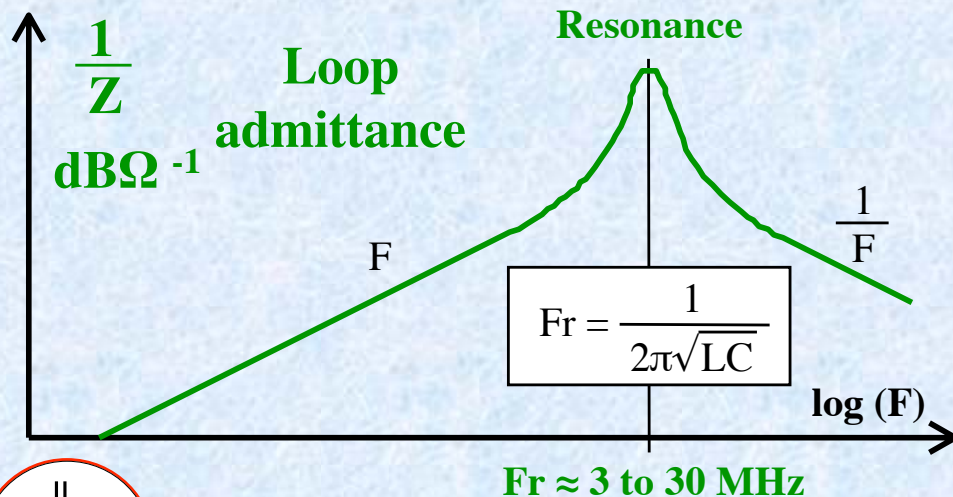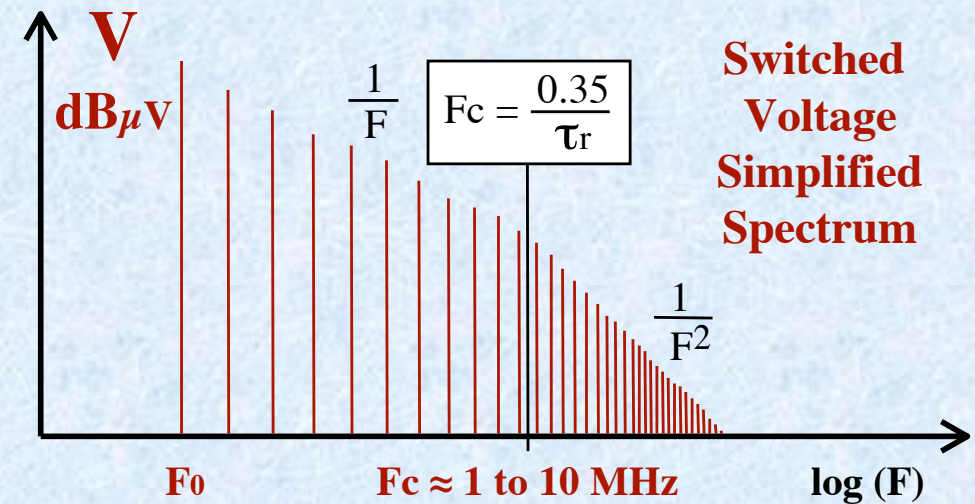
C : Parasitic cap between “hot conductors” & ground





Convolution Result

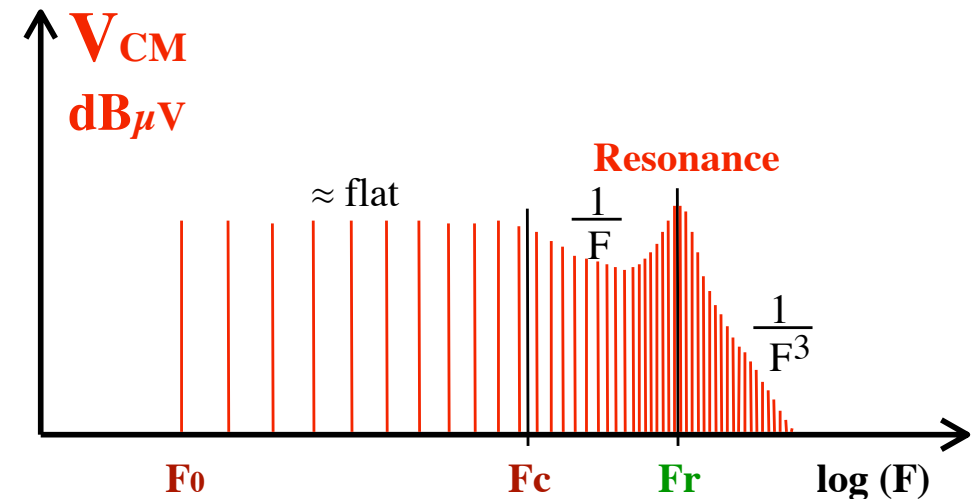

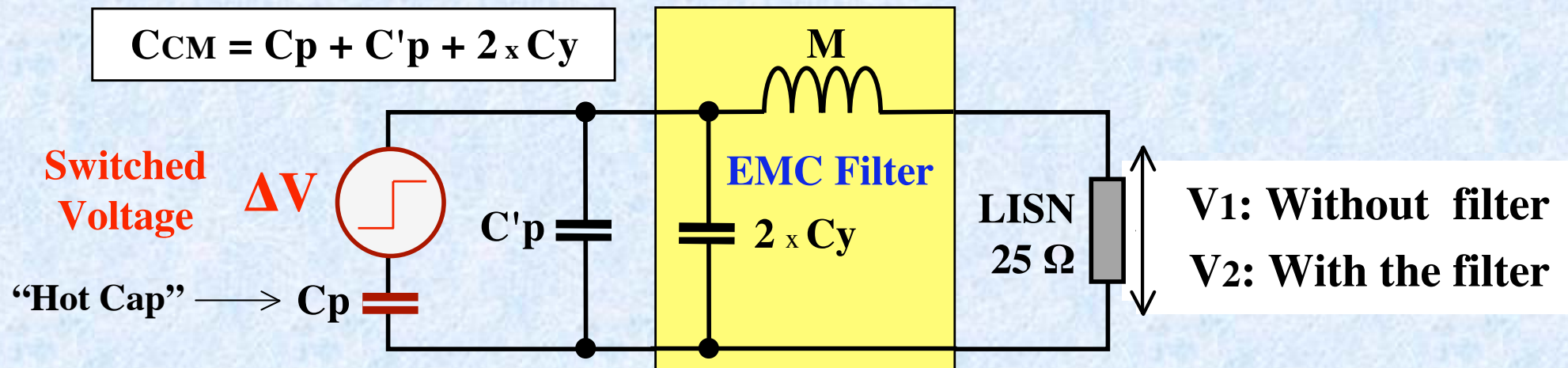Insertion Loss of an EMC Common Mode Filter




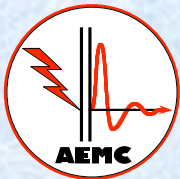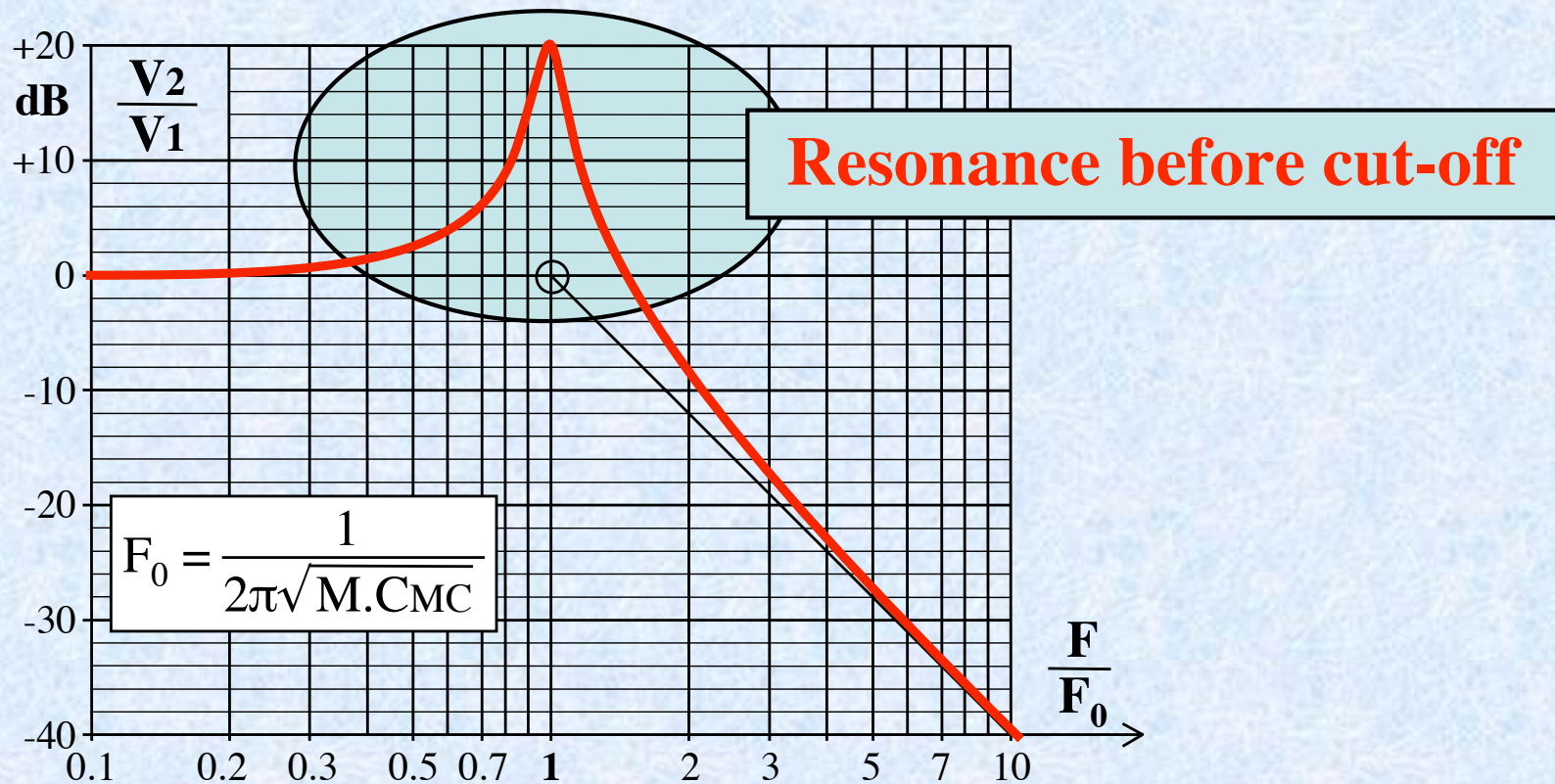CM equivalent scheme of an isolated converter with a filter




The 3 cases of Primary-to-Secondary Common Mode


Metallic chassis

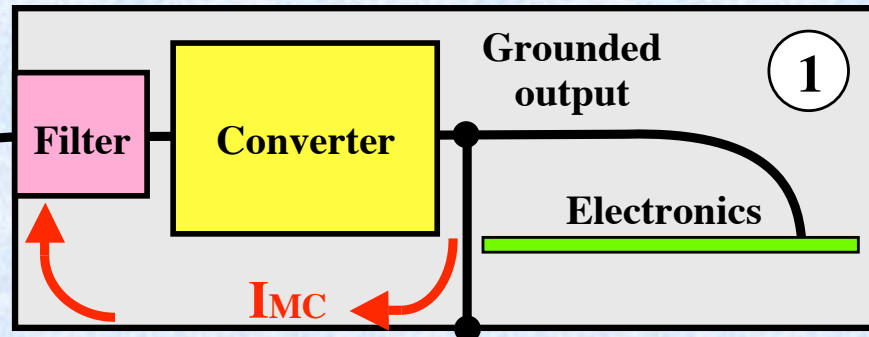

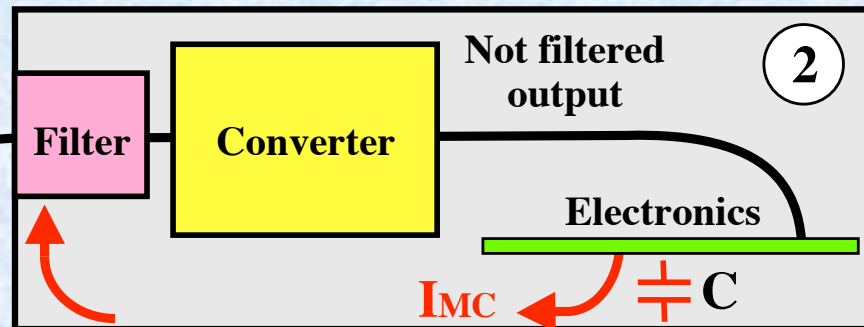- No disturbance outside of the chassis
- No CM noise in electronic circuits
- EMC filter easy to optimize




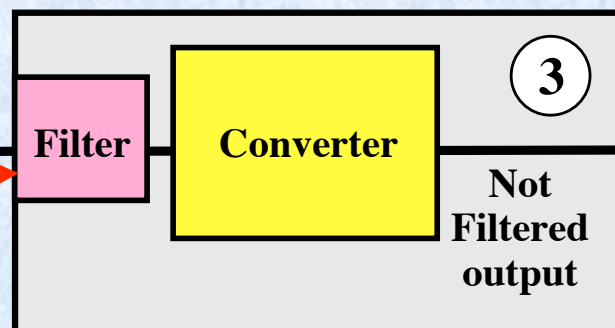- No disturbance outside of the chassis
- CM Noise through electronic circuits
- EMC filter more difficult to optimize





- EM radiations outside of the chassis
- Input filter impossible to optimize
- The output cable must be shielded or filtered


Load

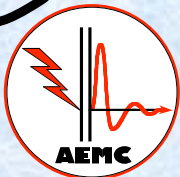

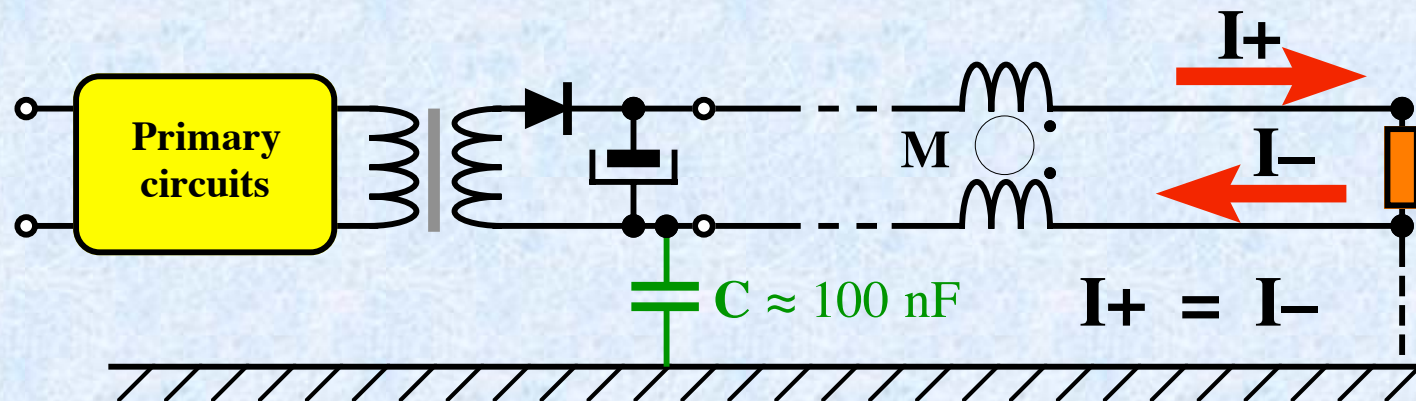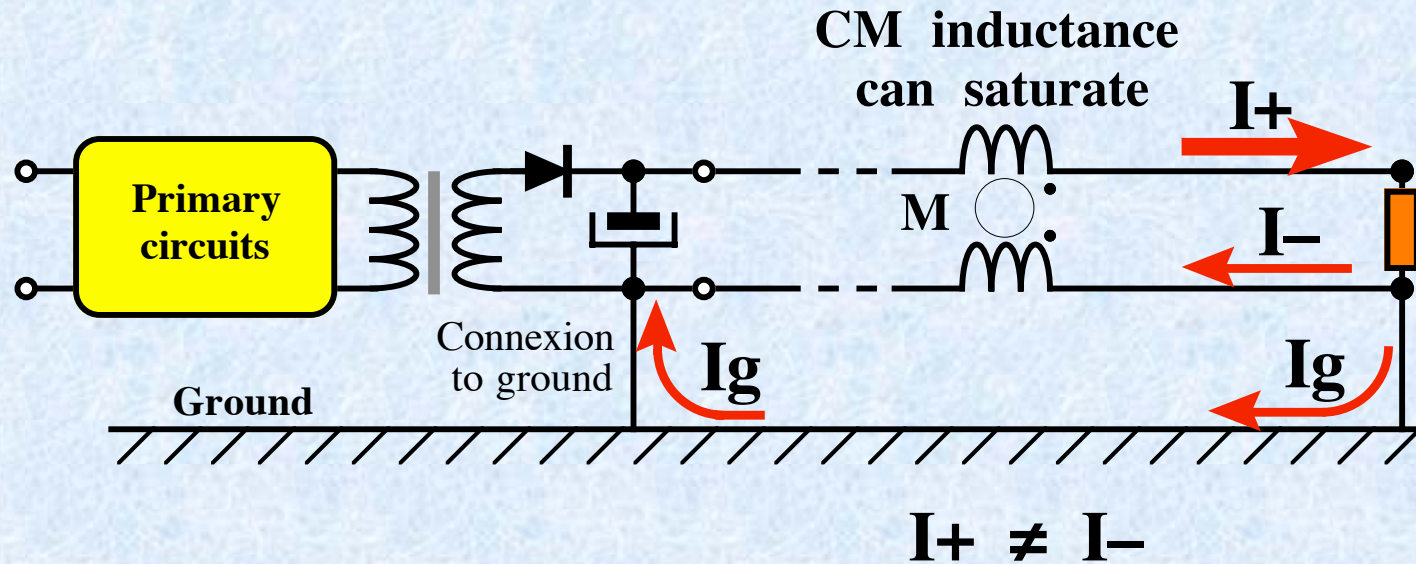
To float or not to float the output, that's the question...



A (nearly) universal solution

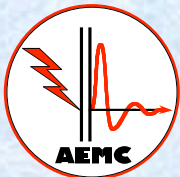


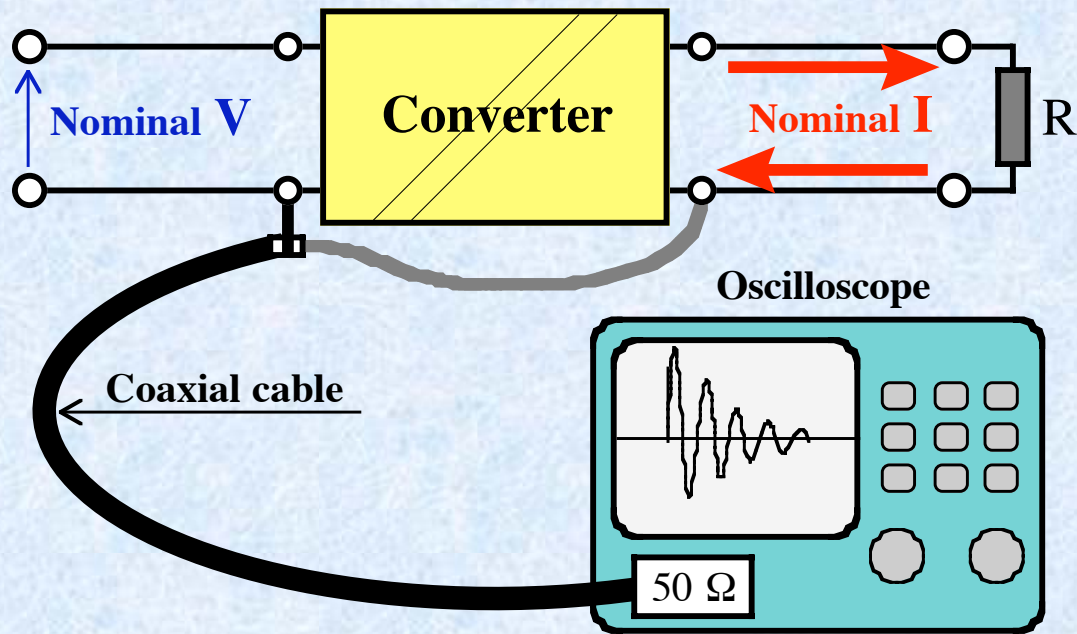How to measure Primary - to - Secondary C. M. current ?



Time measurement


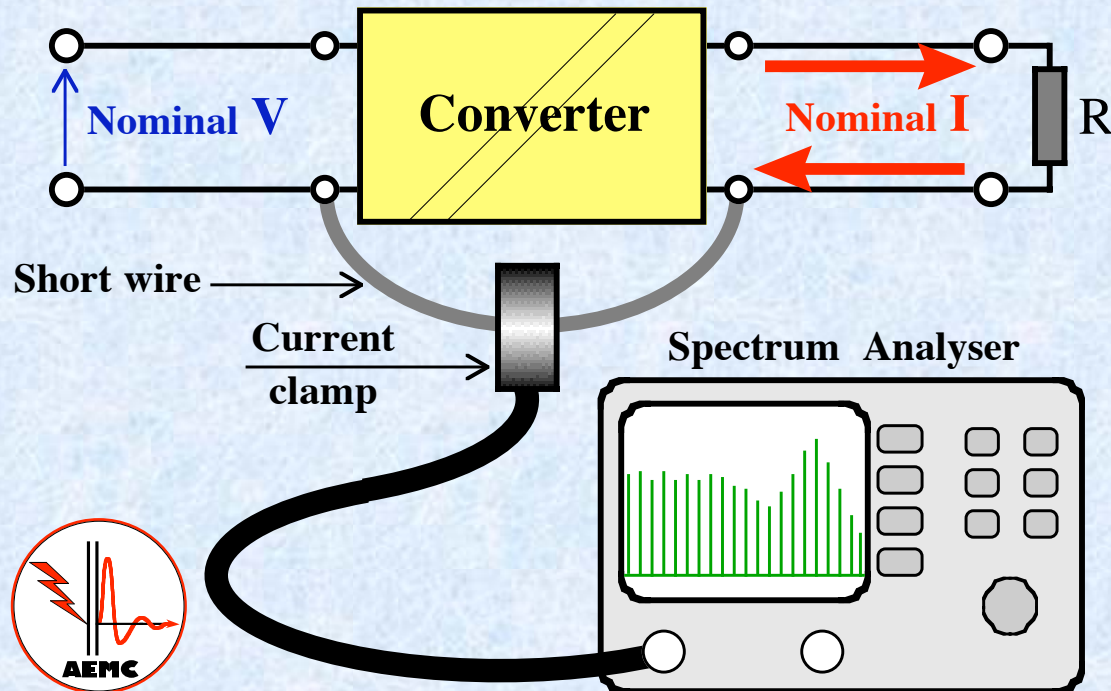
- 50 mV/mA sensitivity
- 100 MHz bandwidth
- 1 mA peak-peak = Excellent
- 10 mA peak-peak = Average
- 100 mA peak-peak = Excessive




Frequency measurement

- 9 or 10 kHz RBW, Peak detection
- Span : 0.1 to 50 MHz (100 MHz)
- 10 dB μ A = Excellent
- 30 dB μ A = Average
- 50 dB μ A = Excessive

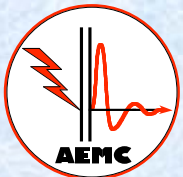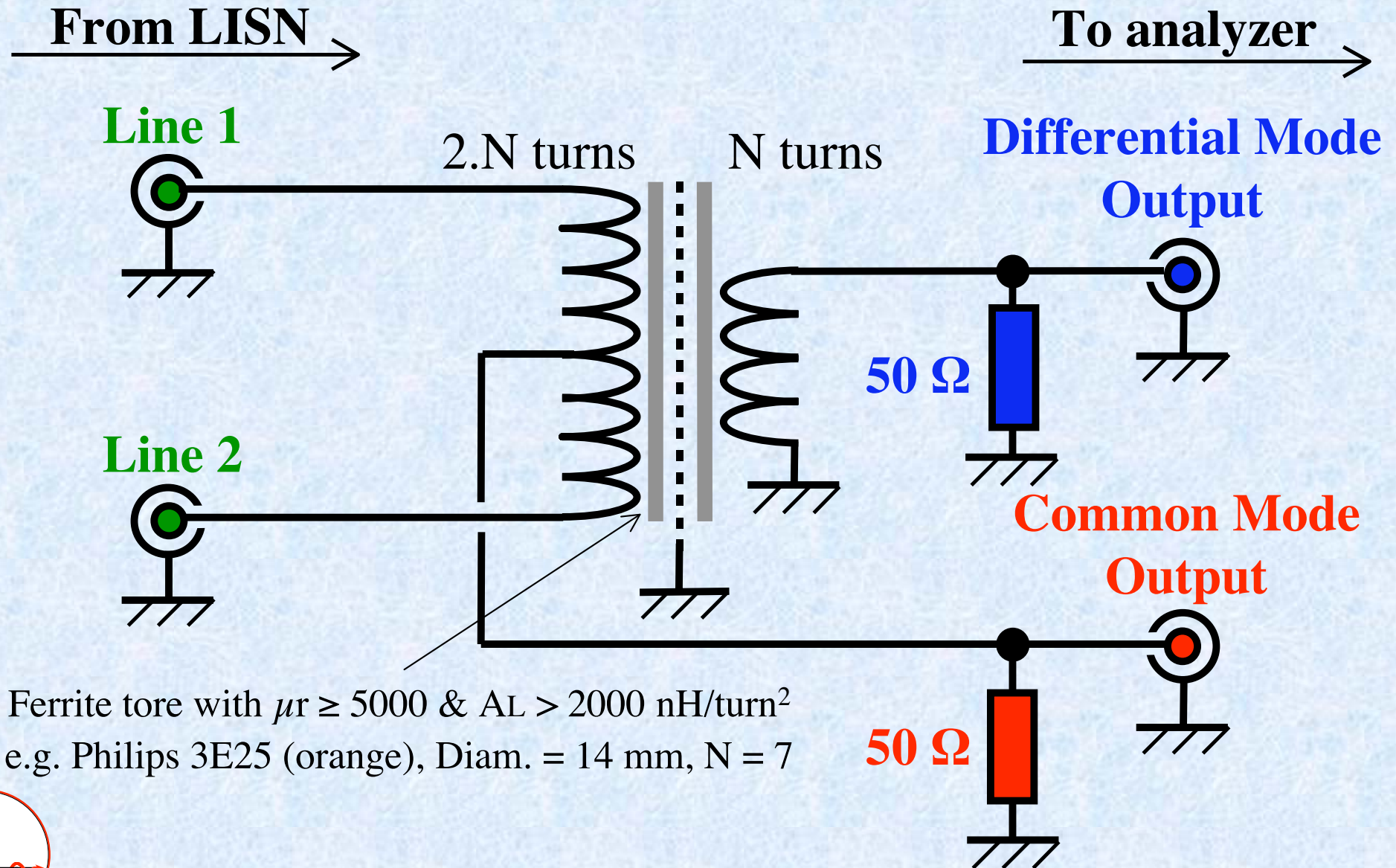
This simple “CM / DM SEPARATOR” reduces by 10 + the time and difficulty to optimize a single-phase EMC filter



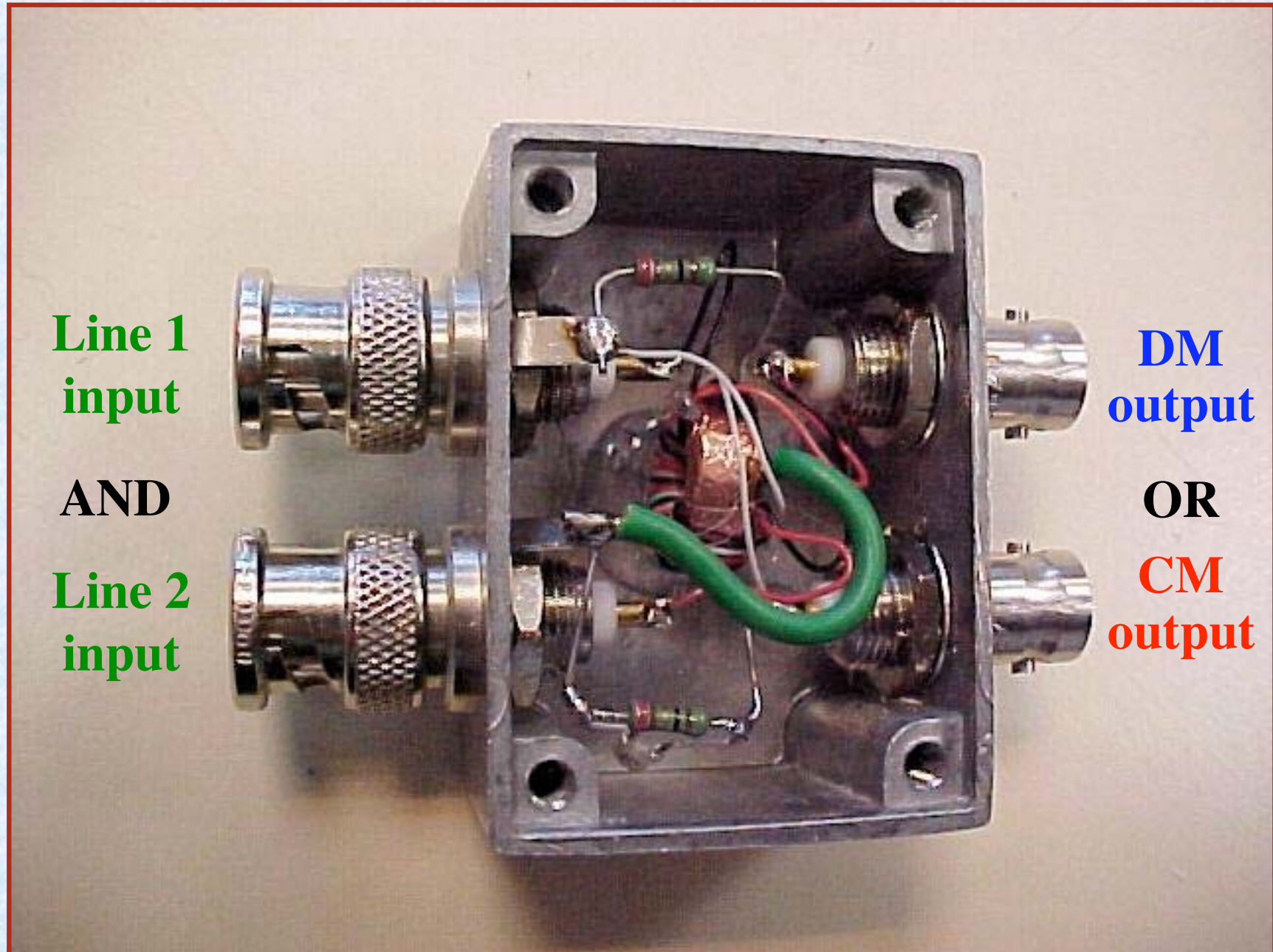
Practical realisation of a “CM / DM SEPARATOR”



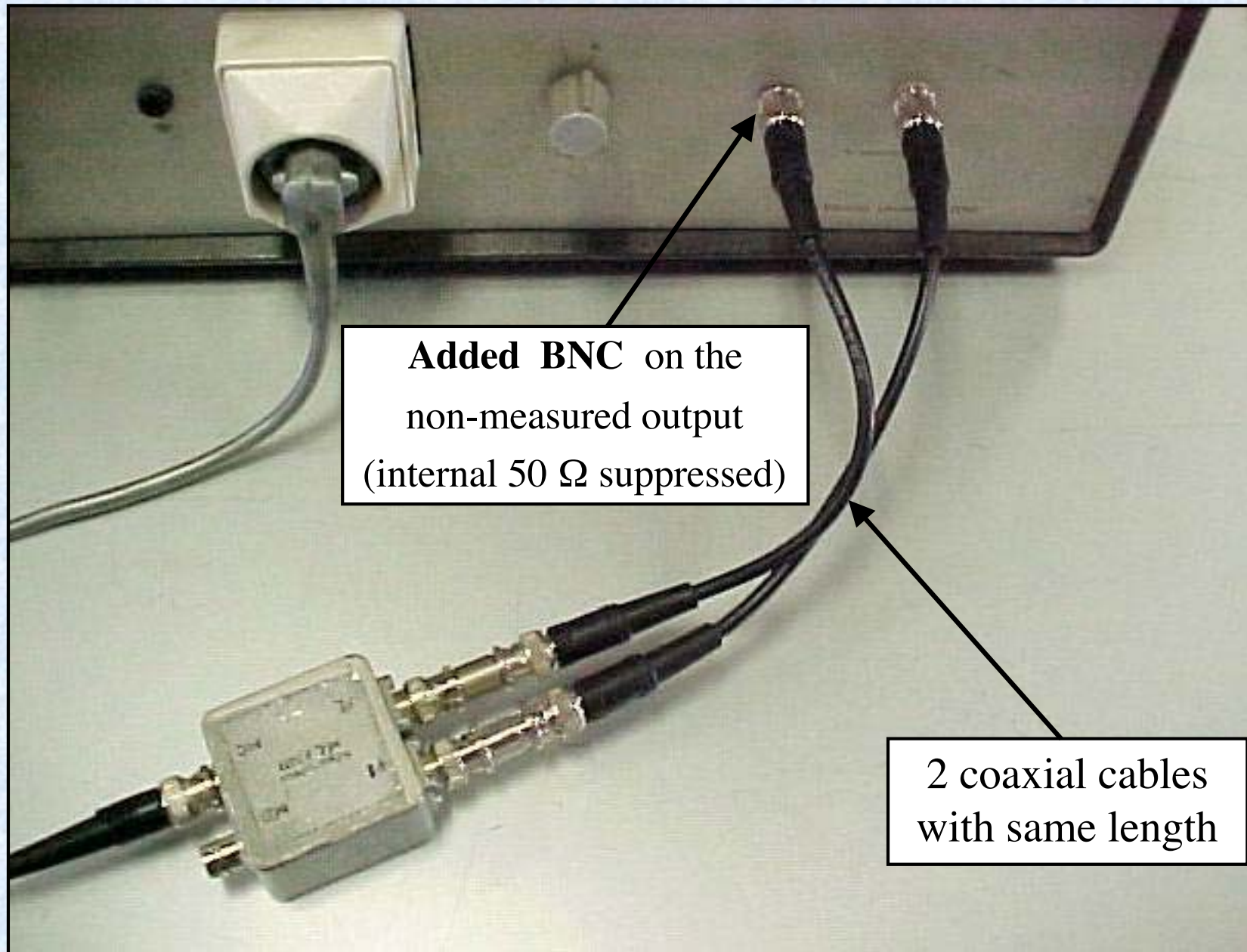
CM / DM separator adaptation on a commercial LISN



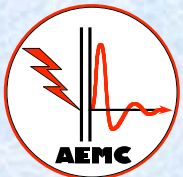- **Introduction**
- **Differential Mode Immunity**
- **Differential Mode Emissions**
- **Common Mode Emissions**
- **Electromagnetic Radiations**



Sources of Electromagnetic Radiations

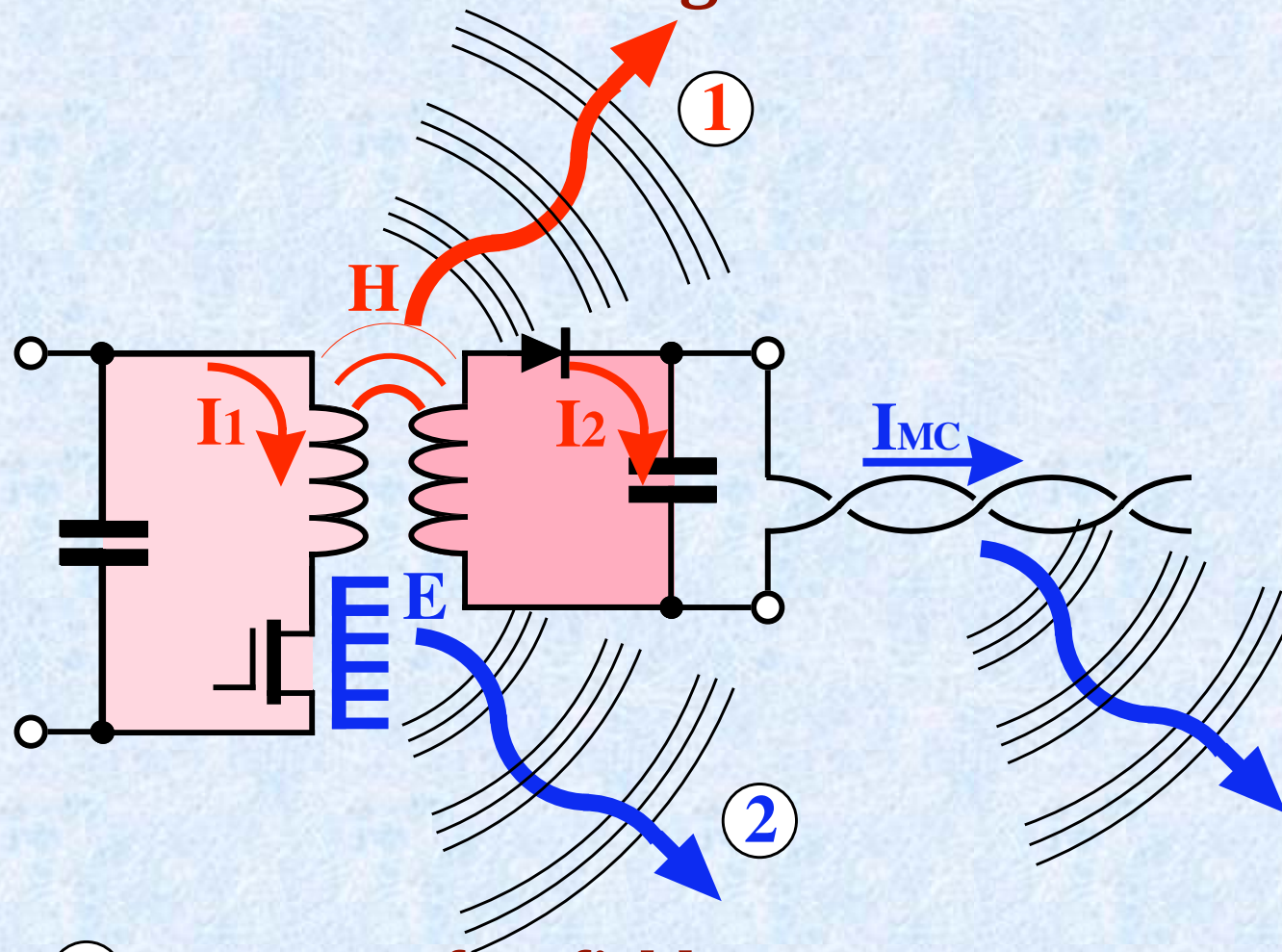

① Sources of H field :

Leakage fields of windings


Secondary loop areas

Primary loop area



② Sources of E field :

High $\Delta V/\Delta t$ conductive parts (Heat sink, ferrite core...)

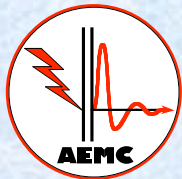HF insufficiently filtered cables (e.g. output cable)




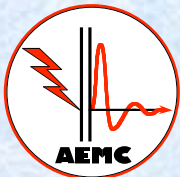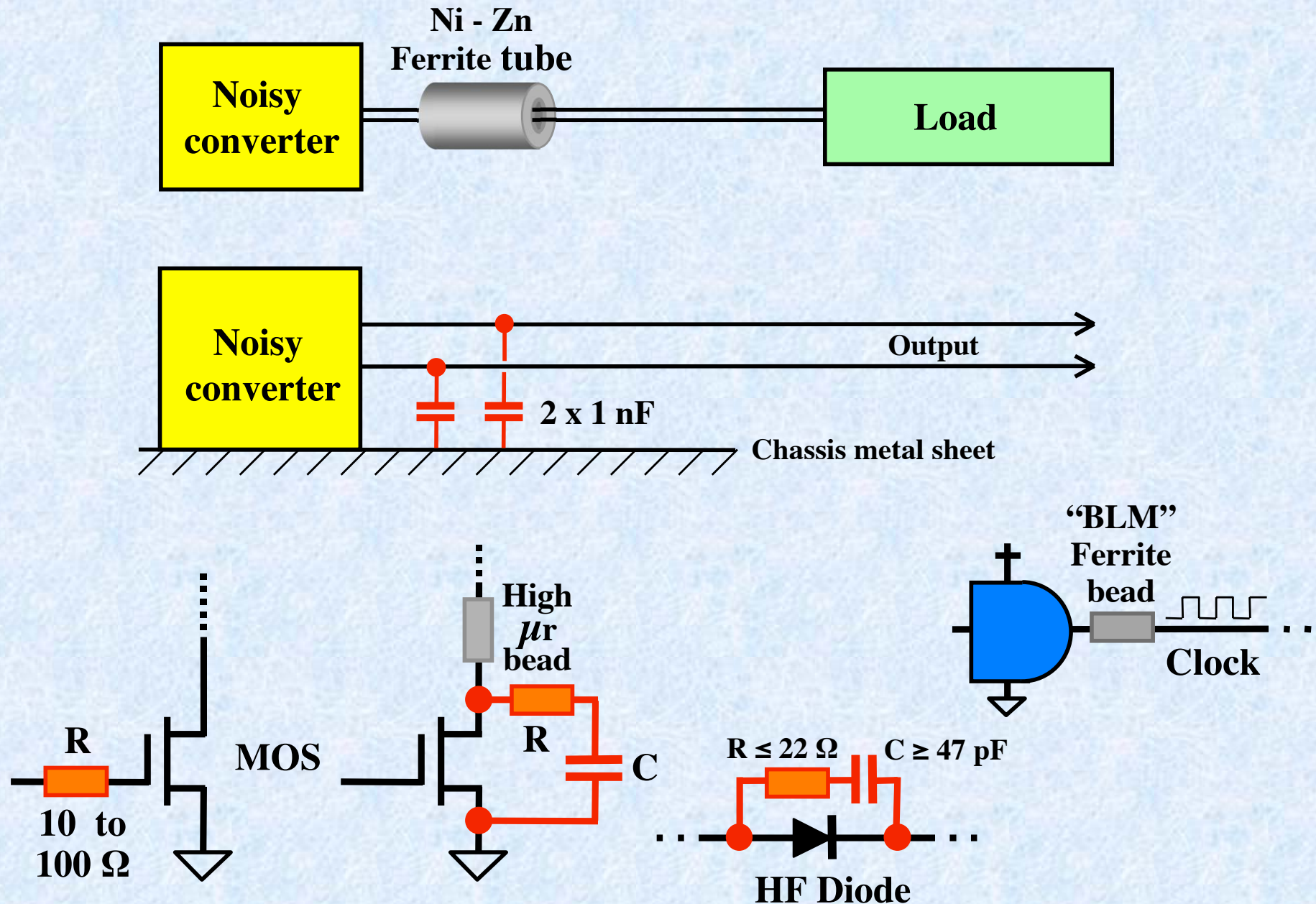HF solutions must be installed close to the sources



Even small converters (few W) can be very noisy (I/O CM & radiation)


Ground Loop : Definition & Effects

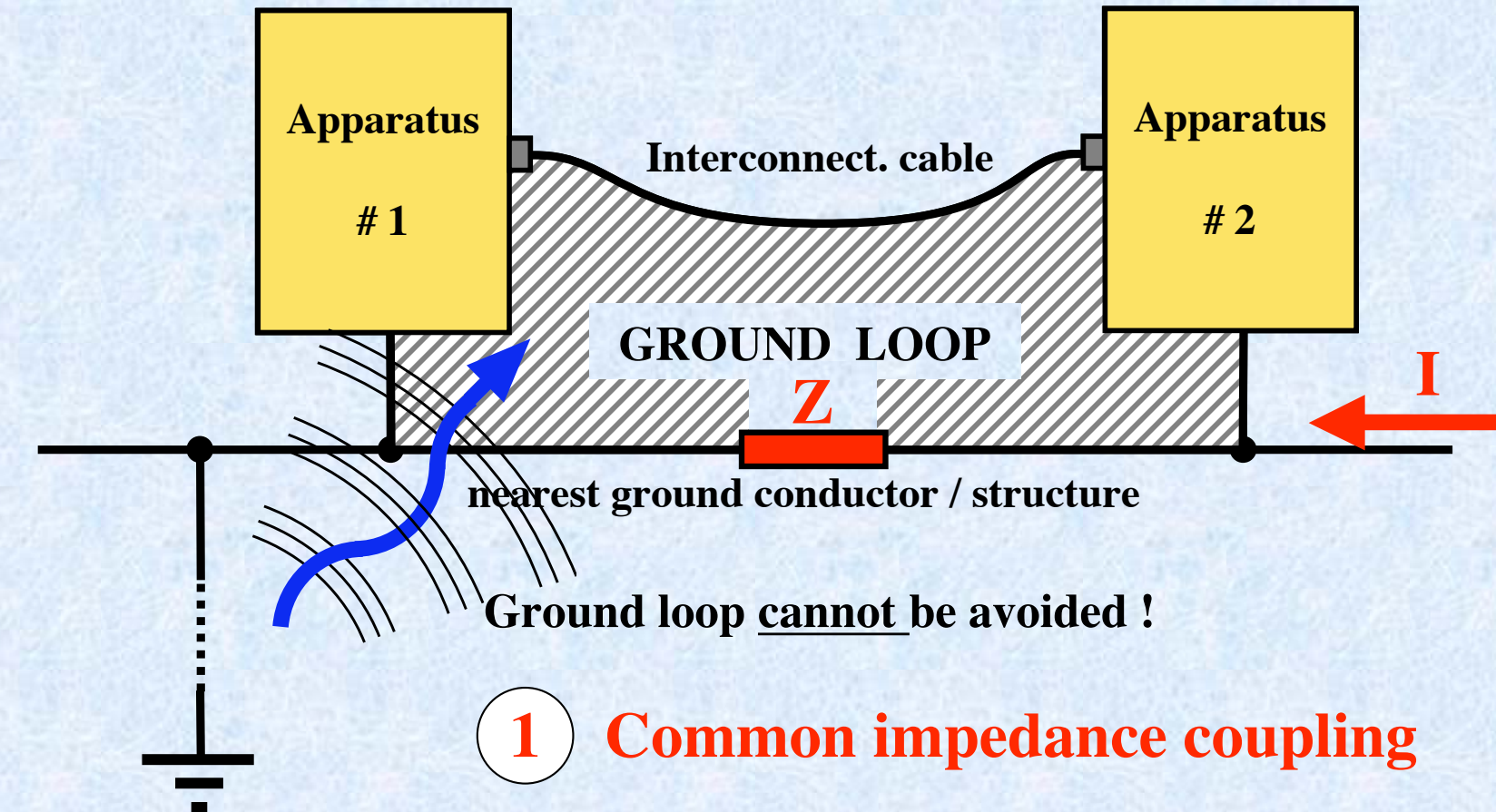


Earth impedance
does not matter

1 Common impedance coupling


2 Field - to - Loop coupling

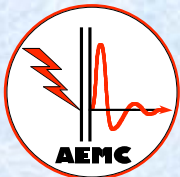


Star Grounding : Principle & Reality

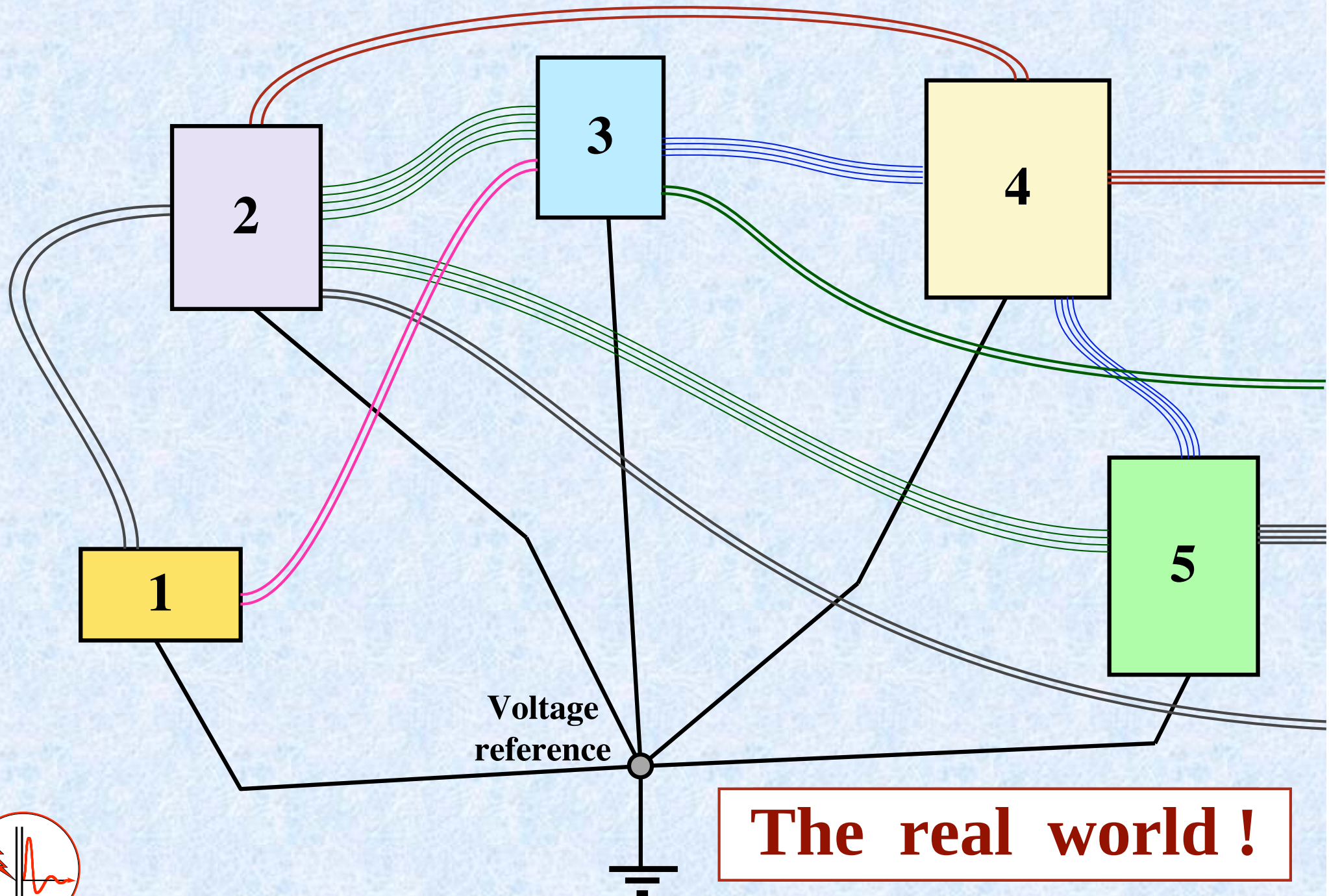



Ground Grid : Definition & Effects

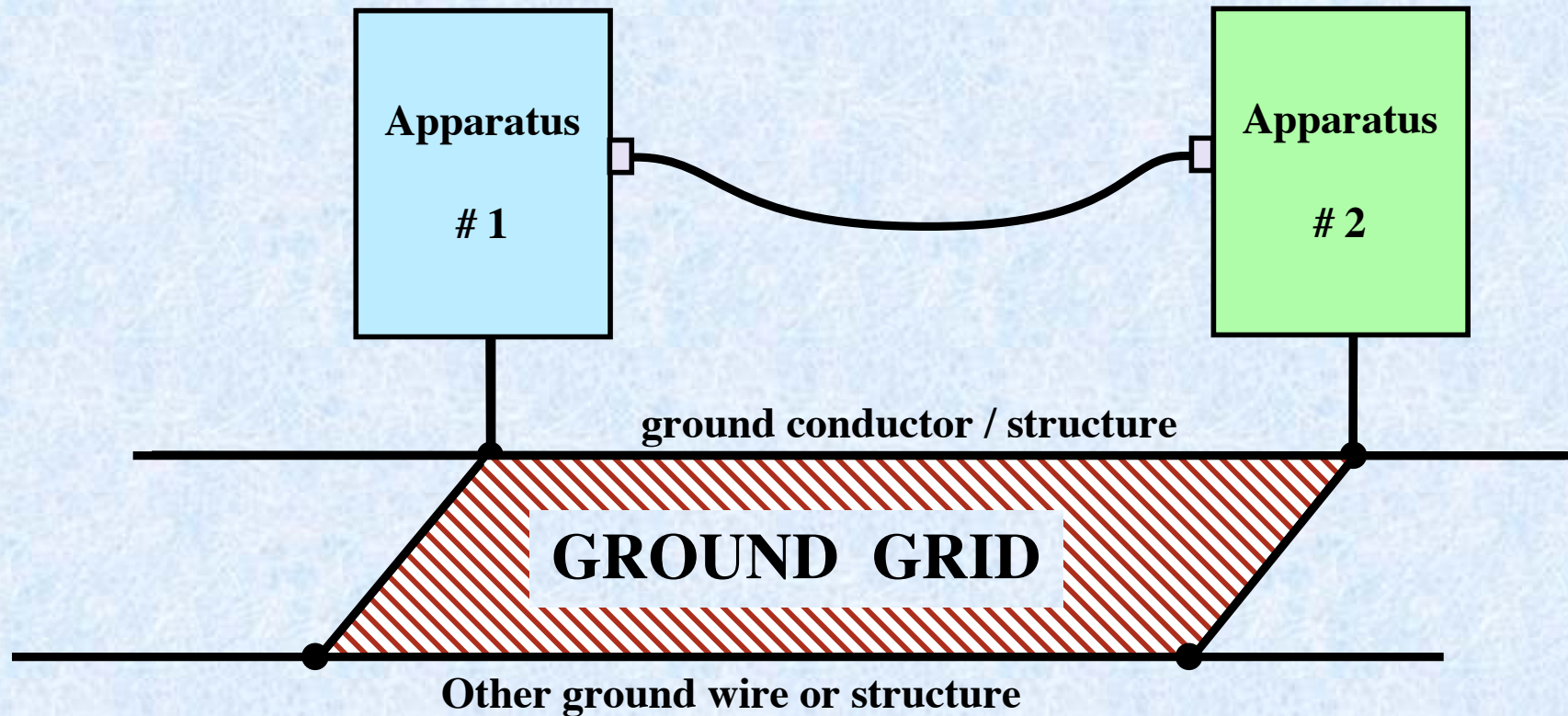

How to improve immunity ?

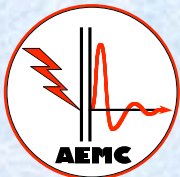

Ground Grid : Definition & Effects

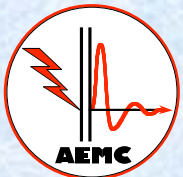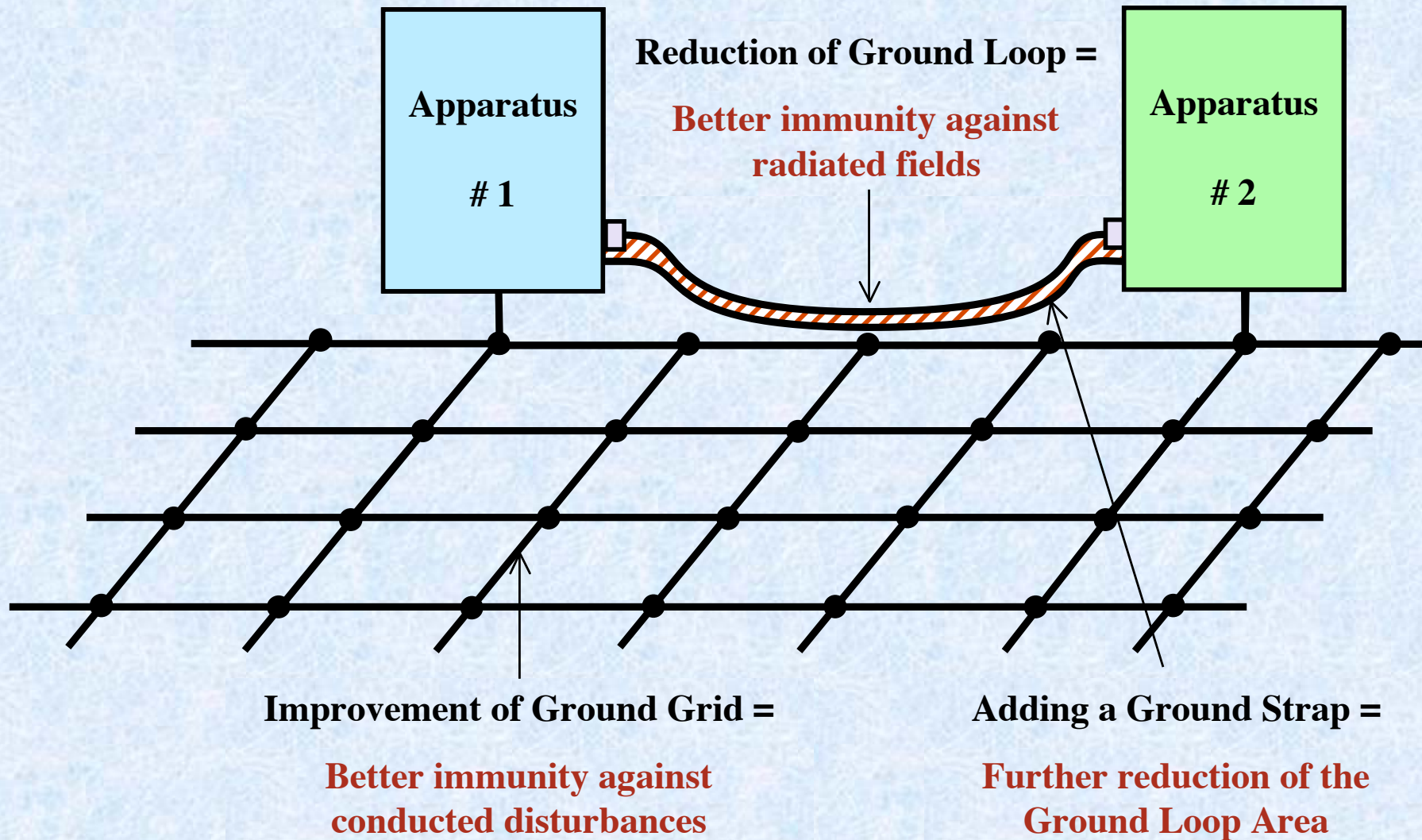


A GROUND GRID is highly recommended !

Where to connect the shielded cables braid ?

- Any power cable : At both ends, to chassis ground, without pigtail.
- High frequency coax : At both ends, to chassis ground, without pigtail.
- Digital link (except coaxial Ethernet): At both ends, to chassis ground...
- High impedance source ($> 10 \text{ k}\Omega$): At both ends, to chassis ground...
- Any cable inside an equipment : At both ends, to chassis ground...
- Any outer shield (not signal return): At both ends, to chassis ground...
- Low voltage signal cable, with low frequencies to transmit, with a low impedance source, in a noisy environment, without balanced transmission (bad CMRR): **At one end only**


... But then good immunity will be hard to achieve !

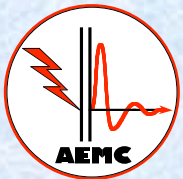Avoid aluminium foil with a drain wire (without braid).



Please, let us remember...

- EMC is not black magic (Just simple physics...)
- Some measurement equipments are required
- Usually, only simple equipments are sufficient
- It's good to be experienced (& confident enough)
- It's important to understand how system works
- It's useful to methodically analyse what happens
- It's efficient to foresee and simplify EMC problems
- It's necessary to know the orders of magnitudes
- It's politically effective to be persuasive (& smiling)
- It's essential never to become discouraged !...

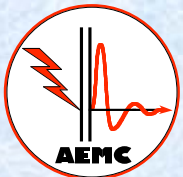

Questions ?

