

Simple Class A Amplifier

A 10-W design giving subjectively better results than class B transistor amplifiers

by J. L. Linsley Hood, M.I.E.E.

0.15% THD at 1KHz and 10 Watts RMS

<http://www.tcaas.btinternet.co.uk/jlh1969.pdf>

.DEFINE PRMS(X) RMS(V(X))*RMS(I(X))

